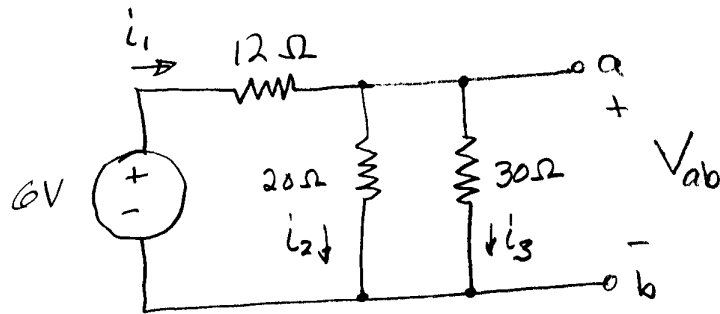


Physics 116A Fall 2004: Exam 1

11/03/2004


Closed book and notes except for one 8.5 x 11 in sheet of paper. Show reasoning for full credit. Complex quantities are in **boldface**, e.g., $H(s)$. Many problems ask for numerical answers. Be sure to put your name on all pages submitted. There are 4 problems and 100 points.



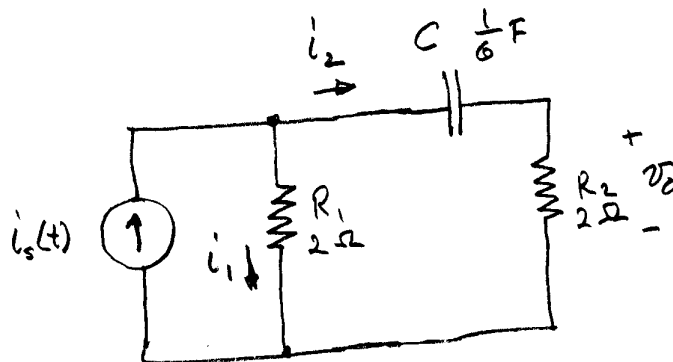1. (23 points)

In the circuit above,


- find V_{ab} ;
- find i_3 ;
- find Thévenin equivalent circuit for the network with output terminals a and b.



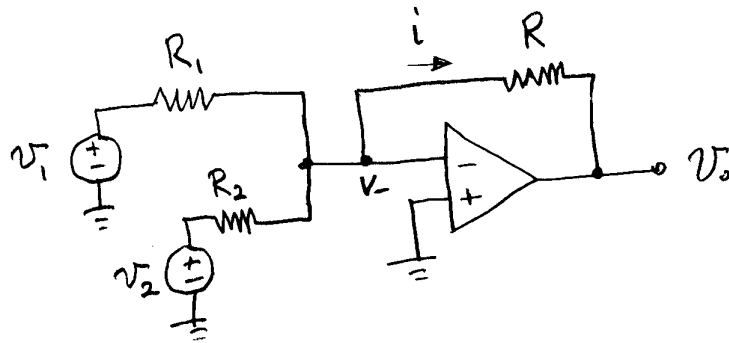2. (24 points)

For the circuit above, $i_s(t) = 5 \cos(3t)$.


- Find Z_2 , the impedance of C in series with R_2 .
- Find i_2 as a phasor. (*Suggestion: use current division*).
- Find $v_o(t)$.
- Find the average power dissipated in R_2 .



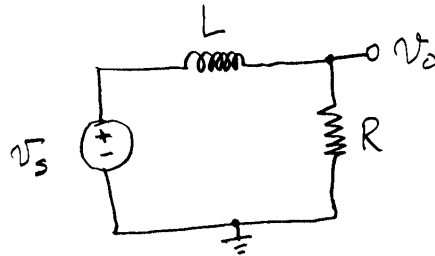3. (15 points)

In the circuit above, the Op-Amp is ideal.

- Does the circuit have a virtual ground? If so, where?
- Find an expression for i in terms of v_1 and v_2 .
- Find an expression for v_o in terms of v_1 and v_2 .



4. (38 points)

Consider the LR circuit above.

- Find an expression for $\mathbf{H}(j\omega) \equiv \mathbf{v}_o/\mathbf{v}_s$.
- Find $A_v \equiv |\mathbf{H}(j\omega)|$
- Show that $\lim_{\omega \rightarrow 0} A_v = 1$. (This is the maximum value of A_v .)
- Find an expression for the corner frequency, ω_c , where A_v has fallen to $1/\sqrt{2}$ of its maximum. (That is, find the value of ω such that $A_v = 1/\sqrt{2}$.)
- Find $\text{ang}(\mathbf{H}(j\omega_c))$. (This is the angle of \mathbf{H} when $\omega = \omega_c$.)
- Find an expression for $\mathbf{H}(s)$.
- Find any values of s for which $\mathbf{H}(s)$ has a pole.
- This circuit is a filter of the following type (*choose one*):
 - low pass
 - bandpass
 - high pass
 - none of the above.