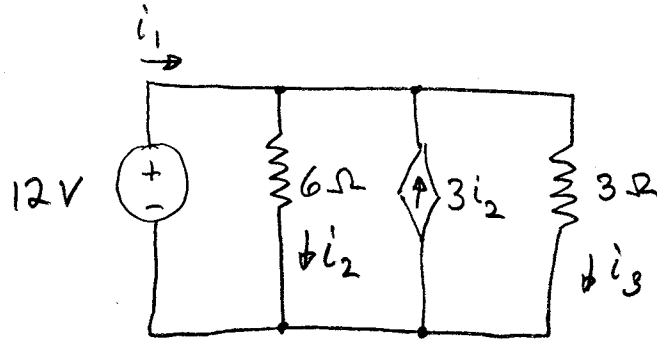


Physics 116A Fall 2003: Exam 1


10/28/2003


Closed book and notes except for one 8.5 in x 11 in sheet of paper. Show reasoning for full credit. Complex quantities are in **boldface**, e.g., $H(s)$. Many problems ask for numerical answers. There are 4 problems and 100 points. *Be sure to put your name on all pages submitted.*



(approx. points)

- 10 1. Find i_1 in the circuit above. (*Hint: you should be able to find i_2 and i_3 pretty quickly.*)
- 40 2. (a) Find the Thévenin equivalent of the circuit below.
- i. Find the open circuit voltage, $V_{ab}(\text{open circuit}) \equiv V_{oc}$.
 - ii. Find the resistance between a and b with the independent sources set to zero, $\equiv R_o$.
 - iii. Draw the Thévenin equivalent circuit.
- (b) For what value of resistance, R_L , connected between a and b will the power dissipated in R_L be maximum?
- (c) Find the maximum power delivered.

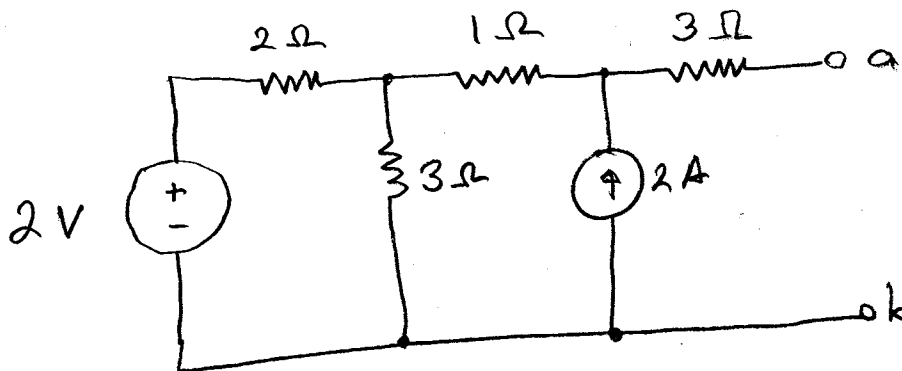

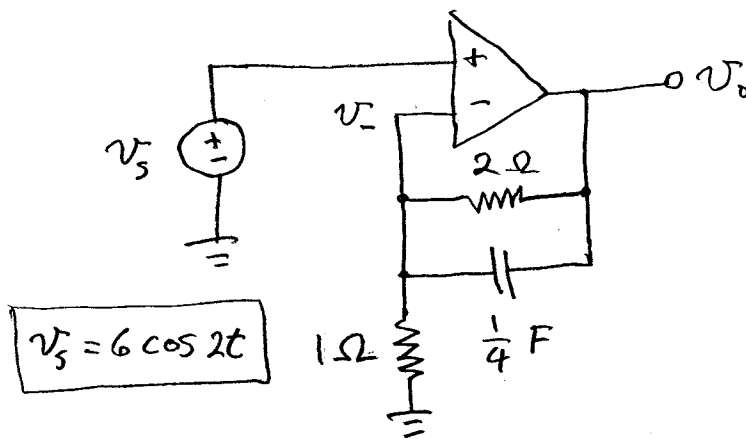

30

3. For the circuit above, $v_s = 6 \cos 2t$ V. Use the rules for ideal op-amps to find the following quantities (at the given frequency).

- Find the combined Z for the 2Ω resistor in parallel with the capacitor.
- Find a phasor expression for V_- in terms of V_o .
- Find $H = V_o/V_s$.
- Find V_o and $v_o(t)$.

20

4. Consider the LRC circuit below with output taken across the capacitor.

- Find an expression for $H(j\omega) \equiv V_o/V_s$.
- Eliminate L , R and C in your expression by expressing your result in terms of $\omega_r \equiv 1/\sqrt{LC}$ and $Q \equiv \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{\omega_r L}{R} = \frac{1}{\omega_r RC}$.
- For the remainder, let $Q = 1/\sqrt{2}$. This is some sort of filter.
 - Find an approximate expression for $|H|$ when $\omega \ll \omega_r$.
 - Find an approximate expression for $|H|$ when $\omega \gg \omega_r$.
 - Find $|H|$ when $\omega = \omega_r$.
 - What kind of filter is this (e.g., high pass, low pass, band pass...)?
- This is called a *two pole filter*. Explain briefly what this means. E.g., what function of which variable has these poles and why are there two of them, given your expression for H ?

