


Physics 116B Winter 2005: Exam 1


2/4/2005

Closed book and notes except for one 8.5 in \times 11 in sheet of paper. Show reasoning for full credit. There are 4 problems and 100 points (*approximate point values are given*). Note: complex quantities are shown in **boldface** type. All transistors and diodes (if any) are silicon at room temperature unless otherwise noted.

1. (44 points) The circuit below shows a TLC555 timer connected as a “one-shot” circuit. The block diagram of the TLC555 (inside the dashed lines) has been simplified slightly for clarity. R and C are connected externally as shown. Initially, $V_{out}(= Q)$ is low, V_{in} is low and the voltage across the capacitor, $V_C = 0$. Assume the logic levels are 0 and 5 V, the MOSFET has $V_T = 1$ V, $R = 10$ k Ω and $C = 0.01$ μ F. Assume that the MOSFET acts like a switch which is open if $V_{GS} < V_T$ and closed for V_{GS} significantly above V_T . See Table 1 for the latch truth table.

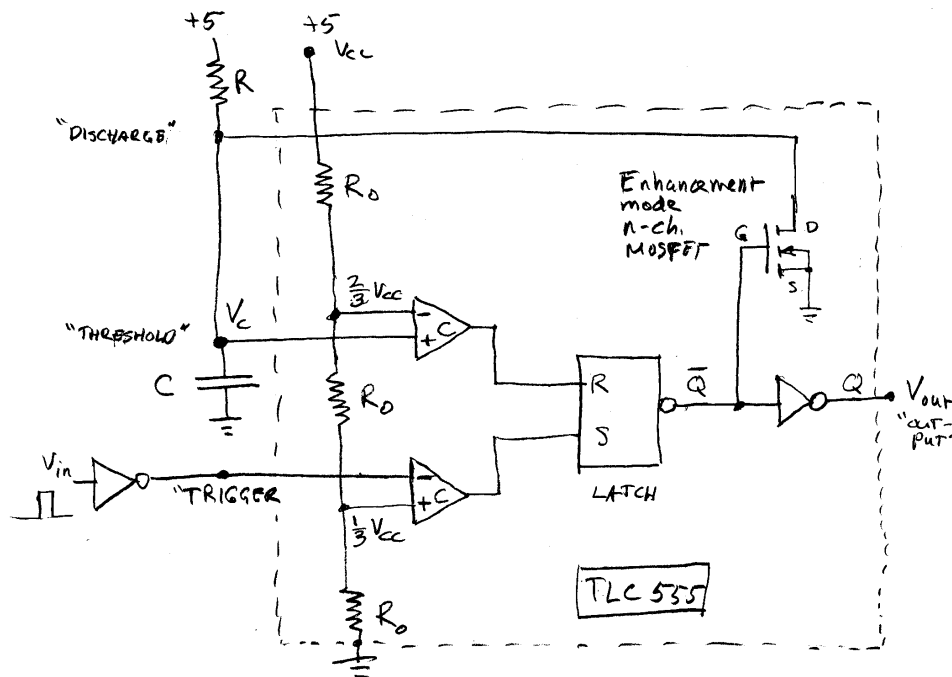- (a) Explain why $V_C = 0$ given the initial state described above.
- (b) What are the initial logic levels of “Trigger,” R and S? Explain briefly. (R and S are the latch inputs.)
- (c) A 10 μ s wide logic pulse is input at V_{in} . Make a timing diagram (3 plots, each stacked above the other, on the same t axis) showing V_{in} , Q and V_C during the production of the output pulse (*neglect the internal delays due to the inverter, comparator and latch circuits*). Explain what causes the latch to be set and what causes it to be reset.
- (d) Write an expression for $V_C(t)$ while Q is high. Use this to find an expression for the width of the output pulse in terms of R and C . Evaluate.
- (e) What happens to V_C when the latch is reset?



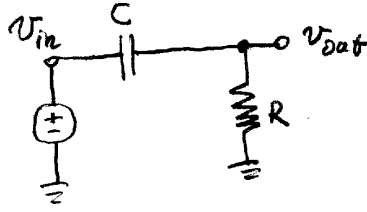

2. (28 points) In the network above, the voltages and currents are zero for $t < 0$. The input pulse is $v_{in}(t) = kt u(t)$, a ramp of slope k V/s starting at $t = 0$. Use the attached Laplace transform table as required for the following. *Note: some additional transform pairs have been added to reduce the need for use of partial fractions.*

- (a) Find $\mathbf{H}(s) \equiv \mathbf{V}_{out}(s)/\mathbf{V}_{in}(s)$ for the circuit.
- (b) Find the Laplace transform of the input waveform and use $\mathbf{H}(s)$ to find $\mathbf{V}_{out}(s)$.
- (c) Find $v_{out}(t)$.
- (d) Make a sketch of $v_{out}(t)$. Does the function have a simple asymptotic form for $t \gg RC$?

3. (10 points) Use theorems of Boolean algebra to simplify the following logical function:

$$\overline{(\overline{A\overline{B}} + \overline{A}B)(AB)}$$

4. (18 points)

- (a) Express the function $F(A, B, C, D)$ given in the Karnaugh map below as a simplified sum of products.
- (b) Implement the function F using two-stage logic with two- and three-input NAND gates and inverters (or even 4-input NANDs if really needed). Remember that De Morgan says that a NAND is equivalent to an OR with inverted inputs.

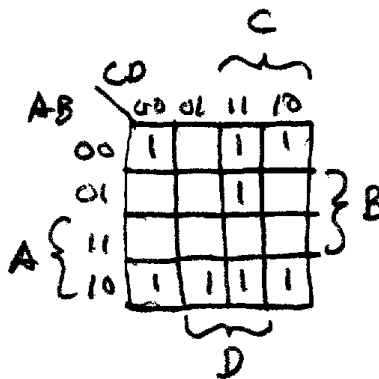


Table 5.1 Table of Laplace Transforms

$f(t)$	Property	$F(s)$
$f(t)$	Definition	$\int_0^{\infty} f(t)e^{-st} dt$
$f_1(t) + f_2(t)$	Linearity	$F_1(s) + F_2(s)$
$Kf(t)$	Linearity	$KF(s)$
$\frac{df(t)}{dt}$	Differentiation	$sF(s) - f(0)$
$\frac{d^2f(t)}{dt^2}$	Differentiation	$s^2F(s) - sf(0) - \frac{df(0)}{dt}$
$\int_0^t f(t) dt$	Integration	$\frac{1}{s} F(s)$
$tf(t)$	Complex differentiation	$-\frac{dF(s)}{ds}$
$e^{-at}f(t)$	Complex translation	$F(s + a)$
$f(t - a) u(t - a)$	Real translation	$e^{-as}F(s)$
$u(t)$		$\frac{1}{s}$
$e^{-at}u(t)$		$\frac{1}{s + a}$
$\cos \beta t u(t)$		$\frac{s}{s^2 + \beta^2}$
$\sin \beta t u(t)$		$\frac{\beta}{s^2 + \beta^2}$
$e^{-\alpha t} \cos \beta t u(t)$		$\frac{s + \alpha}{(s + \alpha)^2 + \beta^2}$
$e^{-\alpha t} \sin \beta t u(t)$		$\frac{\beta}{(s + \alpha)^2 + \beta^2}$
$t u(t)$		$\frac{1}{s^2}$
$te^{-at}u(t)$		$\frac{1}{(s + a)^2}$
$t^n u(t)$		$\frac{n!}{s^{n+1}}$
$(1 - e^{-at})u(t)$		$\frac{a}{s(s+a)}$
$\delta(t)$		1

Table 1: SR Latch Truth Table (S overrides R)

S	R	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Q_n is the present state, Q_{n+1} is the next state after receiving these inputs.


Physics 116 B Winter 2005 Exam 1 solutions

44

1. (a) $Q = 0 \Rightarrow \bar{Q} = 1$ and G of MOSFET is at $+5 \Rightarrow$ MOSFET "ON" ($V_{GS} = 5V > V_T$) ("closed switch") so "DISCHARGE" is connected to ground, $V_C = 0$.

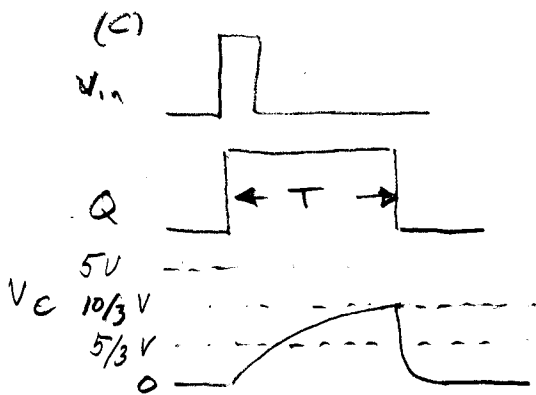(b) $V_{in} = \text{low (0V)}$ so Trigger = 1 so "-" input of S comparator is at $5V > 5/3$ of "+" input so S=0.

$V_C = 0$ so "+" input of R comparator is less than "-" input ($\frac{2}{3} \times 5V$) \Rightarrow R=0.



When $V_{in} \rightarrow 5V$, Trigger $\rightarrow 0V < V_T$ on S comparator, $S \rightarrow 1$ which causes $Q \rightarrow 1$, $\bar{Q} \rightarrow 0$. $\bar{Q} \rightarrow 0$ turns off MOSFET so capacitor charges toward 5V through R.

When V_C reaches $\frac{10}{3}V$, $R \rightarrow 1$, latch resets, $Q \rightarrow 0$, $\bar{Q} \rightarrow 1$ and V_C falls to 0. [We assume the input pulse is shorter than the time Q is high. Check this next.]

(d) While Q is high,

$$V_C = 5V(1 - e^{-t/\tau}) \quad \text{where } \tau = RC$$

$$\frac{2}{3} \times 5V = 5V(1 - e^{-T/\tau}) \Rightarrow e^{-T/\tau} = \frac{1}{3}$$

$$e^{T/\tau} = 3 \Rightarrow T = \tau \ln 3 = 10000 \times 0.01 \times 10^{-6} \times 1.1 \text{ s} \\ = 1.1 \times 10^{-4} \text{ s} = 110 \mu\text{s} \quad (>> 10 \mu\text{s})$$

(e) When the latch is reset, the MOSFET is turned on, causing $V_C \rightarrow 0$.

28

2.

(a)
$$\tilde{V}_{out}(s) = \frac{V_{out}}{V_{in}} = \frac{R}{R + \frac{1}{sC}} = \frac{s}{s + \frac{1}{RC}}$$


(b) $V_{in}(t) = kt u(t) \Rightarrow \tilde{V}_{in}(s) = \frac{k}{s^2}$

$$\tilde{V}_{out}(s) = H \tilde{V}_{in} = \frac{k}{s^2} \frac{s}{s + \frac{1}{RC}} = \frac{k}{s(s + \frac{1}{RC})}$$

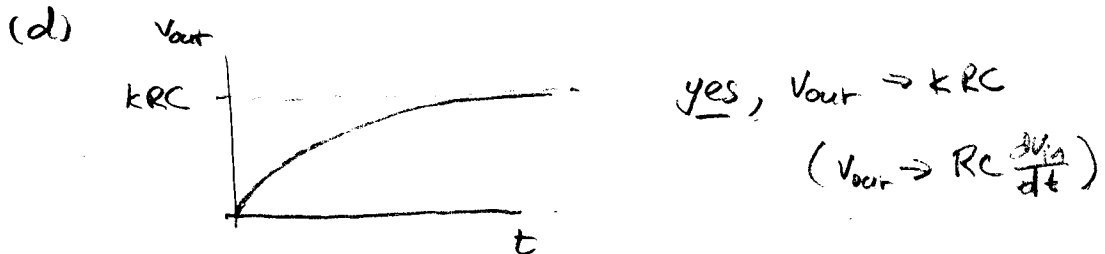(c)
$$\tilde{V}_{out}(s) = \frac{k}{a} \frac{a}{s(s+a)} \quad \text{where } a = \frac{1}{RC}$$

$$V_{out}(t) = \frac{k}{a} (1 - e^{-at}) u(t)$$


$$= \underline{\underline{kRC(1 - e^{-t/RC}) u(t)}}$$



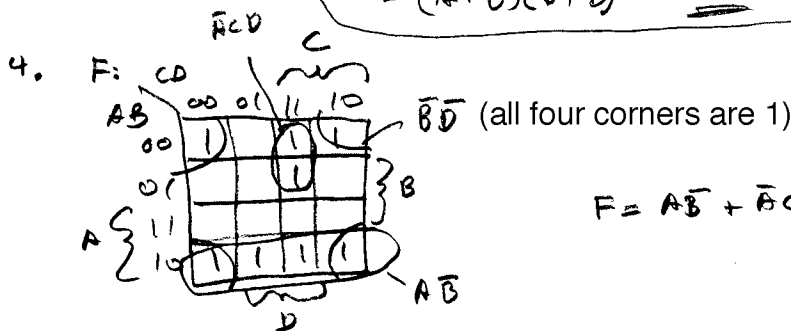
3.
$$\overline{(A\bar{B} + \bar{A}B)(AB)} = A\bar{B} + \bar{A}B + AB \quad (\text{De Morgan})$$

$$= A\bar{B} + (\bar{A} + A)B = A\bar{B} + B$$

$$= (A+B)(\bar{B}+B) = \underline{\underline{A+B}}$$


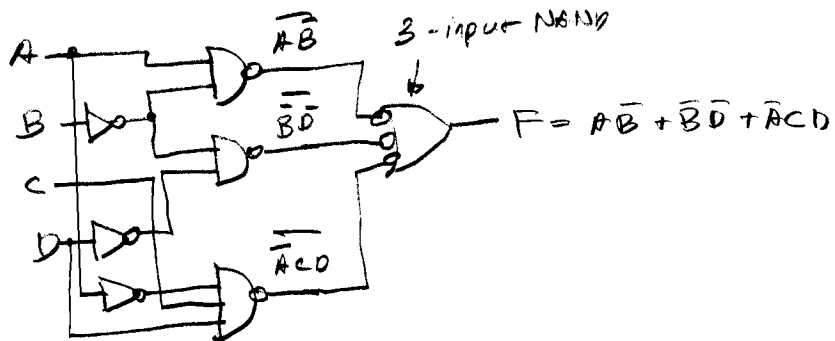
$$F = A\bar{B} + \bar{A}CD + \bar{B}\bar{D}$$



60

18