

Physics 116A Exam 1 1/29/2003 Solutions

10 1. $i_2 = 12V/6\Omega = 2A$, $i_3 = 12V/3\Omega = 4A$.

KCL: $i_1 + 3i_2 = i_2 + i_3 \Rightarrow i_1 = i_3 - 2i_2 = 4A - 4A = \underline{0}$.


40 2. (a)

(i) $V_{oc} \equiv V_2$ in the drawing here since $i = 0$ in the 3Ω resistor connected to a.

KCL: $i_1 + 2A = i_2$


KVL: $2V = 2i_1 + 3i_2$
(left loop)
 $= 2i_1 + 3i_1 + 6$

$i_1 = -4/5 A$


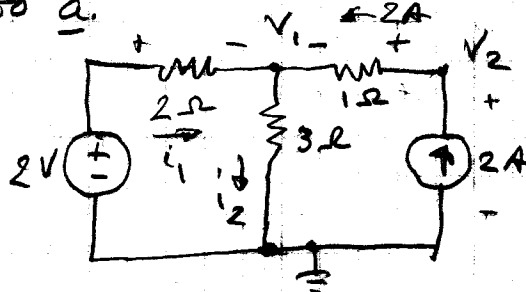


KVL: $2V + 2 \times 1\Omega = 2i_1 + V_2 = -8/5 + V_2 \Rightarrow V_2 = \underline{5.6V}$
(outer loop)
 $V_{oc} = V_2 = \underline{5.6V}$ [or can use nodal analysis to find V_1]

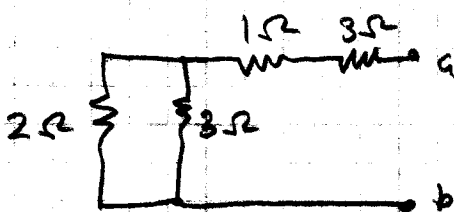(ii) Set independent sources to 0. $\left\{ \begin{array}{l} V(\oplus) \rightarrow \text{short circuit} \\ I(\uparrow) \rightarrow \text{open} \end{array} \right.$



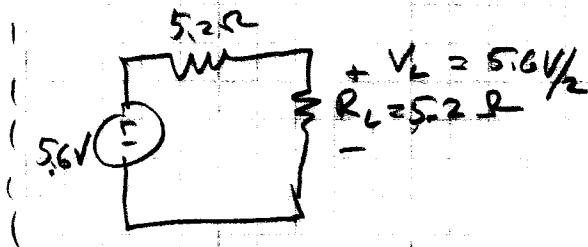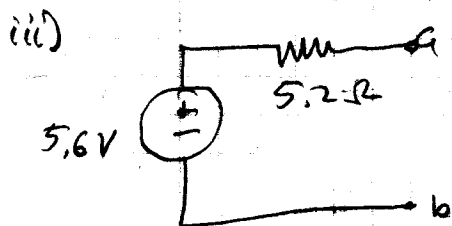$\Rightarrow R_0 = 4\Omega + 2\Omega \parallel 3\Omega$
 $= 4\Omega + \frac{6\Omega}{2+3} = \underline{5.2\Omega}$



(b) Maximum power when $R_L = R_0 = 5.2\Omega$

(c) The resulting circuit is a voltage divider with two equal resistors so $V_L = 5.6V/2$

$P = \frac{V_L^2}{R_L} = \frac{5.6^2 V^2}{4 \times 5.2\Omega} = \underline{1.51W}$

39

$$3. \quad \omega = 2 \text{ rad/s.}$$

$$\begin{aligned} \text{(a)} \quad \underline{Z} &= 2 \Omega \parallel \underline{Z}_C & \underline{Z}_C &= \frac{1}{j\omega C} = -\frac{j\Omega}{2 \times \frac{1}{4}} = -2j\Omega \\ &= \frac{2(-2j)\Omega}{2 - 2j} & &= \frac{-2j\Omega}{1-j} = \underline{(1-j)\Omega} \end{aligned}$$

(b) \underline{Z} and the 1Ω resistor form a voltage divider driven by \underline{V}_0 .

$$\begin{aligned} \underline{V}_- &= \frac{1\Omega}{1\Omega + \underline{Z}} \underline{V}_0 = \frac{\underline{V}_0}{1 + (1-j)} = \frac{1}{2-j} \underline{V}_0 \\ &= \frac{\underline{V}_0}{2.23 \angle -26.6^\circ} = 0.45 \angle 26.6^\circ \underline{V}_0 \end{aligned}$$

$$\text{(c)} \quad \underline{V}_- = \underline{V}_3 \quad (\text{since } V_+ = V_-)$$

$$\underline{H} = \frac{\underline{V}_0}{\underline{V}_3} = \frac{\underline{V}_0}{\underline{V}_-} = \frac{1}{0.45} \angle -26.6^\circ = \underline{2.23 \angle -26.6^\circ}$$

$$\begin{aligned} \text{(d)} \quad \underline{V}_0 &= \underline{H} \underline{V}_3 = 2.23 \angle -26.6^\circ \times 6 \angle 0^\circ = \underline{13.4 \angle -26.6^\circ \text{ V}} \\ \underline{V}_0 &= 13.4 \cos(2t - 26.6^\circ) \text{ V.} \end{aligned}$$

20 4. (a) Again, we have a voltage divider.

$$V_o = \frac{Z_c V_s}{R + Z_L + Z_c}$$

$$\tilde{H} = \frac{V_o}{V_s} = \frac{Z_c}{R + Z_L + Z_c} = \frac{1}{j\omega C} \frac{1}{R + j\omega L + \frac{1}{j\omega C}}$$

$$= \frac{1}{1 - \omega^2 LC + j\omega RC}$$

(b) $\tilde{H} = \frac{1}{1 - \omega^2/\omega_r^2 + \frac{j\omega}{\omega_r Q}}$ since $RC = \frac{1}{\omega_r Q}$

(c) $\tilde{H} = \frac{1}{1 - (\omega/\omega_r)^2 + j\sqrt{2} \omega/\omega_r}$

i) $\omega \ll \omega_r \Rightarrow \tilde{H} \approx 1 \Rightarrow |H| \approx 1$

ii) $\omega \gg \omega_r \Rightarrow \tilde{H} \approx \frac{-1}{(\omega/\omega_r)^2} \Rightarrow |H| \approx \left(\frac{\omega_r}{\omega}\right)^2$
(falls like $\frac{1}{\omega^2}$)

iii) $\omega = \omega_r \Rightarrow \tilde{H} = \frac{1}{j\sqrt{2}} \Rightarrow |H| = \frac{1}{\sqrt{2}}$

iv) Low pass filter. (half-power point)

(d) $\tilde{H}(s) = \frac{1}{1 + \frac{1}{\omega_r^2} s^2 + \frac{\sqrt{2}}{\omega_r} s}$ where $s = \sigma + j\omega$

$\tilde{H}(s)$ has two poles corresponding to the two roots of the quadratic in the denominator,

$$1 + \frac{1}{\omega_r^2} s^2 + \frac{\sqrt{2}}{\omega_r} s = 0.$$

[If we define $s' = s/\omega_r$, poles at $s' = -\frac{\sqrt{2}}{2}(1 \pm j)$]