

23 1. (a) $20 \Omega \parallel 30 \Omega = \frac{20 \times 30}{20 + 30} \Omega = \frac{600 \Omega}{50} = 12 \Omega$

$V_{ab} = 6V \left(\frac{12 \Omega}{12 \Omega + 30 \Omega} \right) = \underline{3V}$.



(b) $i_3 = V_{ab} / 30 \Omega = 3V / 30 \Omega = \underline{0.1 A}$

(c) set independent sources to 0 to find R_{th}

This gives $12 \Omega \parallel 12 \Omega = 6 \Omega$

$V_{o.c.} = V_{ab} = 3V$

Equivalent circuit:

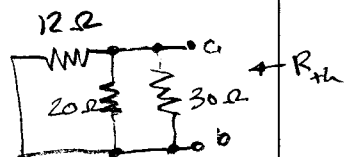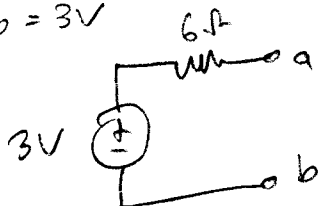

24 2. (a) $Z_2 = R_2 + \frac{1}{j\omega C} = 2 \Omega + \frac{1}{\frac{1}{6} \times 3j} = \underline{2(1-j) \Omega}$

(b) $i_2 = i_5 \frac{R_1}{R_1 + Z_2} = \frac{2 \Omega \times 5 A}{2 \Omega + 2(1-j) \Omega} = \frac{5}{2-j} A$
 $= \frac{5 A}{2.24 \angle -20.6^\circ} = \underline{2.24 \angle 20.6^\circ}$

(c) $\underline{V}_o = i_2 R_2 = 2.24 \angle 20.6^\circ \times 2 \Omega = 4.47 \angle 20.6^\circ V$
 $V_o = 4.47 \cos(3t + 20.6^\circ)$


See note } (d) $P_{av} = \frac{1}{2} \frac{|V_o|^2}{R_2} = \frac{1}{2} \times (4.47)^2 / 2 \Omega = \underline{5 W}$. { For R_1 , $\cos(\phi_1 - \phi_2) = 1$

15 3. (a) - input of op-amp is virtual ground ($V_- = 0V$).

(b) $\frac{V_1}{R_1} + \frac{V_2}{R_2} = i$

(c) $V_o = -iR = -\left[\frac{V_1}{R_1} + \frac{V_2}{R_2} \right] R$

Careful with sign of V_o :

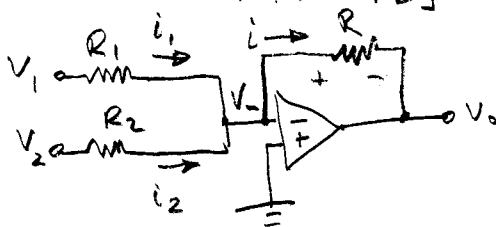

Note $V_- - V_o = iR$
 $V_- = 0$
 $V_o = -iR$

Note on 2(d): In general, $P_{av} = \frac{1}{2} V_m I_m \cos(\phi_1 - \phi_2)$
 where $V_m \equiv |V|$, $I_m \equiv |I|$, $\phi_1 = \text{ang}(V)$, $\phi_2 = \text{ang}(I)$.
 (assuming sinusoidal voltages and currents,
 V and I are phasors.)

$$38 \text{ 4. (a)} \quad \underline{v}_o = \frac{R}{R+j\omega L} \underline{v}_s \Rightarrow \underline{H}(j\omega) = \frac{R}{R+j\omega L} = \frac{1}{1+j\omega L/R}$$

see note
below

$$(b) \quad A_v = \sqrt{\underline{H}^* \underline{H}} = \sqrt{\frac{1}{(1-j\omega L/R)(1+j\omega L/R)}} = \sqrt{\frac{1}{1+\omega^2 L^2/R^2}}$$

$$(c) \quad \text{As } \omega \rightarrow 0 \quad A_v \rightarrow 1. \quad (\text{Just substitute } \omega=0)$$

$$(d) \quad \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1+\omega_c^2 L^2/R^2}} \Rightarrow 2 = 1 + \omega_c^2 L^2/R^2 \Rightarrow \omega_c = \underline{\underline{R/L}}$$

$$(e) \quad \text{ang}(\underline{H}(j\omega_c)) = \text{ang}\left(\frac{1}{1+j}\right) = \text{ang}\left(\frac{1}{\sqrt{2} \angle 45^\circ}\right) = \underline{\underline{-45^\circ}}$$

$$(f) \quad \underline{H}(s) = \frac{1}{1+sL/R} \quad (\text{Note: just substitute } s \text{ for } j\omega)$$

$$(g) \quad \text{Pole where } 1+sL/R = 0 \Rightarrow s = \underline{\underline{-R/L}} (= -\omega_c)$$

(h) low pass filter ($A_v = 1$ at $\omega = 0$ and falls like $1/\omega$ for $\omega \gg \omega_c$)

Note on Part (b): \underline{H}^* is the complex conjugate of \underline{H} (replace j with $-j$ wherever it appears)