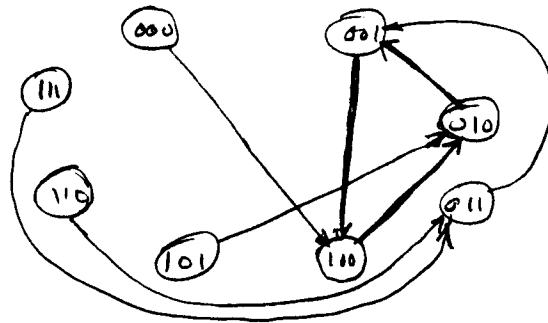


Manuscript problems

1. (a) $D_A = \overline{Q_A + Q_B}$




(c) The circuit is synchronous because all ^{Flip-Flop} transitions are synchronized with the clock pulse (i.e., clock inputs connect only to clock signal, not to other signals.)

(d) Minimum period = FF max delay + NR max delay + FF minimum setup time
 $= 30 \text{ ns} + 15 \text{ ns} + 25 \text{ ns} = 70 \text{ ns}$
 (note that constraint on min. clock pulse width of 20 ns can be easily satisfied with this period)

$f_{\text{max}} = 1/\text{min. period} = \underline{14.3 \text{ MHz}}$

2. (a) The counter is initially 0. It counts up until Q_1 and Q_2 are both 1, at which point the count enable (active low) input goes to 1 and further counting is disabled. Thus, the counter is in the state 0110 = "6" and the output is $\overline{1 \cdot 1} = 0$.

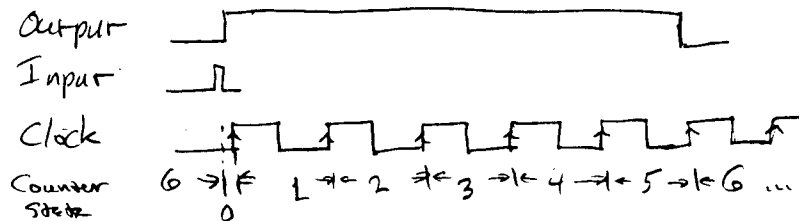(b) The counter is reset to zero, so $\overline{\text{count enable}} = 0$ and remains 0 at the clock transitions until the state "6" is reached. During this time the output is high. The minimum length of the output pulse is slightly more than 5 clock cycles (the clear input must arrive slightly before the clock transition for an immediate 0 \rightarrow 1 transition of the counter. Then there are 5 full states (1, 2, 3, 4, 5). On the sixth clock edge, the reaches 6, the output goes low, and counting stops.



$$\text{Min. output pulse width} \approx 5 \times 10 \mu\text{s} = \underline{50 \mu\text{s}}$$


(c) The output pulse is extended to $\geq 50 \mu\text{s}$ after the second pulse (second input resets the counter to 0).

(d) Yes - for example, in the transition

from 011 to 100, the 110 state can momentarily appear and result in a glitch (toward 0) of the output pulse.

(This will not affect the count sequence since the glitch is momentary (!) and does not come during the 'setup time' for the clock enable input. A glitch on the clear input is another story).

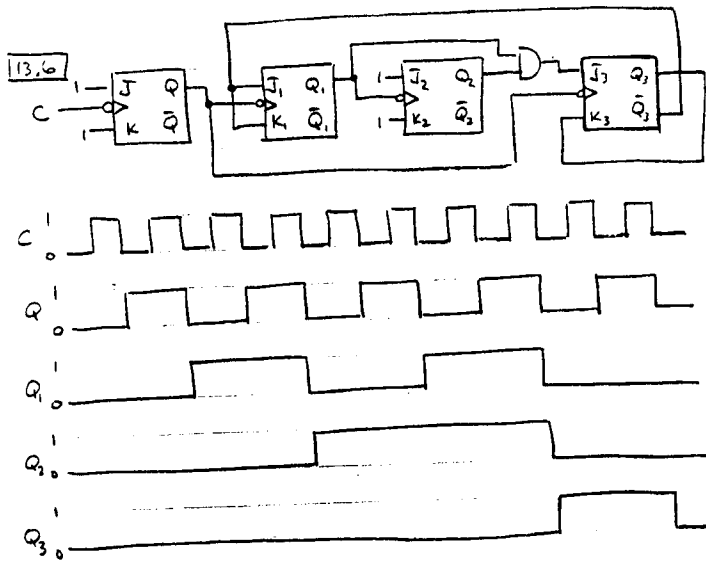From Bobrow, Instructor's Manual,
 Copyright Oxford 1996




13.35

(d.) $\frac{1}{2^n} = \frac{1}{2^6} = \frac{1}{64} = \underline{\underline{1.56\%}}$

(e.) $\frac{1}{2^n} = \frac{1}{2^8} = \frac{1}{256} = \underline{\underline{0.39\%}}$

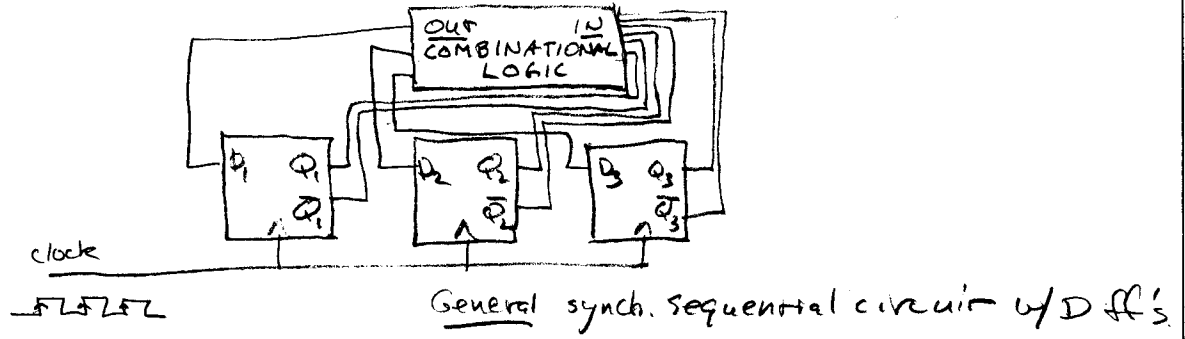Problem based on 13.15: Actually, this sequence can't be realized using the circuit of P13.13 (sorry 'bout that!). It can, of course, be realized with D ff's and more general feedback logic as follows:




State Table

Present State (n)			Next State (n+1)		
Q ₁	Q ₂	Q ₃	Q ₁	Q ₂	Q ₃
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	1	0	0
1	1	0	1	1	1
1	1	1	1	0	1


To achieve the next state,
 $D_i = Q_{i+1}$

We now make K. maps for each D input.

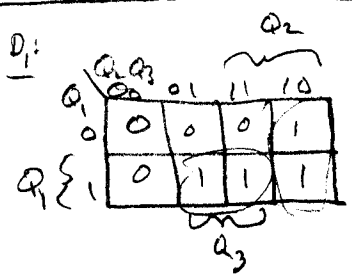
(You could also use the general transition map approach).



$$D_1 = Q_1 Q_3 + Q_2 \bar{Q}_3$$

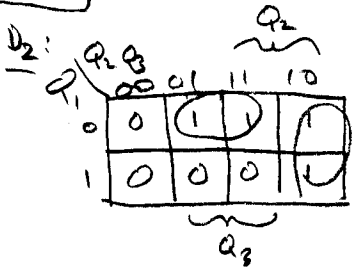

$$D_2 = \bar{Q}_1 Q_3 + Q_2 \bar{Q}_3$$

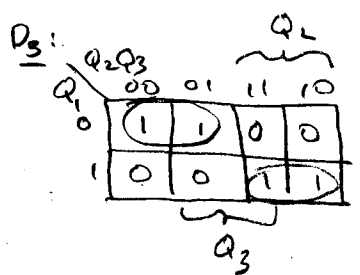

$$D_3 = \bar{Q}_1 \bar{Q}_2 + Q_1 Q_2$$

$$= (\bar{Q}_1) \bar{Q}_2 + (\bar{Q}_1) Q_2$$

$$= \bar{Q}_1 \oplus Q_2$$

Circuit:

