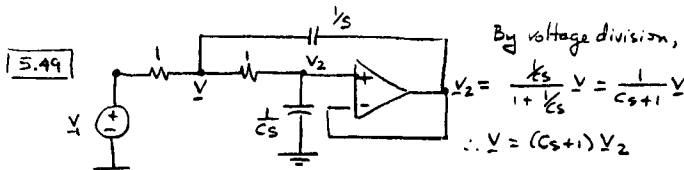


Physics 116A Fall 2004 Problem Set 5 Solutions

From Instructor's Manual for Fundamentals of Electrical Engineering, 2nd Ed.

© Oxford University Press, 1996



By voltage division,

$$V_2 = \frac{1/s}{1 + 1/s} V = \frac{1}{s+1} V$$

$$\therefore V = (s+1)V_2$$

By KCL at node  $V_1$ ,

$$\frac{V-V_1}{1} + \frac{V-V_2}{1} + \frac{V-1/s}{1/s} = 0$$

$$V-V_1 + V-V_2 + sV - sV_2 = 0$$

$$(s+2)V - V_1 - (s+1)V_2 = 0$$

$$(s+2)(s+1)V_2 - (s+1)V_2 = V_1$$

$$(Cs^2 + 2Cs + s + 2 - s - 1)V_2 = V_1$$


$$(Cs^2 + 2Cs + 1)V_2 = V_1$$

$$\therefore \frac{V_2}{V_1} = \frac{1}{Cs^2 + 2Cs + 1}$$

$$\frac{V_2}{V_1} = \frac{1/C}{s^2 + 2s + 1/C}$$


(a)  $C = \frac{1}{2} F \Rightarrow \frac{V_2}{V_1} = \frac{2}{s^2 + 2s + 2}$

$$= \frac{2}{(s+1+j)(s+1-j)}$$

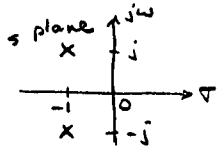


(b)  $C = 1 F \Rightarrow \frac{V_2}{V_1} = \frac{1}{s^2 + 2s + 1}$

$$= \frac{1}{(s+1)^2}$$

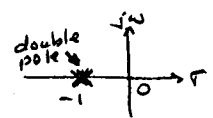

(c)  $C = 2 F \Rightarrow \frac{V_2}{V_1} = \frac{1/2}{s^2 + 2s + 1/2}$

$$= \frac{1/2}{(s + .29)(s + 1.71)}$$

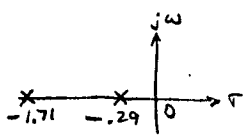

6.2  $L = 1 \text{ m}$   $d = 10^{-3} \text{ m} \Rightarrow r = 0.5 \times 10^{-3} \text{ m}$   $R = 2.2 \times 10^{-2} \Omega$   $i = 2 \text{ A}$

(a)  $J = \frac{i}{A} = \frac{i}{\pi r^2} = \frac{2}{\pi (0.5 \times 10^{-3})^2} = 2.55 \times 10^6 \text{ A/m}^2$

(b)  $J = nq u \Rightarrow u = \frac{J}{nq}$

$$u = \frac{2.55 \times 10^6}{(8.43 \times 10^{28})(1.6 \times 10^{-19})} = 1.89 \times 10^{-4} \text{ m/s}$$

(c)  $v = Ri = (2.2 \times 10^{-2})(2) = 4.4 \times 10^{-2} \text{ V}$

$E = 4.4 \times 10^{-2} \text{ V/m}$

$\mu = \frac{u}{E} = \frac{1.89 \times 10^{-4}}{4.4 \times 10^{-2}} = 4.3 \times 10^{-3} \text{ m}^2/\text{V}\cdot\text{s}$

(d)  $\sigma = nq \mu = (8.43 \times 10^{28})(1.6 \times 10^{-19})(4.3 \times 10^{-3}) = 5.8 \times 10^7 \text{ } \Omega/\text{m}$

6.5  $S_i$   $A = 1 \text{ mm}^2 = (10^{-3})^2 \text{ m}^2 = 10^{-6} \text{ m}^2$   $T = 300 \text{ K}$   $R = 50 \text{ k}\Omega$

$n_i = 1.5 \times 10^{16} \text{ m}^{-3}$   $\mu_n = 0.13 \text{ m}^2/\text{V}\cdot\text{s}$   $\mu_p = 0.05 \text{ m}^2/\text{V}\cdot\text{s}$

(a)  $\sigma = (n\mu_n + p\mu_p) q = (n_i\mu_n + n_i\mu_p) q$

$\sigma = n_i(\mu_n + \mu_p) q$

$$\sigma = (1.5 \times 10^{16})(0.13 + 0.05)(1.6 \times 10^{-19}) = 4.32 \times 10^{-4} \text{ } \Omega/\text{m}$$

(b)  $R = \frac{L}{\sigma A} \Rightarrow L = R\sigma A = 50 \text{ k}(4.32 \times 10^{-4})(10^{-6}) = 2.16 \times 10^{-5} \text{ m}$

$$= 21.6 \text{ } \mu\text{m}$$