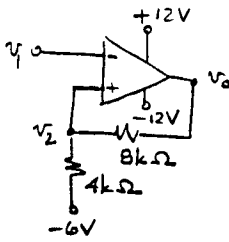


10.70



From Example 10.7,

$$v_1 = \frac{R_1}{R_1+R_2} V_{cc} + \frac{R_2}{R_1+R_2} v_r$$


$$v_1 = \frac{4k}{4k+8k} (12) + \frac{8k}{4k+8k} (-6)$$

$$v_1 = \frac{4k}{12k} (12) + \frac{8k}{12k} (-6) = 4 - 4 = \underline{0V}$$

$$v_2 = \frac{R_1}{R_1+R_2} (-V_{cc}) + \frac{R_2}{R_1+R_2} v_r$$

$$v_2 = \frac{4k}{4k+8k} (-12) + \frac{8k}{4k+8k} (-6) = -4 - 4 = \underline{-8V}$$

Hence, the transfer characteristic is

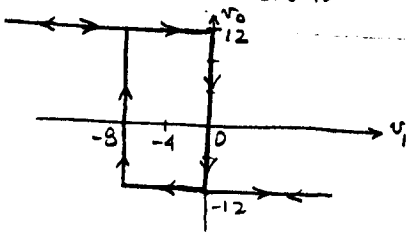

10.78


$$f_0 = \frac{R_2}{4R_1RC}$$

(a) $R_1 = R_2 = 10k\Omega$, $C = 0.05\mu F$

$$f_0 = \frac{10k}{4(10k)(10k)(0.05\mu)} = \underline{500 Hz}$$

3.29


For $t < 0$,

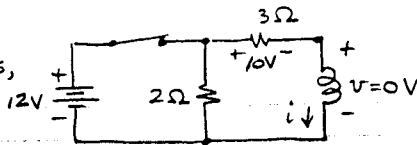

For dc, the inductor is a short circuit. Thus, $v(t) = \underline{0V}$.

By Ohm's law, $i(t) = \frac{12}{3} = 4A \Rightarrow i(0) = 4A$

For $t \geq 0$,

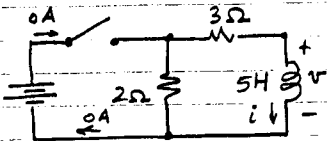

By KVL, $v + 2i + 3i = 0$
 $v + 5i = 0$

Since $v = 5 \frac{di}{dt}$, then



$$5 \frac{di}{dt} + 5i = 0$$

$$\frac{di}{dt} + i = 0 \Rightarrow i(t) = i(0)e^{-t} = \underline{4e^{-t} A}$$


Thus, $v(t) = 5 \frac{di(t)}{dt} = 5 \frac{d}{dt}(4e^{-t}) = \underline{-20e^{-t} V}$

Hence,
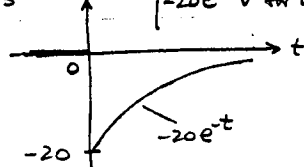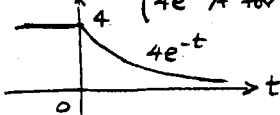
$$i(t) = \begin{cases} 4A & \text{for } t < 0 \\ 4e^{-t} A & \text{for } t \geq 0 \end{cases} \quad v(t) = \begin{cases} 0V & \text{for } t < 0 \\ -20e^{-t} V & \text{for } t \geq 0 \end{cases}$$



10.71

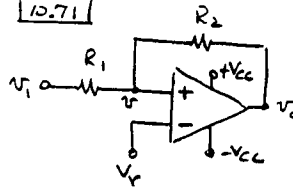

By KCL at node v,

$$\frac{v-v_1}{R_1} + \frac{v-v_0}{R_2} = 0$$

$$R_2 v - R_2 v_1 + R_1 v - R_1 v_0 = 0$$

$$(R_1+R_2)v = R_1 v_0 + R_2 v_1$$

$$v = \frac{R_1}{R_1+R_2} v_0 + \frac{R_2}{R_1+R_2} v_1$$

Suppose that $v_r = 0V$.

When $v_0 = +V_{cc}$, then v_0 remains $+V_{cc}$

for $v > v_r = 0V$, i.e., for

$$v = \frac{R_1}{R_1+R_2} (V_{cc}) + \frac{R_2}{R_1+R_2} v_1 > 0$$

$$R_1 V_{cc} + R_2 v_1 > 0$$

$$R_2 v_1 > -R_1 V_{cc}$$

$$v_1 > -\frac{R_1}{R_2} V_{cc}$$

Thus, when $v_1 < -\frac{R_1}{R_2} V_{cc}$, then v_0 changes to $-V_{cc}$.

When $v_0 = -V_{cc}$, then v_0 remains at $-V_{cc}$

for $v < v_r = 0V$, i.e., for

$$v = \frac{R_1}{R_1+R_2} (-V_{cc}) + \frac{R_2}{R_1+R_2} v_1 < 0$$


$$-R_1 V_{cc} + R_2 v_1 < 0$$

$$R_2 v_1 < R_1 V_{cc}$$


$$v_1 < \frac{R_1}{R_2} V_{cc}$$

Thus, when $v_1 > \frac{R_1}{R_2} V_{cc}$, then v_0 changes to $+V_{cc}$.

Combining the characteristics yields

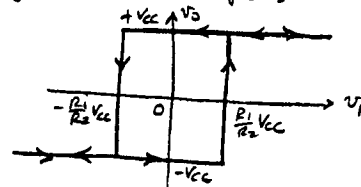

3.42

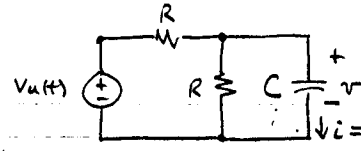

By KCL,

$$\frac{v-v_0(t)}{R} + \frac{v}{R} + C \frac{dv}{dt} = 0$$

$$v - v_0(t) + v + RC \frac{dv}{dt} = 0$$

$$\frac{dv}{dt} + \frac{2}{RC} v = \frac{v_0(t)}{RC}$$

For $t < 0$, $v(t) = 0V$ and $i(t) = 0A$

$$\therefore v(0) = 0V$$

For $t \geq 0$,

$$\frac{dv}{dt} + \frac{2}{RC} v = \frac{v_0}{RC} \Rightarrow v(t) = \frac{v_0}{2RC} + A e^{-2t/RC} = \frac{v_0}{2} + A e^{-2t/RC}$$

$$v(0) = \frac{v_0}{2} + A e^0 = 0 \Rightarrow A = -\frac{v_0}{2}$$

$$\therefore v(t) = \frac{v_0}{2} - \frac{v_0}{2} e^{-2t/RC} = \frac{v_0}{2} (1 - e^{-2t/RC})$$

Thus, $i(t) = C \frac{dv(t)}{dt} = C \frac{d}{dt} \left[\frac{v_0}{2} - \frac{v_0}{2} e^{-2t/RC} \right] = C \left(-\frac{v_0}{2} \right) \left(-\frac{2}{RC} e^{-2t/RC} \right)$

$$i(t) = \frac{v_0}{R} e^{-2t/RC}$$

Hence, $v(t) = \frac{v_0}{2} (1 - e^{-2t/RC}) u(t)$ $i(t) = \frac{v_0}{R} e^{-2t/RC} u(t)$

