

(a) $i_B = \frac{v_i - v_{BE}}{R_B} = \frac{5 - 0.8}{50k} = \frac{4.2}{50k} = 84 \mu A$

$i_C = \frac{v_{CC} - v_{CE}}{R_C} = \frac{5 - 0.2}{1k} = 4.8 mA$

$\therefore h_{FE} \geq \frac{i_C}{i_B} = \frac{4.8m}{84\mu} = 57.1$

(b) As in part (a), $i_B = 84 \mu A$

$i_C = \frac{v_{CC} - v_{CE}}{R_C} = \frac{5 - 0.2}{R_C} = \frac{4.8}{R_C}$

$h_{FE} i_B \geq i_C$

$100(84\mu) \geq \frac{4.8}{R_C} \Rightarrow R_C \geq \frac{4.8}{100(84\mu)} = 571 \Omega$

(c) $i_B = \frac{v_i - v_{BE}}{R_B} = \frac{5 - 0.8}{R_B} = \frac{4.2}{R_B}$

As in part (a), $i_C = 4.8 mA$

$h_{FE} i_B \geq i_C$



$100\left(\frac{4.2}{R_B}\right) \geq 4.8m \Rightarrow \frac{100(4.2)}{4.8m} \geq R_B \Rightarrow R_B \leq 87.5 k\Omega$

(d) $i_B = \frac{v_i - v_{BE}}{R_B} = \frac{v_i - 0.8}{50k}$ As in Part (a), $i_C = 4.8 mA$

$h_{FE} i_B \geq i_C$

$100\left(\frac{v_i - 0.8}{50k}\right) \geq 4.8m$

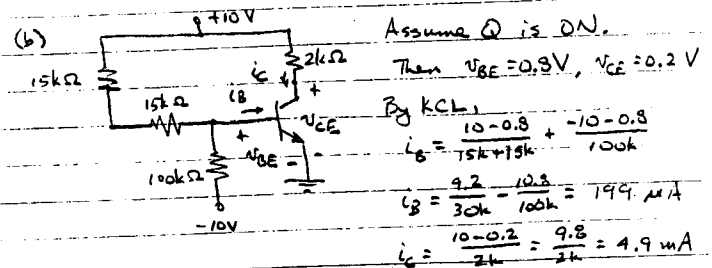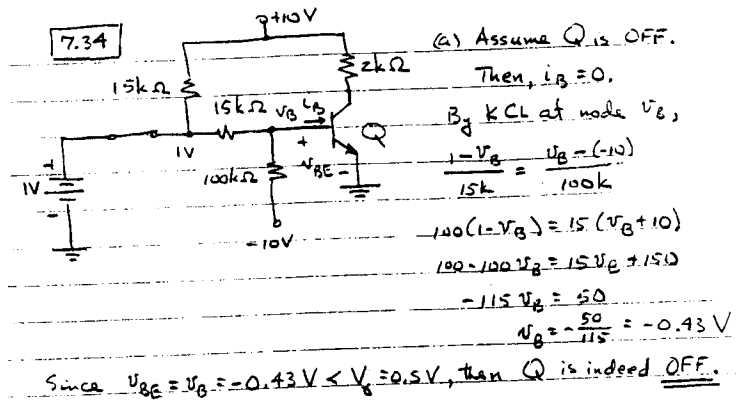$v_i \geq \frac{4.8m}{100} (50k) + 0.8 = 2.4 + 0.8 = 3.2V$



For Q to be ON,

$h_{FE} \geq \frac{i_C}{i_B} = \frac{4.9m}{199\mu} = 24.6$