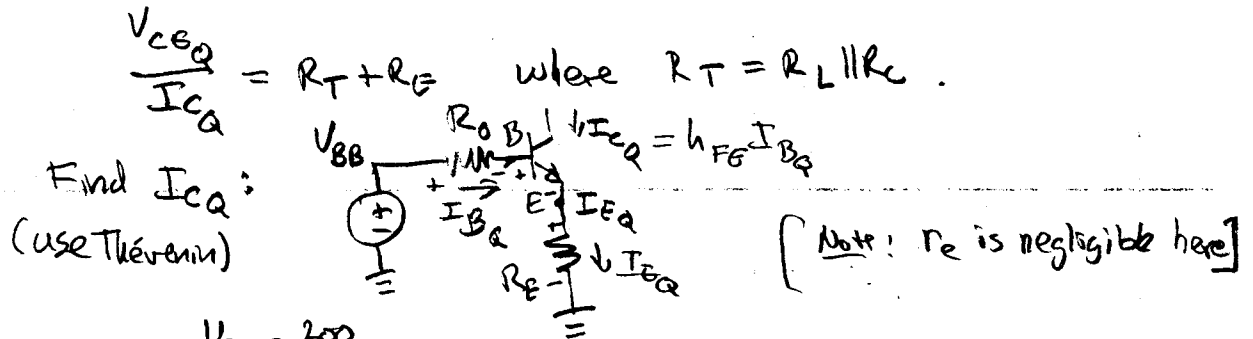


(a) Find R_L for centered Q point (on AC load line).
 See analysis on p. 625. For centered Q-point, " " " .



$$V_{BB} = \frac{200}{500} \times 20V = 8V$$

$$R_0 = R_1 \parallel R_2 = 120\Omega$$

$$V_{BB} - I_{BQ} R_0 - 0.7V - I_{EQ} R_E = 0$$

Express
 in terms
 of I_{CQ}
 and
 solve

$$V_{BB} - \frac{I_{CQ}}{h_{FE}} R_0 - 0.7V - \frac{h_{FE} + 1}{h_{FE}} I_{CQ} R_E = 0$$

$$I_{CQ} = \frac{(V_{BB} - 0.7) h_{FE}}{R_0 + (h_{FE} + 1) R_E}$$

$$I_{CQ} = \frac{7.3V \times 20}{120\Omega + 21 \times 75\Omega} = 86 \mu A$$

$$V_{CEQ} = (V_{CC} - I_{CQ} R_C) - I_{EQ} R_E$$

$$V_{CEQ} = 20V - 86 \mu A \times 50\Omega - \frac{21}{20} \times 86 \mu A \times 75\Omega = 8.9V$$

$$R_T = \frac{V_{CEQ}}{I_{CQ}} - R_C = \frac{8.9V}{86 \mu A} - 50\Omega = 28.5\Omega$$

$$\frac{1}{R_L} = \frac{1}{R_T} - \frac{1}{R_C} = 0.0151 \Omega^{-1} \Rightarrow R_L = \underline{\underline{66\Omega}}$$

(b) Max output signal power = $\frac{1}{2} I_{CQ} V_{CEQ}$
 $= \frac{1}{2} \times 86 \mu A \times 8.9V = \underline{\underline{0.38W}}$

(c) Minimum P_D (max) for transistor = $I_{CQ} V_{CEQ} = \underline{\underline{0.77W}}$
 (minimum transistor power dissipation rating)