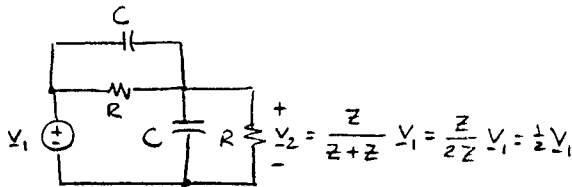



5.5




where $Z = \frac{R(\frac{1}{j\omega C})}{R + \frac{1}{j\omega C}} = \frac{R}{j\omega RC + 1} = \frac{R}{1 + j\omega RC}$

Thus, $\frac{V_2}{V_1} = \frac{1}{2} = 0.5 \Rightarrow |\frac{V_2}{V_1}| = 0.5 \quad \text{ang}(\frac{V_2}{V_1}) = 0^\circ$


Hence, the amplitude response is:

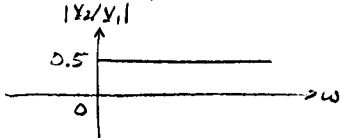

The phase response is:

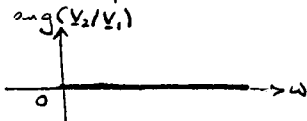

5.21

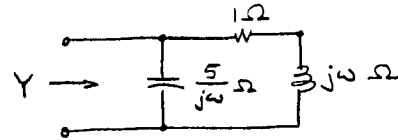

$$Y = \frac{j\omega}{5} + \frac{1}{1+j\omega} = \frac{j\omega(1+j\omega) + 5}{5(1+j\omega)} = \frac{j\omega + (j\omega)^2 + 5}{5(1+j\omega)}$$

$$= \frac{(5-\omega^2) + j\omega}{5(1+j\omega)} \cdot \frac{(1-j\omega)}{1-j\omega} = \frac{(5-\omega^2) + j\omega - (5-\omega^2)j\omega - (j\omega)^2}{5(1+\omega^2)}$$

$$= \frac{5-\omega^2 + j\omega - 5j\omega + \omega^2 j\omega + \omega^2}{5(1+\omega^2)}$$

$$= \frac{5 + j\omega(-4 + \omega^2)}{5(1+\omega^2)} = \frac{5 + j\omega(-4 + \omega^2)}{5(1+\omega^2)}$$

For resonance, $\omega(-4 + \omega^2) = 0$

(See note at bottom)

$\therefore \omega = 0 \text{ rad/s}$ - the trivial case.

$-4 + \omega^2 = 0$

$\omega^2 = 4 \Rightarrow \omega = 2 \text{ rad/s} = \omega_r$

5.39 $R = 1.24 \text{ M}\Omega$, $L = 0.62 \text{ mH}$, $C = 20 \text{ pF}$

(a) $\omega_r = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(0.62\text{m})(20\text{p})}} = 8.98 \text{ M rad/s}$

$f_r = \frac{\omega_r}{2\pi} = \frac{8.98 \text{ M}}{2\pi} = 1.43 \text{ MHz}$

(b) $Q = R\sqrt{\frac{C}{L}} = 1.24 \text{ M} \sqrt{\frac{20\text{p}}{0.62\text{m}}} = 223$

(c) $\text{BW} = \frac{1}{RC} = \frac{1}{(1.24\text{M})(20\text{p})} = 40.32 \text{ k rad/s}$

$\text{BW} = \frac{40.32 \text{ k}}{2\pi} = 6.42 \text{ kHz}$

(d) $Y = \frac{1}{R} + \frac{1}{j\omega L} + j\omega C = \frac{1}{R} + j(\omega C - \frac{1}{\omega L})$

$|Y| = \sqrt{(\frac{1}{R})^2 + (\omega C - \frac{1}{\omega L})^2} \quad \omega = 2\pi(1430 \text{ k}) = 8.985 \text{ M rad/s}$

$|Y| = \sqrt{(\frac{1}{1.24\text{M}})^2 + [(8.985\text{M})(20\text{p}) - \frac{1}{(8.985\text{M})(0.62\text{m})}]^2} = 0.828 \mu \text{ S}$


$|V| = \frac{|I|}{|Y|} = \frac{5 \text{ A}}{0.828 \mu} = 6.04 \text{ V rms}$

(e) $\omega = 2\pi(1450 \text{ k}) = 9.11 \text{ M rad/s}$

$|Y| = \sqrt{(\frac{1}{1.24\text{M}})^2 + [(9.11\text{M})(20\text{p}) - \frac{1}{(9.11\text{M})(0.62\text{m})}]^2} = 5.22 \mu \text{ S}$

$|V| = \frac{|I|}{|Y|} = \frac{5 \text{ A}}{5.22 \mu} = 0.958 \text{ V rms}$

5.41

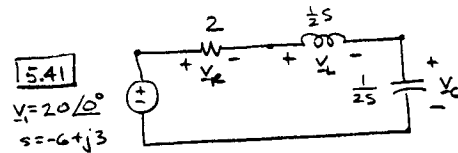

$V_1 = 20 \angle 0^\circ$
 $s = -6 + j3$

(a) $V_R = \frac{2}{2 + \frac{1}{25} + \frac{1}{25}} V_1 = \frac{4s}{4s + s^2 + 1} V_1 = \frac{4s}{s^2 + 4s + 1} V_1$

$= \frac{4(-6 + j3)}{(-6 + j3)^2 + 4(-6 + j3) + 1} V_1 = \frac{12(-2 + j)}{36 - j36 - 9 - 24 + j12 + 1} V_1$

$= \frac{12(-2 + j)}{-4 - j24} V_1 = \frac{3(-2 + j)}{1 - j6} V_1 = \frac{3(\sqrt{5} \angle 153.4^\circ)}{\sqrt{37} \angle -80.5^\circ} (20 \angle 0^\circ)$

$= 22.1 \angle -126^\circ \Rightarrow v_R(t) = 22.1 e^{-6t} \cos(3t - 126^\circ) \text{ V}$

(b) $V_L = \frac{\frac{1}{25}}{2 + \frac{1}{25} + \frac{1}{25}} V_1 = \frac{(\frac{1}{25})(2)}{2 + \frac{1}{25} + \frac{1}{25}} V_1 = \frac{1}{4} s V_R$

$= \frac{1}{4} (-6 + j3) V_R = \frac{3}{4} (-2 + j) V_R = \frac{3}{4} (\sqrt{5} \angle 153.4^\circ) (22.06 \angle -126^\circ)$

$= 37 \angle 27.4^\circ \Rightarrow v_L(t) = 37 e^{-6t} \cos(3t + 27.4^\circ) \text{ V}$

(c) $V_C = \frac{\frac{1}{25}}{2 + \frac{1}{25} + \frac{1}{25}} V_1 = \frac{(\frac{1}{25})(2)}{2 + \frac{1}{25} + \frac{1}{25}} V_1 = \frac{1}{45} V_R$

$= \frac{1}{4(-6 + j3)} V_R = \frac{1}{12(-2 + j)} V_R = \frac{22.06 \angle -126^\circ}{12(\sqrt{5} \angle 153.4^\circ)}$

$= 0.822 \angle 80.6^\circ \Rightarrow v_C(t) = 0.822 e^{-6t} \cos(3t + 80.6^\circ) \text{ V}$

Note on 5.21- High-Q coil criterion is not met in this case. Text defines resonance frequency as ω where the imaginary part of the admittance or impedance equals zero (for a circuit with at least one capacitor and one inductor). There may be more than one such frequency. See text, p. 276.