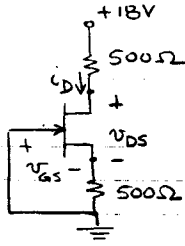


8.6



$I_{DSS} = 16 \text{ mA}$ $V_p = -4 \text{ V}$

Assume active region.

$\therefore i_D = I_{DSS} \left(1 - \frac{v_{GS}}{V_p}\right)^2$

8.8

For ohmic region:

$i_D = I_{DSS} \left[2 \left(1 - \frac{v_{GS}}{V_p}\right) \frac{v_{DS}}{-V_p} - \left(\frac{v_{DS}}{V_p}\right)^2 \right]$ (8.2)

On the border between the active and the ohmic regions,

$v_{DS} = v_{GS} - V_p$

$i_D = I_{DSS} \left[2 \left(1 - \frac{v_{GS}}{V_p}\right) \frac{v_{GS} - V_p}{-V_p} - \left(\frac{v_{GS} - V_p}{V_p}\right)^2 \right]$

$i_D = I_{DSS} \left[2 \left(\frac{V_p - v_{GS}}{V_p}\right) \frac{V_p - v_{GS}}{V_p} - \left(\frac{V_p - v_{GS}}{V_p}\right)^2 \right]$

$i_D = I_{DSS} \left[2 \left(\frac{V_p - v_{GS}}{V_p}\right)^2 - \left(\frac{V_p - v_{GS}}{V_p}\right)^2 \right]$

$i_D = I_{DSS} \left(\frac{V_p - v_{GS}}{V_p}\right)^2$

$i_D = I_{DSS} \left(1 - \frac{v_{GS}}{V_p}\right)^2$ (8.3)

(a)

$i_D = -\frac{v_{GS}}{500} = 16 \text{ m} \left(1 + \frac{v_{GS}}{4}\right)^2$

$-2 \text{ m} v_{GS} = 16 \text{ m} \left(1 + \frac{v_{GS}}{4}\right)^2$

$-2 v_{GS} = 16 + 8 v_{GS} + v_{GS}^2$

$v_{GS}^2 + 10 v_{GS} + 16 = 0$

$(v_{GS} + 2)(v_{GS} + 8) = 0 \Rightarrow v_{GS} = -2 \text{ V}, -8 \text{ V}$


Since $0 \geq v_{GS} \geq -4 \text{ V}$, then $v_{GS} = -2 \text{ V}$

(b) $i_D = -\frac{v_{GS}}{500} = \frac{2}{\frac{1}{2} \text{ k}} = 4 \text{ mA}$

(c) $v_{DS} = -500 i_D + 18 - 500 i_D = 18 - 1 \text{ k} i_D = 18 - 1 \text{ k}(4 \text{ m})$
 $= 18 - 4 = 14 \text{ V}$

(d) Since $v_{DS} = 14 \text{ V} > v_{GS} - V_p = -2 + 4 = 2 \text{ V}$
 then active-region operation is confirmed.

8.12

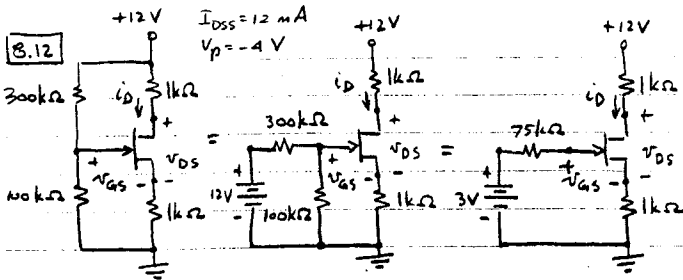

(a) Assume active-region operation: Then $i_G = 0 \text{ A}$ and

$i_D = I_{DSS} \left(1 - \frac{v_{GS}}{V_p}\right)^2 = 12 \text{ m} \left(1 + \frac{v_{GS}}{4}\right)^2 = 12 \text{ m} \left(1 + \frac{v_{GS}}{2} + \frac{v_{GS}^2}{16}\right)$

Also, $i_D = \frac{-v_{GS} + 3}{1 \text{ k}} = 12 \text{ m} \left(1 + \frac{v_{GS}}{2} + \frac{v_{GS}^2}{16}\right)$

$-v_{GS} + 3 = 12 + 6 v_{GS} + \frac{3}{4} v_{GS}^2$

$\frac{3}{4} v_{GS}^2 + 7 v_{GS} + 9 = 0$

$3 v_{GS}^2 + 28 v_{GS} + 36 = 0 \Rightarrow v_{GS} = \frac{-28 \pm \sqrt{28^2 - 4(3)(36)}}{2(3)} = -7.8, -1.54 \text{ V}$


Since $-4 \leq v_{GS} \leq 0 \text{ V}$, then $v_{GS} = -1.54 \text{ V}$

(b) $i_D = \frac{-v_{GS} + 3}{1 \text{ k}} = \frac{1.54 + 3}{1 \text{ k}} = 4.54 \text{ mA}$

(c) $v_{DS} = -1 \text{ k} i_D + 12 - 1 \text{ k} i_D = -2 \text{ k} i_D + 12 = -2 \text{ k}(4.54 \text{ m}) + 12 = 2.92 \text{ V}$

(d) Since $v_{DS} = 2.92 > v_{GS} - V_p = -1.54 + 4 = 2.46 \text{ V}$, then
 active-region operation is confirmed.

8.40

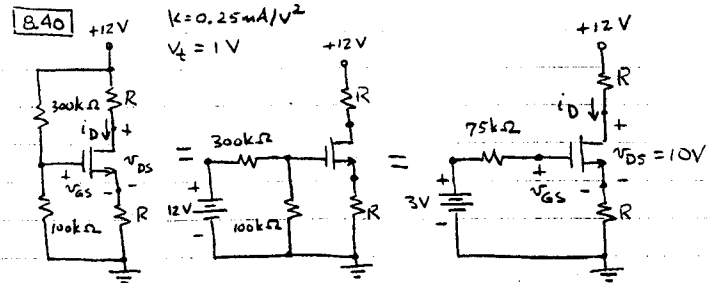

(a) By KVL, $12 = R_{iD} + v_{DS} + R_{iD}$ By KVL, $3 = 75 \text{ k} i_G + v_{GS} + R_{iD}$

$12 = 2 R_{iD} + 10$

$2 = 2 R_{iD}$

$R_{iD} = 1$

$3 = 0 + v_{GS} + 1$

$\therefore v_{GS} = 2 \text{ V}$


(b) Since $v_{DS} = 10 > v_{GS} - V_t = 2 - 1 = 1 \text{ V}$, then the MOSFET is in the
 active region.

Thus, $i_D = k(v_{GS} - V_t)^2 = 0.25 \text{ m}(2 - 1)^2 = 0.25 \text{ mA}$

(c) $R_{iD} = 1 \Rightarrow R = \frac{1}{i_D} = \frac{1}{0.25 \text{ m}} = 4 \text{ k}\Omega$

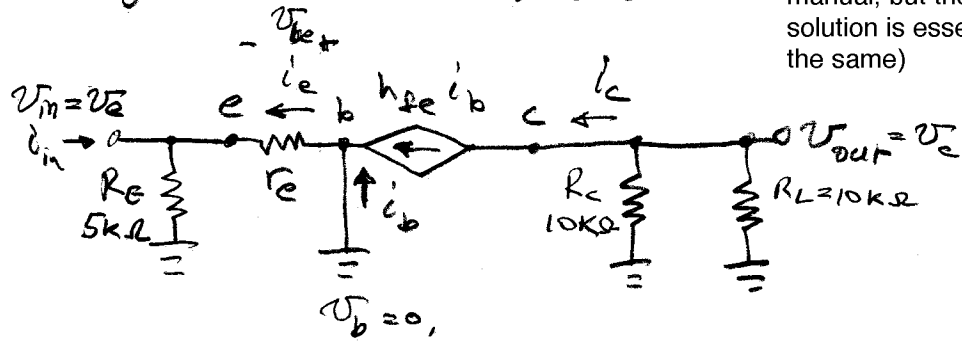9.21 Small signal AC model ($C_1, C_2, C_B \rightarrow \infty$)

(Not from instructor's manual, but their solution is essentially the same)



(a)

$$A_v = \frac{v_c}{v_e}, \quad v_c = -i_c R_c \parallel R_L$$

$$v_e = -v_{be} = -i_e r_e$$

$$A_v = + \frac{i_c}{i_e} \frac{R_c \parallel R_L}{r_e} = \frac{h_{fe} i_b}{h_{fe} i_b + i_b} \frac{R_c \parallel R_L}{r_e}$$

$$= \frac{h_{fe}}{h_{fe} + 1} \frac{R_c R_L}{(R_c + R_L) r_e}$$

$$r_e = \frac{kT/q}{I_{E_Q}} = \frac{26mV}{I_{E_Q}} = \frac{26mV}{\frac{h_{FE} + 1}{h_{FE}} I_{C_Q}} = \frac{26mV}{\frac{101}{100} \times 9.3mA} \quad @ 300k$$

$$= \underline{28\Omega}$$

$$A_v = \frac{100}{101} \times \frac{5k\Omega}{28\Omega} = \underline{177}$$

(b) $R_{in} = R_e \parallel r_e$ [Note that the resistance looking into the emitter is $\frac{v_e}{-i_e} = r_e$]

$$= 5k\Omega \parallel 28\Omega \approx \underline{28\Omega}$$

(c) R_o is the resistance looking into the amplifier output (neglecting the load resistance, R_L).


Set $v_m = 0$ and find Thevenin equiv. resistance of circuit. If $v_m = 0, i_e = 0 \Rightarrow i_b = 0$ and $h_{fe} i_b = i_c = 0$. Thus the output node sees R_c connected to ground.

$$R_o = R_c = \underline{10k\Omega}$$

Note

This is a voltage amplifier suitable for a signal with a low source impedance. With the $1k\Omega$ source imped. shown in Fig. P9.21, $v_{out}/v_s = 4.8$, much less than A_v .

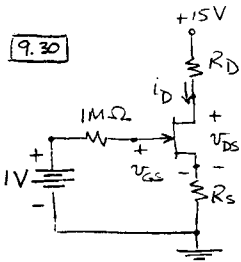
Assignment 8 Solutions from Instructor's Manual for Fundamentals of Elec. Engr., 2nd ed.
 © 1996 Oxford Univ. press



$I_{DSS} = 16 \text{ mA}$ $V_p = -4 \text{ V}$
 $I_{DQ} = 1 \text{ mA}$ $V_{DSQ} = 7 \text{ V}$
 For active region: $i_D = I_{DSS} \left(1 - \frac{v_{GS}}{V_p}\right)^2$
 Thus,
 $\sqrt{\frac{i_D}{I_{DSS}}} = 1 - \frac{v_{GS}}{V_p} \Rightarrow \frac{v_{GS}}{V_p} = 1 - \sqrt{\frac{i_D}{I_{DSS}}}$
 $\therefore v_{GS} = V_p \left(1 - \sqrt{\frac{i_D}{I_{DSS}}}\right) = -4 \left(1 - \sqrt{\frac{1 \text{ mA}}{16 \text{ mA}}}\right) = -4 \left(\frac{3}{4}\right)$

Since $i_G = 0 \text{ A}$,
 $R_S = \frac{-v_{GS} + 1}{i_D} = \frac{-(-3) + 1}{1 \text{ mA}} = 4 \text{ k}\Omega$
 Also, $R_D = \frac{15 - v_D}{i_D} = \frac{15 - (v_{DS} - v_{GS} + 1)}{1 \text{ mA}} = \frac{15 - (7 + 3 + 1)}{1 \text{ mA}} = 4 \text{ k}\Omega$

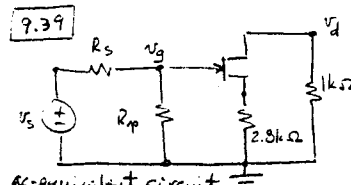Since $v_{DS} = 7 > v_{GS} - V_p = -3 + 4 = 1 \text{ V}$, then active-region operation is confirmed.





ac-equivalent circuit ac-equivalent circuit with small-signal model

$R_p = 50 \text{ k}\Omega // 250 \text{ k}\Omega = 167 \text{ k}\Omega$
 $I_{DSS} = 10 \text{ mA}$ $V_p = -4 \text{ V}$ $V_{GSQ} = -2 \text{ V}$ $I_{DQ} = 2.5 \text{ mA}$
 $g_m = -\frac{2}{V_p} \sqrt{i_{DQ} I_{DSS}} = -\frac{2}{-4} \sqrt{(2.5 \text{ mA})(10 \text{ mA})} = \frac{1}{2} (5 \text{ mA}) = 2.5 \text{ mS}$

(a) By KCL at node v_d ,

$g_m v_{gs} = \frac{v_d}{2.8 \text{ k}\Omega}$
 $2.5 \text{ mS} (v_g - v_d) = \frac{v_d}{2.8 \text{ k}\Omega}$
 $7 v_g - 7 v_d = v_d$
 $7 v_g = 8 v_d$
 $v_d = \frac{7}{8} v_g$
 $\therefore \frac{v_d}{v_g} = \frac{7}{8} = 0.875$

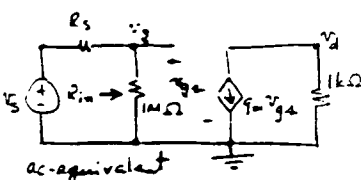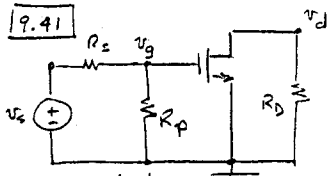(b) $v_d = -1 \text{ k}\Omega g_m v_{gs}$
 $v_d = -1 \text{ k}\Omega (2.5 \text{ mS})(v_g - v_d)$
 $v_d = -2.5 (v_g - \frac{7}{8} v_g)$
 $v_d = -\frac{2.5}{8} v_g$
 $\therefore \frac{v_d}{v_g} = -\frac{2.5}{8} = -0.313$




ac-equivalent circuit $R_p = 2 \text{ M}\Omega // 2 \text{ M}\Omega = 1 \text{ M}\Omega$ ac-equivalent circuit with small-signal model

$V_{GSQ} = 6 \text{ V}$, $I_{DQ} = 4 \text{ mA}$, $V_{DSQ} = 12 \text{ V}$, $K = 0.25 \text{ mA/V}^2$, $V_t = 2 \text{ V}$

$g_m = 2 \sqrt{K i_D} = 2 \sqrt{(0.25 \text{ mA})(4 \text{ mA})} = 2 \text{ mS}$

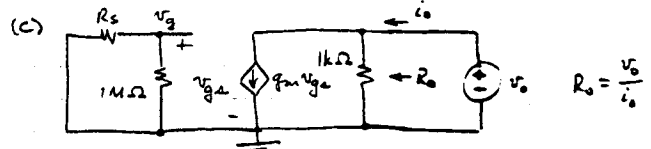(a) $v_d = -1 \text{ k}\Omega g_m v_{gs} = -1 \text{ k}\Omega (2 \text{ mS}) v_g = -2 v_g$
 $\therefore \frac{v_d}{v_g} = -2$ (b) $R_{in} = 1 \text{ M}\Omega$



By KCL at node v_g , $\frac{v_g}{R_S} + \frac{v_g}{1 \text{ M}\Omega} = 0 \Rightarrow v_g = 0 \text{ V} \Rightarrow v_{gs} = v_g = 0 \text{ V}$

By KCL,
 $i_o = g_m v_{gs} + \frac{v_o}{1 \text{ k}\Omega} = 2 \text{ mS} v_g + \frac{v_o}{1 \text{ k}\Omega} = \frac{v_o}{1 \text{ k}\Omega}$

$\therefore R_o = \frac{v_o}{i_o} = 1 \text{ k}\Omega$