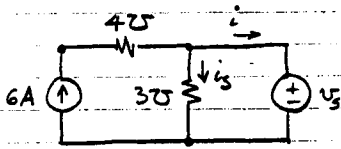


1.16 (a) $v_1 = 30V \Rightarrow i_1 = \frac{v_1}{5} = \frac{30}{5} = \underline{6A}$

(c) $v_3 = -9V \Rightarrow i_3 = -\frac{v_3}{3} = -\frac{-9}{3} = \underline{3A}$

1.17




By Ohm's law, $i_3 = 3V$

By KCL, $i = 6 - i_3 = 6 - 3V$

(a) $v_3 = 1V: i = 6 - 3(1) = \underline{3A}$

1.18

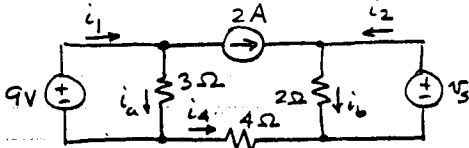

By Ohm's law,


$i_a = \frac{9}{3} = 3A \quad i_b = \frac{v_5}{2}$

By KCL, $i_1 = i_a + 2 = 3 + 2 = \underline{5A} \quad i_4 = i_a - i_1$
 $i_2 = i_b - 2 = \frac{v_5}{2} - 2 \quad i_4 = 3 - 5 = \underline{-2A}$

By Ohm's law, $v_4 = 4i_4 = 4(-2) = \underline{-8V}$

(a) $v_5 = 2V: i_1 = \underline{5A}, i_2 = \frac{v_5}{2} - 2 = \frac{2}{2} - 2 = \underline{-1A}$

$v_4 = \underline{-8V}$

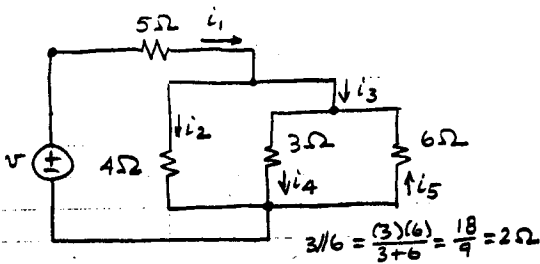

$\frac{3 \parallel 6}{3+6} = \frac{(3)(6)}{3+6} = \frac{18}{9} = 2\Omega$


1.21 $i_2 = -2A$. Using the current-divider formula,

$i_2 = \frac{3 \parallel 6}{4+3 \parallel 6} i_1 = \frac{2}{4+2} i_1 = \frac{1}{3} i_1 \Rightarrow i_1 = 3i_2 = 3(-2) = \underline{-6A} = i_1$

$i_3 = \frac{4}{4+3 \parallel 6} i_1 = \frac{4}{4+2} i_1 = \frac{2}{3} (-6) = \underline{-4A} = i_3$

$i_4 = \frac{6}{3+6} i_3 = \frac{6}{3+6} (-4) = \frac{-24}{9} = \underline{-\frac{8}{3}A} = i_4$

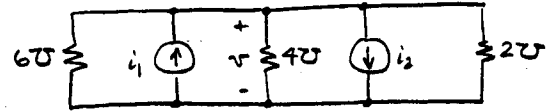$-i_5 = \frac{3}{3+6} i_3 = \frac{3}{3+6} (-4) = \frac{-12}{9} = \frac{-4}{3} \Rightarrow i_5 = \underline{\frac{4}{3}A} = i_5$



Careful: this means 6VxV, a current.


1.23 By KCL, $6V + 4V + 2V + i_2 = i_1$

$12V = i_1 - i_2$

$v = \frac{i_1 - i_2}{12}$

(c) $i_1 = 2A, i_2 = 3A \Rightarrow v = \frac{2-3}{12} = \underline{-\frac{1}{12}V}$

1.34

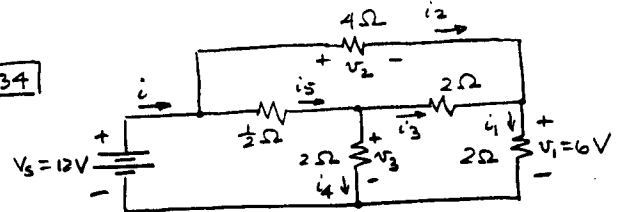

By Ohm's law, $i_1 = \frac{v_1}{2} = \frac{6}{2} = 3A$

By KVL, $v_2 = v_5 - v_1 = 12 - 6 = 6V$

By Ohm's law, $i_2 = \frac{v_2}{4} = \frac{6}{4} = \frac{3}{2}A$

By KCL, $i_3 = i_1 - i_2 = 3 - \frac{3}{2} = \frac{3}{2}A$

By KVL, $v_3 = 2i_3 + v_1 = 2(\frac{3}{2}) + 6 = 9V$


By Ohm's law, $i_4 = \frac{v_3}{2} = \frac{9}{2}A$

By KCL, $i_5 = i_3 + i_4 = \frac{3}{2} + \frac{9}{2} = 6A$

By KCL, $i = i_2 + i_5 = \frac{3}{2} + 6 = \frac{15}{2}A$

$\therefore R_{eq} = \frac{v_5}{i} = \frac{12}{15/2} = \frac{24}{15} = \frac{8}{5} = \underline{1.6\Omega}$

1.42

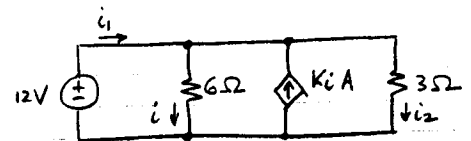


By Ohm's law, $i = \frac{12}{6} = 2A \quad i_2 = \frac{12}{3} = 4A$

By KCL, $i_1 = i - Ki + i_2 = (1-K)i + i_2$

$i_1 = (1-K)2 + 4$

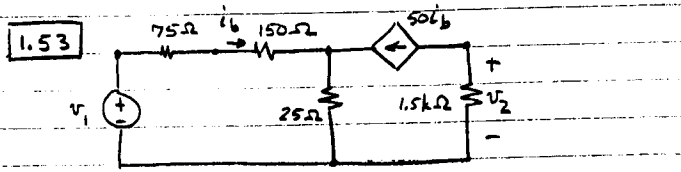(b) $K = 3 \Rightarrow i_1 = (1-3)2 + 4 = -4 + 4 = \underline{0A}$




(a) $v_1 = 75i_b + 150i_b + 25(50i_b) = (75 + 150 + 1275)i_b = 1500i_b$

$i_b = \frac{v_1}{1500}$

(b) $v_2 = -1.5 \times 10^3 (50i_b) = -75 \times 10^3 \left(\frac{v_1}{15 \times 10^3} \right) = -50v_1$

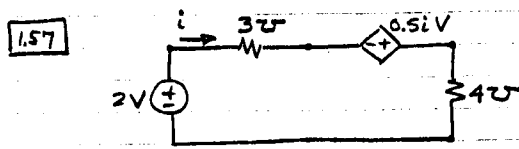(c) $v_2 = -50(0.1 \cos 120\pi t) = -5 \cos 120\pi t \text{ V}$



$i = 24 \text{ A}$

The power absorbed by the 2-V voltage source is

$p_s = 2(-i) = 2(-24) = -48 \text{ W}$

The power absorbed by the 3-ohm conductance is


$p_3 = (1/3)i^2 = (1/3)(24^2) = 192 \text{ W}$

The power absorbed by the dependent voltage source is

$p_D = (0.5i)(-i) = (0.5)(24)(-24) = -288 \text{ W}$

The power absorbed by the 4-ohm conductance is

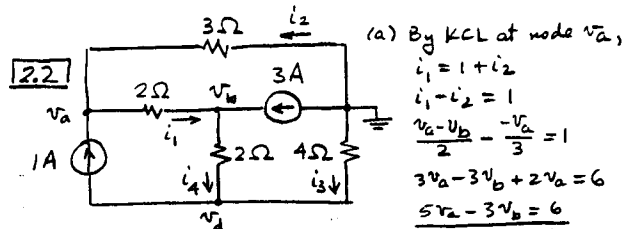$p_4 = (1/4)i^2 = (1/4)(24^2) = 144 \text{ W}$



(a) By KCL at node v_a ,
 $i_1 = i + i_2$
 $i_1 - i_2 = 1$
 $\frac{v_a - v_b}{2} - \frac{-v_a}{3} = 1$
 $3v_a - 3v_b + 2v_a = 6$
 $5v_a - 3v_b = 6$

By KCL at node v_b ,

$i_1 + 3 = i_4$

$i_1 - i_4 = -3$

$\frac{v_a - v_b}{2} - \frac{v_b - v_d}{2} = -3$

$v_a - v_b - v_b + v_d = -6$

$v_a - 2v_b + v_d = -6$

By KCL at node v_d ,

$i_3 + i_4 = 1$

$-\frac{v_d}{4} + \frac{v_b - v_d}{2} = 1$

$-v_d + 2v_b - 2v_d = 4$

$2v_b - 3v_d = 4$

$D = \begin{vmatrix} 5 & -3 & 0 \\ 1 & -2 & 1 \\ 0 & 2 & -3 \end{vmatrix} = 30 - 10 - 9 = 11$

$D_a = \begin{vmatrix} 6 & -3 & 0 \\ -6 & -2 & 1 \\ 4 & 2 & -3 \end{vmatrix} = 36 - 12 - 12 + 54 = 66 \Rightarrow v_a = \frac{D_a}{D} = \frac{66}{11} = 6 \text{ V}$

$D_b = \begin{vmatrix} 5 & 6 & 0 \\ 1 & -6 & 1 \\ 0 & 4 & -3 \end{vmatrix} = 90 - 20 + 18 = 88 \Rightarrow v_b = \frac{D_b}{D} = \frac{88}{11} = 8 \text{ V}$

$D_d = \begin{vmatrix} 5 & -3 & 6 \\ 1 & -2 & -6 \\ 0 & 2 & 4 \end{vmatrix} = -40 + 12 + 60 + 12 = 44 \Rightarrow v_d = \frac{D_d}{D} = \frac{44}{11} = 4 \text{ V}$

(b) $i_1 = \frac{v_a - v_b}{2} = \frac{6 - 8}{2} = -1 \text{ A}$ $i_2 = \frac{-v_a}{3} = \frac{-6}{3} = -2 \text{ A}$

$i_3 = \frac{-v_d}{4} = \frac{-4}{4} = -1 \text{ A}$ $i_4 = \frac{v_b - v_d}{2} = \frac{8 - 4}{2} = 2 \text{ A}$