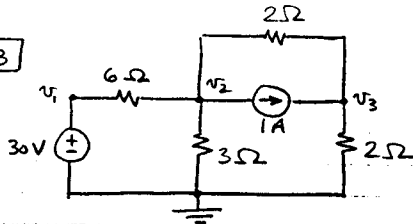


2.8



For node  $v_1$ , by KVL,  $v_1 = 30V$

By KCL at node  $v_2$ ,

$$\frac{v_2 - 30}{6} + \frac{v_2}{3} + \frac{v_2 - v_3}{2} + 1 = 0$$

$$v_2 - 30 + 2v_2 + 3v_2 - 3v_3 + 6 = 0$$

$$6v_2 - 3v_3 = 24$$

$$2v_2 - v_3 = 8$$

By KCL at node  $v_3$ ,

$$\frac{v_3 - v_2}{2} + \frac{v_3}{2} = 1$$

$$v_3 - v_2 + v_3 = 2$$

$$-v_2 + 2v_3 = 2$$


$$4v_2 - 2v_3 = 16$$

$$3v_2 = 18$$

$$\therefore v_2 = 6V$$

$$v_3 = 2v_2 - 8 = 2(6) - 8 = 4V$$

2.14

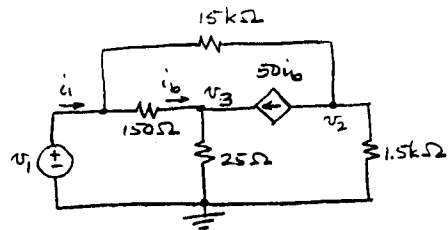

By KCL at node  $v_3$ ,

$$i_b + 50i_b = \frac{v_3}{25}$$

$$51i_b = \frac{v_3}{25}$$

$$\text{or } \frac{v_1 - v_3}{150} = \frac{v_3}{25}$$

$$51v_1 - 51v_3 = 6v_3$$

$$51v_1 = 57v_3$$

$$v_3 = \frac{51}{57}v_1$$

By KCL at node  $v_2$ ,

$$50i_b + \frac{v_2 - v_1}{15k} + \frac{v_2}{1.5k} = 0$$

$$50\left(\frac{v_1 - v_3}{150}\right) + \frac{v_2 - v_1}{15k} + \frac{v_2}{1.5k} = 0$$

$$5k v_1 - 5k v_3 + v_2 - v_1 + 10v_2 = 0$$

$$4999v_1 - 5000v_3 = -11v_2$$

$$4999v_1 - 5000\left(\frac{51}{57}\right)v_1 = -11v_2$$

$$525v_1 = -11v_2$$

$$\therefore \frac{v_2}{v_1} = \frac{525}{-11} = -47.7$$

(b) By KCL,  $i_1 = \frac{v_1 - v_2}{15k} + \frac{v_1 - v_3}{150}$


$$i_1 = \frac{v_1 - (-47.7v_1)}{15k} + \frac{v_1 - \frac{51}{57}v_1}{150}$$

$$\frac{i_1}{v_1} = \frac{48.7}{15k} + \frac{6/57}{150} = 3.24m + 0.702m$$

$$\frac{i_1}{v_1} = 3.94m$$

$$\frac{v_1}{i_1} = \frac{1}{3.94m} = 254\Omega$$

2.20

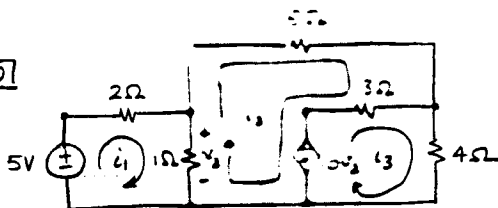

For mesh  $i_1$ , by KVL,

$$5 = 2i_1 + 1(i_1 - i_2)$$

$$3i_1 - i_2 = 5$$

For mesh  $i_2$ , by KVL,

$$5 - 2 \cdot 3(i_2 - i_1) - 10v_2 - v_2 = 0$$

$$5 - 2 \cdot 3 \cdot 3i_2 + 11[1(i_1 - i_2)] = 0$$

$$-11i_1 + 11i_2 - 3i_3 = 0$$

For mesh  $i_3$ , by KVL,

$$3(i_3 - i_2) + 4i_3 + 10v_2 = 0$$

$$3i_3 - 3i_2 + 4i_3 + 10[1(i_1 - i_2)] = 0$$

$$10i_1 - 13i_2 + 7i_3 = 0$$

$$D = \begin{vmatrix} 3 & -1 & 0 \\ -11 & -19 & -3 \\ 10 & -13 & 7 \end{vmatrix} = 399 \cdot 10 - 117 \cdot 77 = 235$$

$$D_1 = \begin{vmatrix} 5 & -1 & 0 \\ 0 & -19 & -3 \\ 0 & -13 & 7 \end{vmatrix} = 665 - 117 = 470$$

$$\therefore i_1 = \frac{D_1}{D} = \frac{470}{235} = 2A$$


$$D_2 = \begin{vmatrix} 3 & 5 & 0 \\ -11 & 0 & -3 \\ 10 & 0 & 7 \end{vmatrix} = -150 + 385 = 235$$

$$\therefore i_2 = \frac{D_2}{D} = \frac{235}{235} = 1A$$

$$D_3 = \begin{vmatrix} 3 & -1 & 5 \\ -11 & -19 & 0 \\ 10 & -13 & 0 \end{vmatrix} = 715 - 950 = -235$$

$$\therefore i_3 = \frac{D_3}{D} = \frac{-235}{235} = -1A$$

2.24

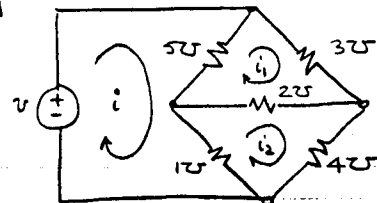

By KVL for mesh  $i_1$ ,

$$v = \frac{1}{2}(i_1 - i_2) + \frac{1}{4}(i_1 - i_2)$$

$$5V = i_1 - i_2 + 5i_1 - 5i_2$$

$$6i_1 - i_2 - 5i_2 = 5V$$

By KVL for mesh  $i_2$ ,

$$\frac{1}{3}i_1 + \frac{1}{2}(i_1 - i_2) + \frac{1}{5}(i_1 - i_2) = 0$$

$$10i_1 + 15i_1 - 15i_2 + 6i_1 - 6i_2 = 0$$

$$-6i_1 + 3i_1 - 15i_2 = 0$$

By KVL for mesh  $i_2$ ,

$$\frac{1}{4}i_2 + \frac{1}{4}(i_2 - i_1) + \frac{1}{2}(i_2 - i_1) = 0$$

$$i_2 + 4i_2 - 4i_1 + 2i_2 - 2i_1 = 0$$

$$-4i_1 - 2i_1 + 7i_2 = 0$$

$$D = \begin{vmatrix} 6 & -1 & -5 \\ -6 & 31 & -15 \\ -4 & -2 & 7 \end{vmatrix} = 1302 - 60 - 60 - 620 - 180 - 42 = 340$$


$$D_i = \begin{vmatrix} 5V & -1 & -5 \\ 0 & 31 & -15 \\ 0 & -2 & 7 \end{vmatrix} = 1085V - 150V = 935V$$

$$\therefore i = \frac{D_i}{D} = \frac{935V}{340}$$

Hence,

$$G = \frac{i}{v} = \frac{935}{340} = \frac{11}{4} = 2.75S$$

2.28

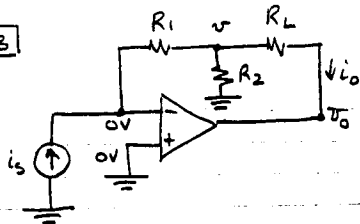

(a) By KCL at the inverting input, By KCL at node v,  

$$i_s = \frac{v}{R_1} \Rightarrow v = -R_1 i_s$$

$$\frac{v}{R_1} + \frac{v}{R_2} + \frac{v - v_o}{R_L} = 0$$

$$\frac{-R_1 i_s}{R_1} - \frac{R_1 i_s}{R_2} - \frac{R_1 i_s}{R_L} = \frac{v_o}{R_L}$$


$$\therefore v_o = -R_L i_s - \frac{R_1 R_L}{R_2} i_s - R_1 i_s = -\left(R_L + R_1 + \frac{R_1 R_L}{R_2}\right) i_s$$

(b) 
$$i_o = \frac{v - v_o}{R_L} = \frac{-R_1 i_s + R_L i_s + R_1 i_s + \frac{R_1 R_L}{R_2} i_s}{R_L}$$

$$i_o = \frac{\left(R_L + \frac{R_1 R_L}{R_2}\right) i_s}{R_L}$$

$$i_o = \left(1 + \frac{R_1}{R_2}\right) i_s$$

2.30

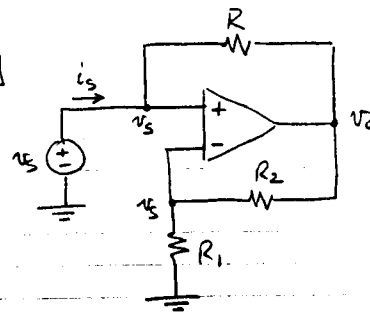

(a) By KCL at the inverting input of the op amp,  

$$\frac{v_s}{R_1} + \frac{v_s - v_o}{R_2} = 0$$

$$R_2 v_s + R_1 v_s - R_1 v_o = 0$$

$$(R_1 + R_2) v_s = R_1 v_o$$


$$\therefore v_o = \frac{R_1 + R_2}{R_1} v_s = \left(1 + \frac{R_2}{R_1}\right) v_s$$

(b) 
$$i_s = \frac{v_s - v_o}{R} = \frac{v_s - \frac{R_1 + R_2}{R_1} v_s}{R} = \frac{R_1 v_s - (R_1 + R_2) v_s}{R_1 R}$$

$$i_s = \frac{-R_2 v_s}{R_1 R}$$


$$\therefore \frac{v_s}{i_s} = -\frac{R_1 R}{R_2}$$

2.37

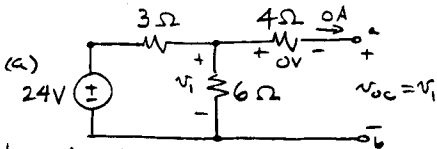


By voltage division,
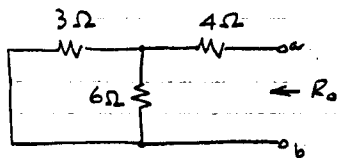
$$v_{oc} = \frac{6}{3+6} (24) = \frac{2}{3} (24) = \underline{16V}$$



$$R_o = 4 + 3 \parallel 6 = 4 + \frac{(3)(6)}{3+6} = 4 + \frac{18}{9} = \underline{6\Omega}$$


(b)

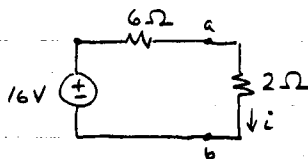

By KVL,  $16 = 6i + 2i = 8i \Rightarrow i = \frac{16}{8} = 2A$

$$\therefore p_2 = 2i^2 = 2(2)^2 = \underline{8W}$$


(c)

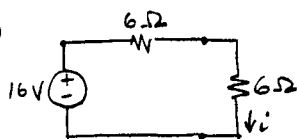

$$i = \frac{16}{6+6} = \frac{16}{12} = \frac{4}{3} A$$

$$P_6 = 6i^2 = 6\left(\frac{4}{3}\right)^2 = \underline{10.7W}$$

2.39

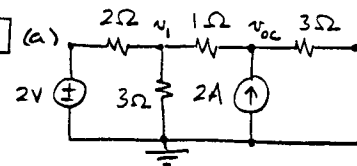

By KCL at node v1,  

$$\frac{v_1 - 2}{2} + \frac{v_1}{3} + \frac{v_1 - v_{oc}}{1} = 0$$

$$3v_1 - 6 + 2v_1 + 6v_1 - 6v_{oc} = 0$$

$$11v_1 - 6v_{oc} = 6$$

By KCL at node v\_{oc},

$$\frac{v_{oc} - 2}{1} + 2 = 0$$


$$v_{oc} - 2 = -2$$

$$\therefore 11(v_{oc} - 2) - 6v_{oc} = 6$$

$$11v_{oc} - 22 - 6v_{oc} = 6$$

$$5v_{oc} = 28$$
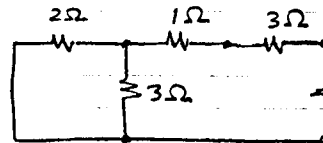
$$v_{oc} = \frac{28}{5} = \underline{5.6V}$$




$$R_o = 2 \parallel 1 + 3$$

$$R_o = \frac{(2)(1)}{2+1} + 3$$

$$R_o = \frac{2}{5} + 3 = \frac{26}{5} = \underline{5.2\Omega}$$


(b)

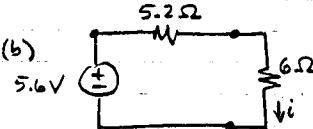

$$i = \frac{5.6}{5.2+6} = \underline{0.5A}$$

$$P_6 = 6i^2 = 6(0.5)^2 = \underline{1.5W}$$

(c)

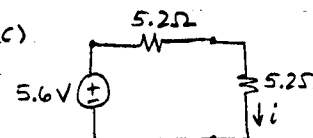

$$i = \frac{28/5}{26/5 + 26/5} = \frac{28}{52} = \frac{7}{13} A$$

$$P_{5.2} = 5.2 \left(\frac{7}{13}\right)^2 = \underline{1.51W}$$