
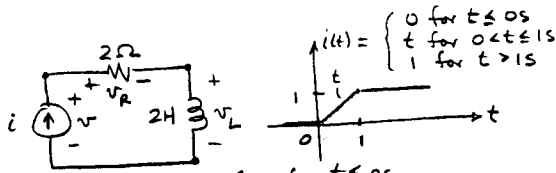



3.5

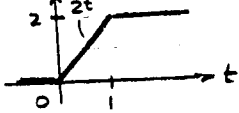


$$(a) v_R(t) = R i(t) = 2i(t) = \begin{cases} 0 & \text{for } t \leq 0 \\ 2t & \text{for } 0 < t \leq 1 \\ 2 & \text{for } t > 1 \end{cases}$$



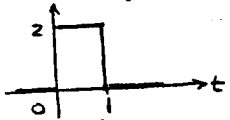
$$(b) v_L(t) = L \frac{di(t)}{dt} = 2 \frac{di(t)}{dt} = \begin{cases} 0 & \text{for } t \leq 0 \\ 2 & \text{for } 0 < t \leq 1 \\ 0 & \text{for } t > 1 \end{cases}$$


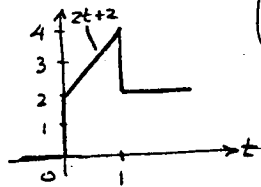
$$(c) v(t) = v_R(t) + v_L(t) = \begin{cases} 0 & \text{for } t \leq 0 \\ 2t+2 & \text{for } 0 < t \leq 1 \\ 2 & \text{for } t > 1 \end{cases}$$




3.7

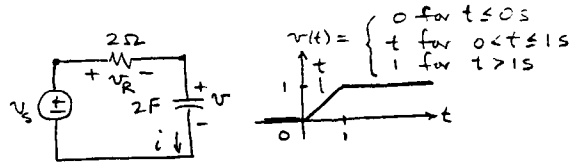


$$(a) i(t) = C \frac{dv(t)}{dt} = 2 \frac{dv(t)}{dt} = \begin{cases} 0 & \text{for } t \leq 0 \\ 2 & \text{for } 0 < t \leq 1 \\ 0 & \text{for } t > 1 \end{cases}$$


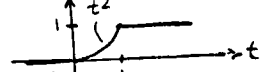
$$(b) w_C(t) = \frac{1}{2} C v^2(t) = v^2(t) = \begin{cases} 0 & \text{for } t \leq 0 \\ t^2 & \text{for } 0 < t \leq 1 \\ 1 & \text{for } t > 1 \end{cases}$$



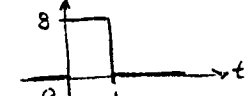
$$(c) p_R(t) = R i^2(t) = 2i^2(t) = \begin{cases} 0 & \text{for } t \leq 0 \\ 8 & \text{for } 0 < t \leq 1 \\ 0 & \text{for } t > 1 \end{cases}$$




$$(d) v_R(t) = R i(t) = 2i(t) = \begin{cases} 0 & \text{for } t \leq 0 \\ 4 & \text{for } 0 < t \leq 1 \\ 0 & \text{for } t > 1 \end{cases}$$


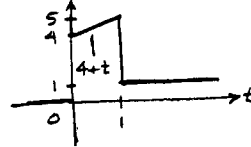
$$(e) v_s(t) = v_R(t) + v(t) = \begin{cases} 0 & \text{for } t \leq 0 \\ 4+t & \text{for } 0 < t \leq 1 \\ 1 & \text{for } t > 1 \end{cases}$$



4.7

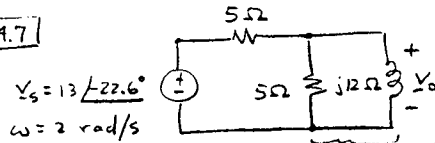

$$\omega = 2 \text{ rad/s}$$

$$Z = \frac{5(j12)}{5+j12} = \frac{j60}{5+j12} \cdot \frac{5-j12}{5-j12}$$

$$Z = \frac{j300 + 720}{25 + 144} = \frac{720}{169} + j\frac{300}{169}$$

$$Z = 4.26 + j1.78$$


By voltage division,

$$V_o = \frac{Z}{5+Z} V_s = \frac{4.26 + j1.78}{5 + (4.26 + j1.78)} (13 \angle -22.6^\circ)$$

$$V_o = \frac{4.62 \angle 22.7^\circ}{9.43 \angle 10.9^\circ} (13 \angle -22.6^\circ) = 6.37 \angle -10.8^\circ$$

Thus,

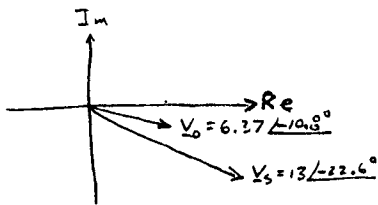
$$v_o(t) = 6.37 \cos(2t - 10.8^\circ) \text{ V}$$



Since $\text{ang } V_o = -10.8^\circ > \text{ang } V_s = -22.6^\circ$, $v_o(t)$ leads $v_s(t)$ by $-10.8^\circ + 22.6^\circ = 11.8^\circ$

Hence, the circuit is a lead network.

4.9

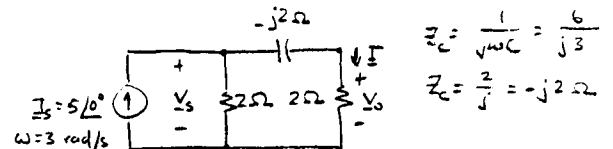

By current division,

$$I = \frac{2}{2 + (-j2)} I_s = \frac{2}{4 - j2} I_s = \frac{1}{2 - j} I_s = \frac{1}{\sqrt{5} \angle -26.6^\circ} (5 \angle 0^\circ)$$

$$I = \sqrt{5} \angle 26.6^\circ$$

$$\therefore V_o = 2I = 2(\sqrt{5} \angle 26.6^\circ) = 4.47 \angle 26.6^\circ$$

Hence,

$$v_o(t) = 4.47 \cos(3t + 26.6^\circ) \text{ V}$$


$$\text{Also, } V_s = (2 - j2)I = (2\sqrt{2} \angle -45^\circ)(\sqrt{5} \angle 26.6^\circ) = 2\sqrt{10} \angle -18.4^\circ$$

$$V_s = 6.32 \angle -18.4^\circ$$

Hence,

$$v_s(t) = 6.32 \cos(3t - 18.4^\circ) \text{ V}$$

4.12

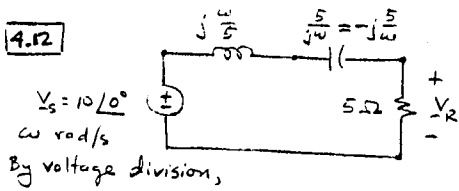

By voltage division,

$$V_R = \frac{5}{5 + j\frac{\omega}{5} - j\frac{\omega}{5}} V_s = \frac{5}{5 + j(\frac{\omega}{5} - \frac{\omega}{5})} (10\angle 0^\circ)$$

(a) $\omega = 1 \text{ rad/s}$

$$V_R = \frac{5}{5 + j(\frac{1}{5} - \frac{1}{5})} (10) = \frac{50}{5 - j4.8} = \frac{50}{6.93\angle -43.8^\circ}$$

$$V_R = 7.22\angle 43.8^\circ \Rightarrow V_R(t) \text{ leads } v_s(t) \text{ by } 43.8^\circ$$

(b) $\omega = 5 \text{ rad/s}$


$$V_R = \frac{5}{5 + j(1-1)} (10) = 10\angle 0^\circ \Rightarrow V_R(t) \text{ is in phase with } v_s(t)$$

(c) $\omega = 10 \text{ rad/s}$


$$V_R = \frac{5}{5 + j(2 - \frac{1}{2})} (10) = \frac{50}{5 + j1.5} = \frac{50}{5.22\angle 16.7^\circ}$$

$$V_R = 9.58\angle -16.7^\circ \Rightarrow V_R(t) \text{ lags } v_s(t) \text{ by } 16.7^\circ$$

4.18

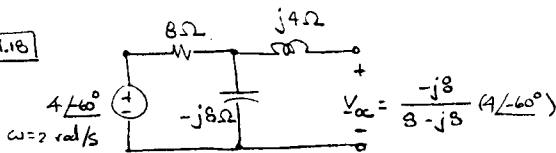

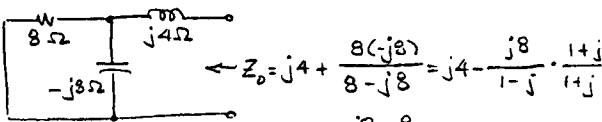
$$V_{oc} = \frac{-j}{1-j} (4\angle 60^\circ) = \frac{1\angle 90^\circ}{\sqrt{2}\angle 45^\circ} (4\angle 60^\circ) = 2\sqrt{2}\angle -105^\circ$$



$$Z_0 = j4 + \frac{8(-j8)}{8-j8} = j4 - \frac{j8}{1-j} \cdot \frac{1+j}{1+j}$$

$$Z_0 = j4 - \frac{j8-8}{1+1} = j4 - (j4-4)$$

$$Z_0 = 4\Omega$$

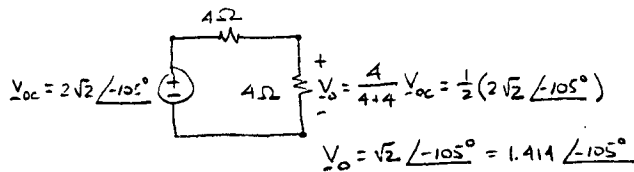


$$V_0 = \frac{4}{4+4} V_{oc} = \frac{1}{2} (2\sqrt{2}\angle -105^\circ)$$

$$V_0 = \sqrt{2}\angle -105^\circ = 1.414\angle -105^\circ$$

$$\therefore v_0(t) = \sqrt{2} \cos(2t - 105^\circ) = 1.41 \cos(2t - 105^\circ) \text{ V}$$

4.16

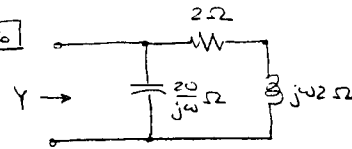

$$Y = \frac{j\omega}{20} + \frac{1}{2 + j\omega 2}$$

$$Y = \frac{j\omega}{20} + \frac{1}{2 + j\omega 2} \cdot \frac{2 - j\omega 2}{2 - j\omega 2}$$

$$= \frac{j\omega}{20} + \frac{2 - j\omega 2}{4 + 4\omega^2} = \frac{j\omega}{20} + \frac{1 - j\omega}{2 + 2\omega^2}$$


$$= \frac{(2 + 2\omega^2)j\omega + 20(1 - j\omega)}{20(2 + 2\omega^2)} = \frac{j\omega 2 + j\omega^3 2 + 20 - j\omega 20}{20(2 + 2\omega^2)}$$

$$= \frac{20 + j\omega^3 2 - j\omega 18}{20(2 + 2\omega^2)} = \frac{10 + j\omega^3 - j\omega 9}{20(1 + \omega^2)}$$

$$= \frac{10}{20(1 + \omega^2)} + \frac{j\omega(\omega^2 - 9)}{20(1 + \omega^2)}$$

$$= \frac{1}{2(\omega^2 + 1)} + j \frac{\omega(\omega^2 - 9)}{20(\omega^2 + 1)}$$

4.29

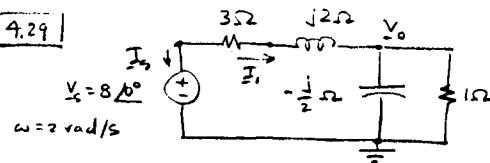

By KCL at node V_0 ,

$$\frac{V_0 - 8}{3 + j2} + \frac{V_0}{-j/2} + \frac{V_0}{1} = 0$$

$$\frac{V_0 - 8}{3 + j2} + j2V_0 + V_0 = 0$$

$$V_0 - 8 + (3 + j2)(j2V_0) + (3 + j2)V_0 = 0$$

$$V_0 - 8 - 4V_0 + j6V_0 + 3V_0 + j2V_0 = 0$$

$$j8V_0 = 8$$

$$V_0 = \frac{8}{j8} = -j1 = 1\angle -90^\circ \Rightarrow I_1 = \frac{V_0 - V_0}{3 + j2} = \frac{8 + j}{3 + j2} = \frac{\sqrt{65}\angle 7.13^\circ}{\sqrt{13}\angle 33.7^\circ}$$

$$I_1 = \sqrt{5}\angle 26.6^\circ$$

$$I_2 = -I_1 = (-1)\sqrt{5}\angle 26.6^\circ = \sqrt{5}\angle -153.4^\circ$$

For 3-Ω resistor,

$$P_3 = \frac{1}{2} R_3 |I_1|^2 = \frac{1}{2} (3) (\sqrt{5})^2 = 7.5 \text{ W}$$

For 1-Ω resistor, $P_1 = \frac{1}{2} \frac{|V_0|^2}{R_1} = \frac{1}{2} \frac{(1)^2}{1} = 0.5 \text{ W}$

For inductor, $P_L = 0 \text{ W}$
 For capacitor, $P_C = 0 \text{ W}$
 For voltage source, } by inspection

$$P_S = \frac{1}{2} |V_S| |I_S| \cos[\text{ang}(V_S) - \text{ang}(I_S)]$$

$$P_S = \frac{1}{2} (8) (\sqrt{5}) \cos(0^\circ + 153.4^\circ) = -8.0 \text{ W}$$