

11.33 (the text solution considers $\overline{(\overline{A+B})(\overline{A+B})} = A+B$)

But the actual problem was

$$\overline{(\overline{A+B})(\overline{A+B})} = A\overline{B} + \overline{A}B + \overline{(\overline{A+B})} \quad (\text{de Morgan})$$

$$\begin{aligned} &= A\overline{B} + \overline{A}B + A + \overline{B} \quad (") \\ &= (\overline{A}B + \overline{B}) + (A + \overline{A}B) \quad (\text{rearrange}) \\ &= \overline{B} + \underbrace{(A + \overline{A})}_{1}(\overline{A+B}) \quad (\text{absorption, distrib. law}) \\ &= \underbrace{\overline{B} + B}_{1} + A = \underline{1} \end{aligned}$$

11.37 $AB + \overline{A}C = (AB + \overline{A}BC) + (\overline{A}C + \overline{A}C\overline{B})$ since $A = A + AB$
 $= (AB + \overline{A}C) + (\overline{A}C\overline{B} + \overline{A}C\overline{A}B)$ commutative laws
 $= AB + \overline{A}C + (\overline{A} + \overline{A})\overline{B}C$ distributive & comm.
 $= AB + \overline{A}C + \overline{B}C$ $A + \overline{A} = 1, 1 \cdot A = A$
 $= \overline{A}C + AB + \overline{B}C$ commutative law
 $= \overline{A}A + \overline{A}C + AB + \overline{B}C$ since $\overline{A}A = 0$
 $= \overline{A}(A+C) + B(A+C)$ distributive law
 $= (\overline{A} + B)(A+C)$ distributive law

11.46



A	B	C	A+B	B+C	A+C	F = (A+B)(B+C)(A+C)
0	0	0	0	0	0	0
0	0	1	0	1	1	0
0	1	0	1	1	0	0
0	1	1	1	1	1	1
1	0	0	1	0	1	0
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1

12.17

A	B	C	D	E	F
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	1
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	1	1	1
1	1	0	1	0	1
1	1	1	1	0	0

$D = m_4 + m_5 + m_6 + m_7$
 $E = m_2 + m_3 + m_4 + m_5$
 $F = m_1 + m_2 + m_5 + m_6$
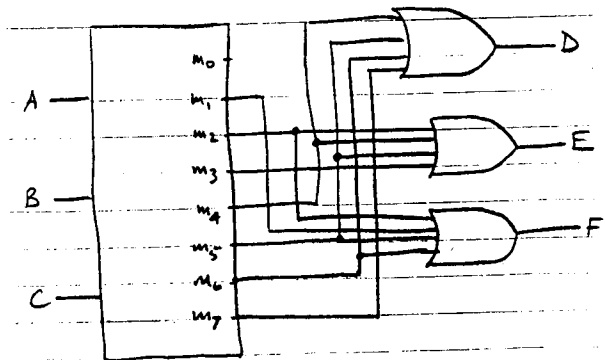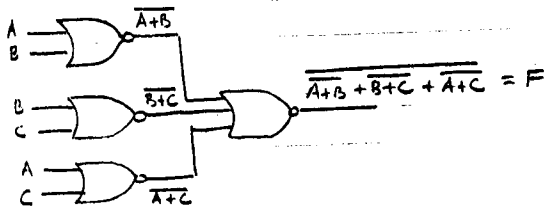
$$F = \overline{(\overline{A+B})(\overline{B+C})(\overline{A+C})} = \overline{\overline{A+B} + \overline{B+C} + \overline{A+C}}$$



11.51


(a)

BC	00	01	11	10
0		1		1
1	1		1	

$F = \overline{A}BC + \overline{A}B\overline{C} + A\overline{B}C + ABC$
 cannot be simplified

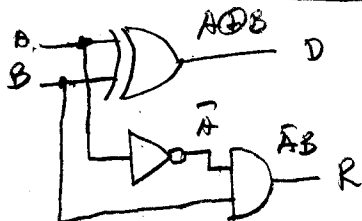12.3


$$D = A \oplus B, \quad R = \overline{A}B$$



12.22

$$\begin{aligned} F &= \overline{A}B\overline{C} + \overline{A}B\overline{C} + \overline{A}B\overline{C} + \overline{A}B\overline{C} \\ &= \overline{A}B(0) + \overline{A}B\overline{C} + \overline{A}B\overline{C} + \overline{A}B\overline{C} \\ &= \overline{A}B\overline{C} + \overline{A}B\overline{C} + \overline{A}B \\ &= \overline{A}B\overline{C} + \overline{A}(\overline{B}C + B) \\ &= \overline{A}B\overline{C} + \overline{A}(B+C) \\ &= \overline{A}B\overline{C} + \overline{A}B + \overline{A}C \\ &= (A+C)B + \overline{A}C \\ &= AB + AC + \overline{A}C \end{aligned}$$


11,53(c)

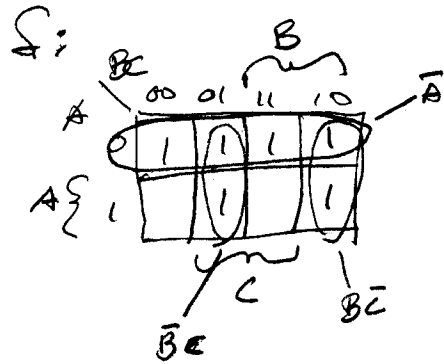


$$\underline{\underline{f = \bar{A} + \bar{B}C + B\bar{C}}}$$

• Implement with two-stage logic using NANDS & Inverters.

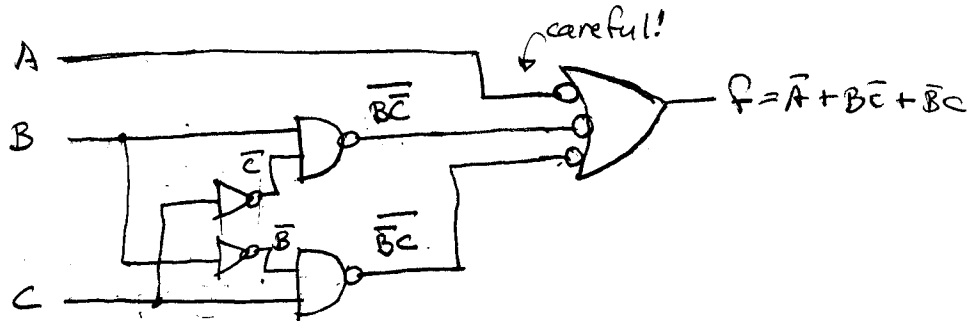[Note \equiv $\bar{A}BC = \bar{A} + \bar{B} + \bar{C}$ (de Morgan)]



11,57(b)

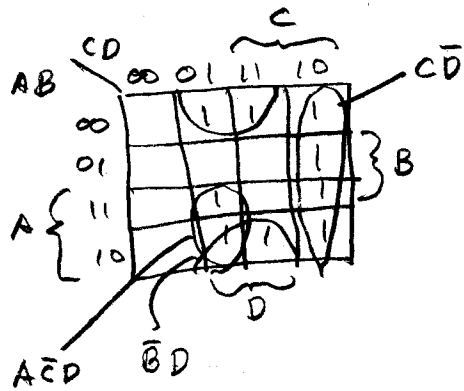

$$\underline{\underline{f = \bar{A}\bar{C}\bar{D} + \bar{B}D + C\bar{D}}}$$

