

Pulse Problem Solutions - Winter 2005

1. $V_{out}(t) = V(1 - e^{-t/\tau})$ $\tau = RC$.

R.T. = Rise time = $t_2 - t_1$

$0.9V = V(1 - e^{-t_2/\tau})$

$0.9 = 1 - e^{-t_2/\tau}$

$e^{-t_2/\tau} = 0.1$

$e^{t_2/\tau} = 10$

$t_2 = \tau \ln 10$

R.T. = $t_2 - t_1 = \tau \ln 9 = RC \ln 9$

R.T. = $\frac{\ln 9}{2\pi BW} = \frac{0.35}{BW}$

$0.1V = V(1 - e^{-t_1/\tau})$

$0.1 = 1 - e^{-t_1/\tau}$

$e^{-t_1/\tau} = 0.9$

$e^{t_1/\tau} = 10/9$

$t_1 = \tau (\ln 10 - \ln 9)$

but $RC = \frac{1}{2\pi f_c} = \frac{1}{2\pi BW}$

(or R.T. = 2.2τ)

2. $BW = f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi \times 1k\Omega \times 50pF} = 3.2 \text{ MHz}$.

R.T. = $0.35/BW = 0.35/3.2 \text{ MHz} = 110 \text{ ns}$.

3.

(a) $H(j\omega) = \frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2}$


where

$Z_1 = R_1 \parallel Z_{C1} = \frac{R_1 \frac{1}{j\omega C_1}}{R_1 + \frac{1}{j\omega C_1}} = \frac{R_1}{1 + j\omega R_1 C_1}$

$Z_2 = R_2 \parallel Z_{C2} = \frac{R_2}{1 + j\omega R_2 C_2}$

$H(j\omega) = \frac{\frac{R_2}{1 + j\omega R_2 C_2}}{\frac{R_1}{1 + j\omega R_1 C_1} + \frac{R_2}{1 + j\omega R_2 C_2}} = \frac{R_2}{\frac{R_1(1 + j\omega R_2 C_2)}{1 + j\omega R_1 C_1} + R_2}$

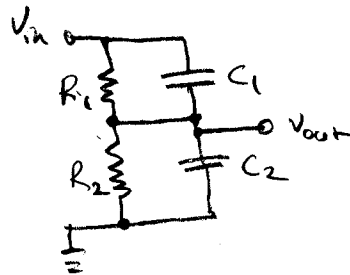$= \frac{R_2}{\frac{9R_2(1 + j\omega R_2 C_2)}{1 + j\omega(9R_2)C_2/9} + R_2} = \frac{R_2}{9R_2 + R_2} = 0.1$



$R_1 = 9R_2$

$C_1 = C_2/9$

$R_2 = 1M\Omega$

$C_2 = 50pF$

(note: $R_1 C_1 = R_2 C_2$)

3 (b). $Z_{in} = Z_1 + Z_2 = \frac{R_1}{1+j\omega R_1 C_1} + \frac{R_2}{1+j\omega R_2 C_2} = \frac{9R_2 + R_2}{1+j\omega R_2 C_2} = \frac{10R_2}{1+j\omega R_2 C_2}$
 $= \frac{10R_2}{1+j\omega(10R_2)(C_2/10)} = \frac{R'}{1+j\omega R' C'}$
 $R' = 10 \mu\Omega, C' = 5 \text{ pF}$

(c) Equiv. circuit:




Where $R_0 = R_5 || R' = 1 \text{ k}\Omega || 10 \text{ M}\Omega \approx 1 \text{ k}\Omega$

$V_b = \frac{R'}{R_5 + R'} V$
 $= \frac{10 \text{ M}\Omega}{1 \text{ k}\Omega + 10 \text{ M}\Omega} V \approx V$

$R.T. = 2.2 \tau = 2.2 \times R_0 C' = 2.2 \times (1 \text{ k}\Omega) \times 5 \text{ pF} = 11 \text{ ns}$. (or use BW relation)

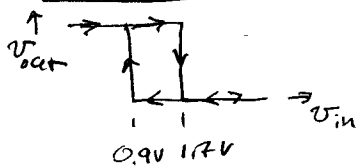
Pulse Problem 4: Note terminology of problem is a bit unclear.



0.9V = threshold for Schmitt trigger low to high transition. 1.7V = threshold for high to low.

Neglect Schmitt trigger propagation delay and assume the output is a step fun. (actual device will have delay, pulse rise time).

S.T. transfer fun.

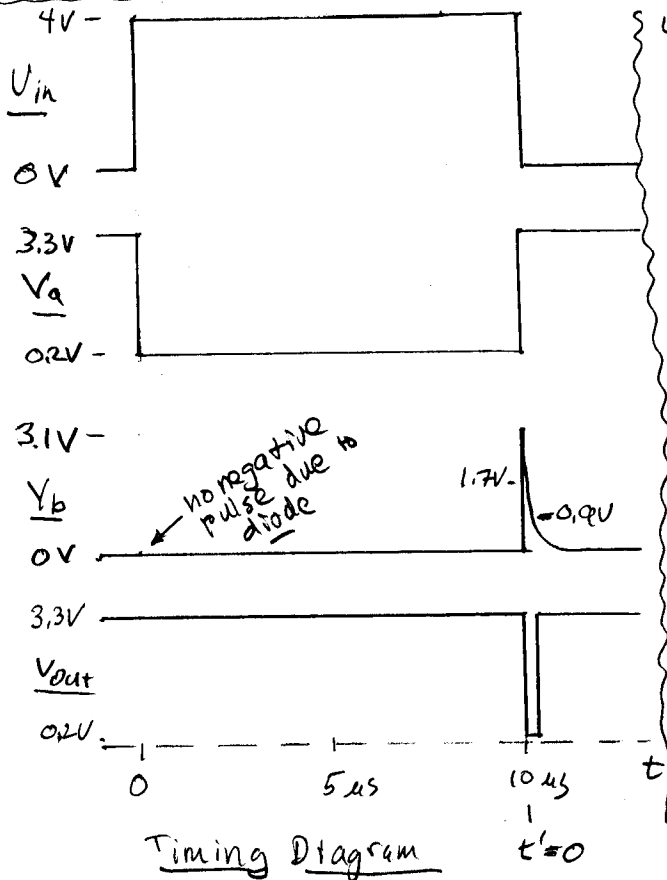

width of output pulse:

Consider V_b . At $t = 10 \mu\text{s}$, the positive-going edge of V_a leads to ($t \geq 10 \mu\text{s}$):

$V_b(t') = 3.1 \text{ V} (e^{-t'/\tau}) u(t')$

where $t' = t - 10 \mu\text{s}$, and

$\tau = RC = 1000 \mu \times 100 \times 10^{-12} \text{ F} = 0.10 \mu\text{s}$

The positive transition causes V_{out} to go to 3.3V at $t = 10 \mu\text{s}$. It falls to 0.2V when $V_b = 0.9 \text{ V}$.

$0.9 \text{ V} = 3.1 \text{ V} (e^{-t'/0.10 \mu\text{s}})$

$t' = 0.10 \mu\text{s} \ln(3.1/0.9) = 0.12 \mu\text{s}$

(width of "notch" in output pulse.)

⇒ circuit produces negative-going pulse synchronized with trailing edge of input pulse.