

Physics 116A Notes Fall 2004


David E. Pellett

Preliminary Draft v.0.8

- Notes Copyright 2004 David E. Pellett unless stated otherwise.
- References:
 - Text for course:
Fundamentals of Electrical Engineering, second edition, by Leonard S. Bobrow, published by Oxford University Press (1996)
 - Others as noted

BJT Temperature Dependence and Bias Stability

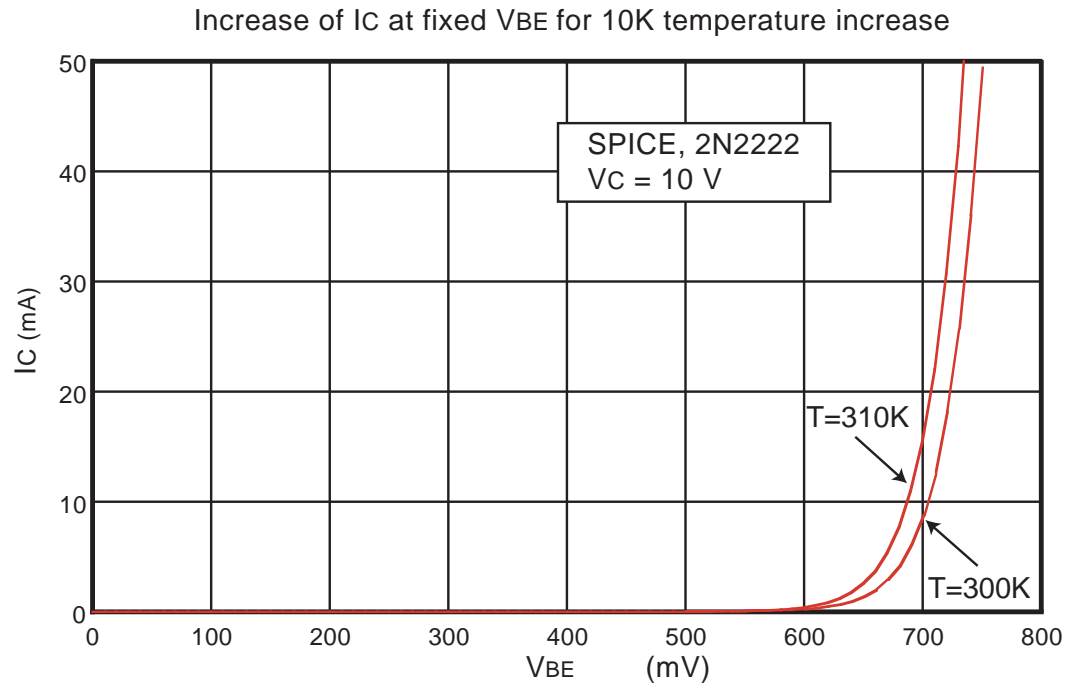
- SPICE analysis, $V_{CE} = 10\text{ V}$, emitter grounded, $T = 300\text{ K}$ and $T = 310\text{ K}$



- In active region, I_C increases significantly for 10 K temperature increase (I_E does the same)

Emitter Resistor Gives Bias Stability

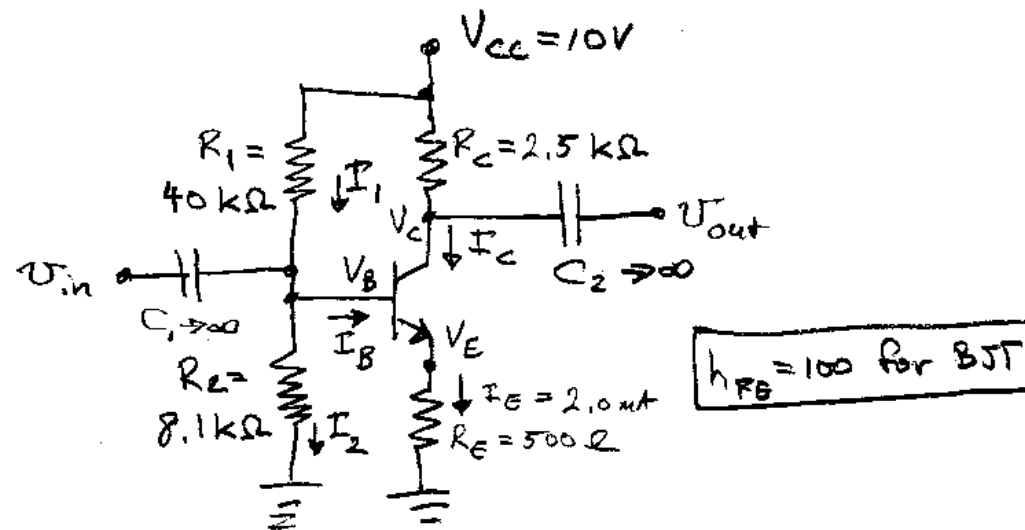- Due to the voltage drop across R_E , an increase in I_E causes a reduction in V_{BE} (since V_B is approximately constant)
- This negative feedback yields a stable operating point despite variations in temperature, etc.




- For example, if T increases, I_E increases for fixed V_{BE}
- But the increased I_E increases the voltage drop across R_E , raising V_E and reducing V_{BE} : this brings I_E back toward the design value

Comment on Negative Feedback and Gain

- The negative feedback also reduces the amplifier gain
- The AC gain can be recovered by bypassing R_E with a large C_E in parallel with R_E
- In this way one can bias stability and high gain
- This was shown in the last slide of the previous set of notes

Bias Stability with R_E : SPICE Example

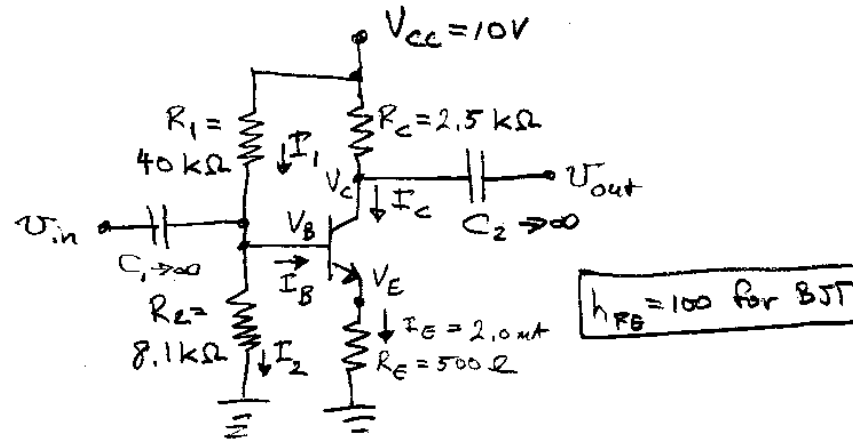
- Our initial estimate assumed $I_{E_Q} = 2$ mA and $h_{FE} = 100$. We calculated $V_{E_Q} = 1$ V, $V_{B_Q} = 1.7$ V and $V_{C_Q} = 5$ V



- Simulate using SPICE and a 2N2222 BJT at $T=300$ K and $T=310$ K
- At $T=300$ K, $I_{E_Q} = 1.89$ mA, $V_{E_Q} = 0.95$ V, $V_{B_Q} = 1.61$ V and $V_{C_Q} = 5.3$ V (reasonable agreement with our estimate—within 6%)
- At $T=310$ K, $I_{E_Q} = 1.93$ mA, $V_{E_Q} = 0.97$ V, $V_{B_Q} = 1.61$ V and $V_{C_Q} = 5.2$ V
- Q point is reasonably stable

SPICE Example without R_E

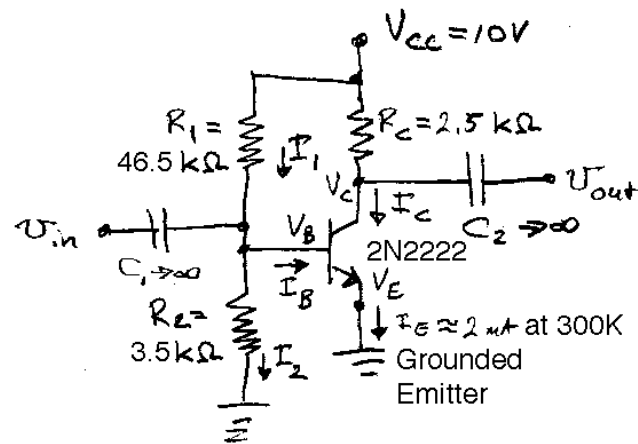- Now eliminate R_E and choose new values for $R_1 = 46.5 \text{ K}\Omega$ and $R_2 = 3.5 \text{ K}\Omega$ to give $I_{E_Q} \approx 2 \text{ mA}$ at $T=300\text{K}$ (using SPICE and a 2N2222 BJT)



- At $T=300 \text{ K}$, $I_{E_Q} = 2.1 \text{ mA}$, $V_{E_Q} = 0\text{V}$, $V_{B_Q} = 0.66\text{V}$ and $V_{C_Q} = 5.1\text{V}$
- At $T=310 \text{ K}$, $I_{E_Q} = 2.8 \text{ mA}$, $V_{E_Q} = 0\text{V}$, $V_{B_Q} = .65\text{V}$ and $V_{C_Q} = 3.6\text{V}$
- At $T=320 \text{ K}$, $I_{E_Q} = 3.5 \text{ mA}$, $V_{E_Q} = 0\text{V}$, $V_{B_Q} = .64\text{V}$ and $V_{C_Q} = 1.9\text{V}$
- Q point is not stable.** As T increases, I_{E_Q} increases and V_{C_Q} falls significantly. The BJT tends toward saturation with increasing T .