
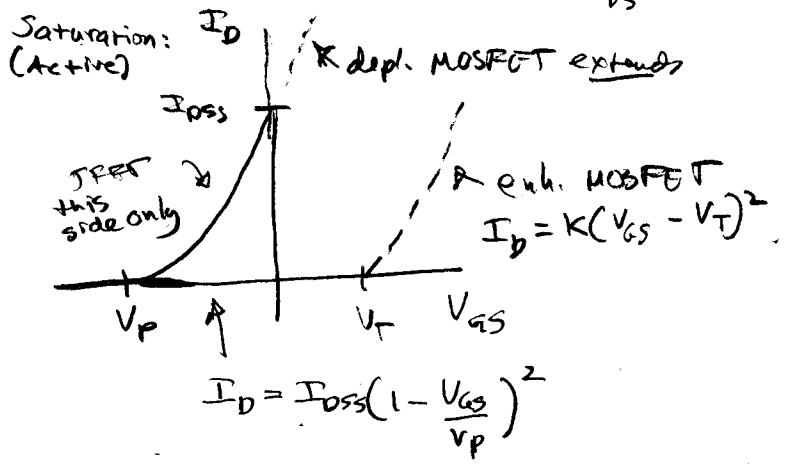


FET summary - stress the active region.



n-channel or p-channel (n-channel shown)
JFET or MOSFET (Metal-Oxide-Semiconductor Field-Effect Transistor)
↳ depletion or enhancement

$I_G \approx 0$
 $I_D = I_S$

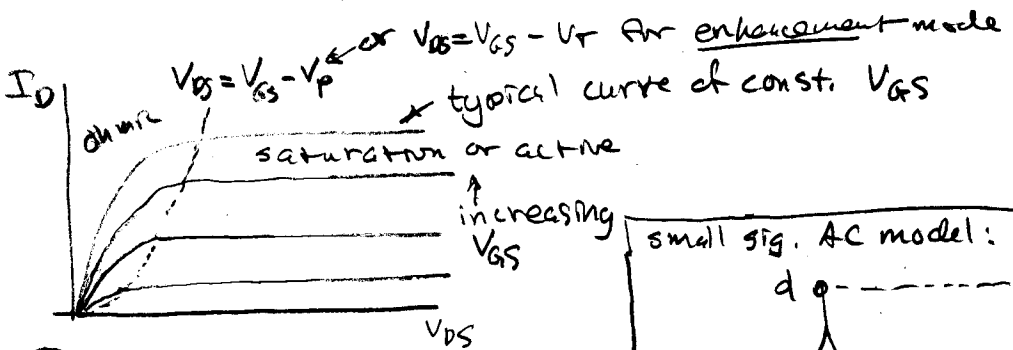

small sig. AC model:

$g_m = \frac{dI_D}{dV_{GS}} \Big|_Q = -\frac{2}{V_P} \sqrt{\frac{I_D I_{DSS}}{I_{DSS}}}$
 $(= 2K(V_{GS} - V_T) \text{ ENH. MOSFET})$
 May add r_d in parallel
 $r_d = \frac{dV_{GS}}{dI_D} \Big|_Q \approx \begin{cases} 100 \text{ k}\Omega \text{ (JFET)} \\ 10 \text{ k}\Omega \text{ (MOS)} \end{cases}$

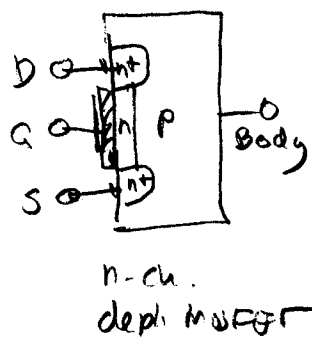
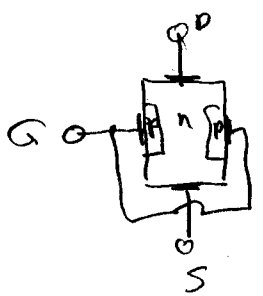


n-ch. enh. MOSFET

channel
Body
gate oxide layer

ENH. MOSFET GATE TOP VIEW
 $I_D = \frac{W \mu_n C_{ox}}{2L} (V_{GS} - V_T)^2$

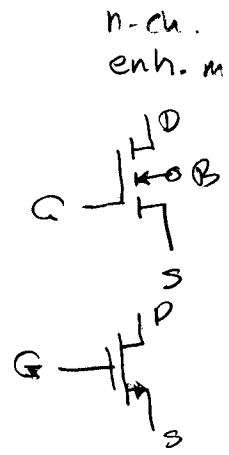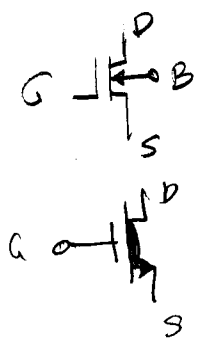$C_{ox} = C/A$ of oxide layer
 $= \frac{\epsilon_{ox}}{t_{ox}}$
 t_{ox} = oxide layer thickness
 $\mu_n = e^-$ mobility




(body connected to source)


* extra material, Enhancement MOSFET.
 possible numbers:
 $t_{ox} = 55 \text{ nm}$, $\epsilon_{ox} = 3.9 \times 8.85 \times 10^{-12} \text{ F/m}$
 $L \approx 1 \mu\text{m}$, $W \approx 12 \mu\text{m}$, $\mu_n = 0.13 \text{ m}^2 \text{ V}^{-1} \text{ s}^{-1}$

SOURCE FOLLOWER

CIRCUIT (Bias set by R_S)

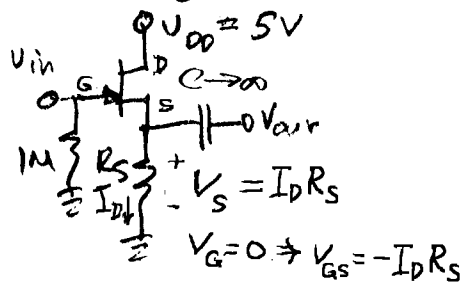

JFET CURVE

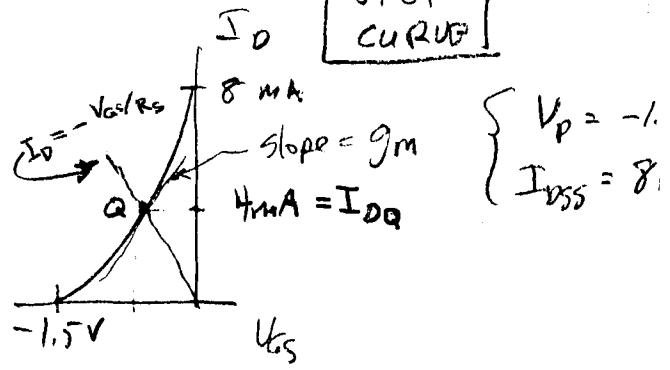

$I_{DQ} = 4mA$

Find V_{GSQ} and V_{DSQ} , verify active region, find R_S

$I_D = I_{DSS} (1 - V_{GS}/V_P)^2$ OPERATING POINT

$I_{DQ} = I_{DSS} (1 - V_{GSQ}/V_P)^2 = 4mA$

$(1 - V_{GSQ}/V_P) = \pm \sqrt{\frac{4mA}{8mA}} = \pm \sqrt{\frac{1}{2}}$

$\frac{V_{GSQ}}{V_P} = 1 \mp \frac{1}{\sqrt{2}} = 1 - \frac{1}{\sqrt{2}}$ (other root $< V_P$)

$V_{GSQ} = (1 - 0.707)V_P = 0.29 \times -1.5V = -0.44V$


since $V_{GQ} = 0$, $V_{SQ} = -V_{GSQ} = +0.44V$

$V_{DSQ} = V_D - V_{SQ} = 5V - 0.44V = 4.56V$

$4.56 = V_{DSQ} > V_{GS} - V_P = -0.44 + 1.5 = 1.06V$
Active - OK


$R_S = -\frac{V_{GSQ}}{I_{DQ}} = \frac{0.44V}{4mA} = 110\Omega$

Source follower voltage gain

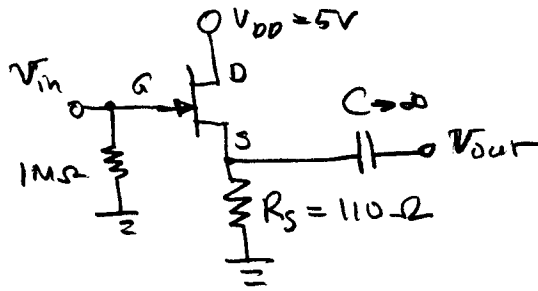

For JFET $V_p = -1.5V$
 $I_{DSS} = 8mA$
 $I_{DQ} = 4mA$

s.s. AC circuit: (ignore V_d)

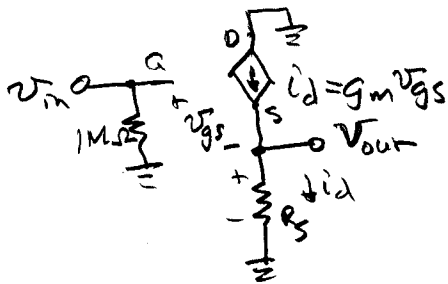

$$g_m = -\frac{2}{V_p} \sqrt{I_{DQ} I_{DSS}}$$

$$= -\frac{2}{-1.5V} \sqrt{4mA \times 8mA}$$

$$= \underline{7.5 mS}$$

$$A_v = \frac{v_{out}}{v_{in}}$$

$$v_{out} = i_d R_S$$


$$v_{in} = v_{gs} + v_{out} = v_{gs} + i_d R_S$$

$$A_v = \frac{i_d R_S}{v_{gs} + i_d R_S} = \frac{R_S}{\frac{v_{gs}}{i_d} + R_S} = \frac{R_S}{\frac{1}{g_m} + R_S} = \frac{110\Omega}{133\Omega + 110\Omega}$$

$$= 0.45$$

Can be improved using a current source in place of R_S , as was done in lab.

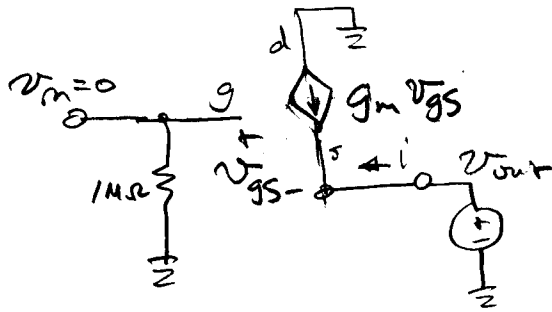Output impedance: $v_m = 0$. Apply source at v_{out}



Find:

$R_{eff} \equiv$ Effective resistance looking into source.


$$= \frac{v_{out}}{i} \quad \text{but } \begin{cases} i = -g_m v_{gs} \\ v_{out} = -v_{gs} \end{cases}$$

$$= \frac{-v_{gs}}{-g_m v_{gs}} = \frac{1}{g_m}$$

$$R_{out} = R_{eff} \parallel R_s = 133\Omega \parallel 110\Omega = \underline{\underline{60\Omega}}$$

Enhancement-mode MOSFET bias & common source amplifier

Based on Example 9.6 in text (p. 596)

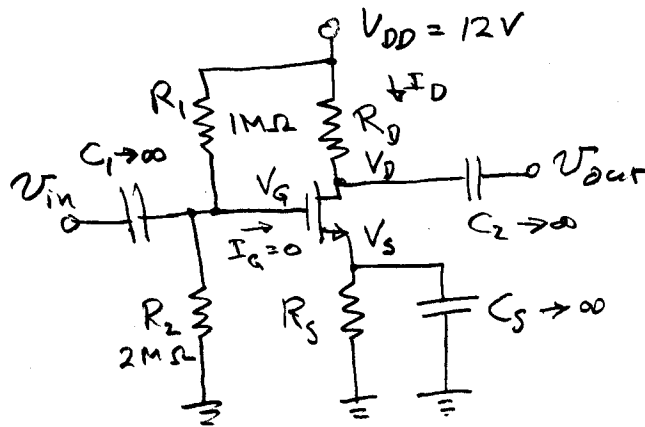

{ enh. mode
 n-channel MOSFET
 $K = 0.25 \text{ mA/V}^2$
 $V_T = 2 \text{ V}$

Q-point:

$$I_{DQ} = 4 \text{ mA}$$

$$V_{DSQ} = 6 \text{ V}$$

R_1 & R_2 are given - as shown. Find R_S , R_D , verify "active" region operation.

$$I_S = I_D \text{ (since } I_G = 0)$$

$$V_{DSQ} = V_{DD} - I_{DQ}(R_D + R_S)$$

$$6 \text{ V} = 12 \text{ V} - 4 \text{ mA}(R_D + R_S)$$

$$(R_D + R_S) = \frac{6 \text{ V}}{4 \text{ mA}} = 1500 \Omega \quad (1)$$

Find V_{GSQ} :

$$I_{DQ} = K(V_{GSQ} - V_T)^2$$

$$4 \text{ mA} = 0.25 \text{ mA/V}^2 (V_{GSQ} - 2 \text{ V})^2$$

$$V_{GSQ} - 2 \text{ V} = \pm 4 \text{ V} \Rightarrow V_{GSQ} = \underline{6 \text{ V}} \text{ (+ chosen, - below } V_T)$$

Find V_S :

$$V_G = V_{DD} \frac{R_2}{R_1 + R_2} = 12 \text{ V} \cdot \frac{2}{3} = \underline{8 \text{ V}}$$

$$V_{GSQ} = V_G - V_S \Rightarrow V_S = V_G - V_{GSQ} = 8 \text{ V} - 6 \text{ V} = \underline{2 \text{ V}}$$


Find R_S , R_D :
(use eqn. (1) above)

$$R_S = \frac{V_S}{I_{DQ}} = \frac{2 \text{ V}}{4 \text{ mA}} = \underline{500 \Omega}, R_D = 1500 - R_S = \underline{1000 \Omega}$$

Active? $V_{DSQ} \stackrel{?}{>} V_{GSQ} - V_T$ $6 \text{ V} \stackrel{?}{>} 6 \text{ V} - 2 \text{ V} = 4 \text{ V}$ OK.

Find G_m

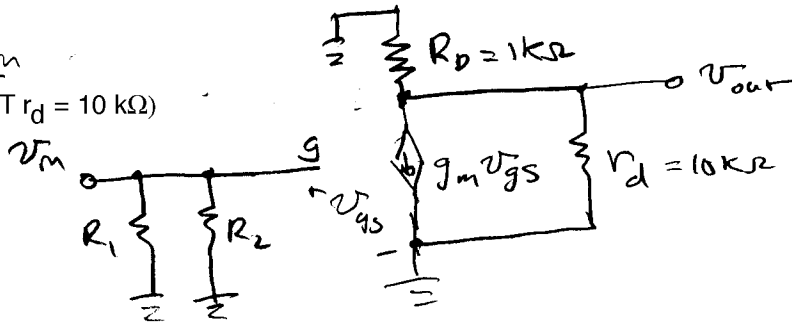(Assume MOSFET $r_d = 10 \text{ k}\Omega$)



$$v_m = v_{gs}$$

$$v_{out} = -g_m v_{gs} (r_d \parallel R_D)$$

$$A_v = -g_m (r_d \parallel R_D)$$

$$g_m = 2K (V_{GSQ} - V_T) = 2 \times 0.25 \text{ mA} / V_2 (6V - 2V) \\ = 2 \text{ mS}$$

$$A_v = -2 \text{ mS} \times 0.909 \text{ k}\Omega = \underline{\underline{-1.8}}$$