

Physics 116A
12/8/04

- * Clarify signs in phase shift oscillator example
- * Amplifier frequency response
 - Series, shunt capacitor corner freq.
 - Small signal models of BJT and FET showing shunt C's which limit HF response
 - Miller's Theorem
- * gain-BW product
- * BJT example (9.54)
- * FET example (9.57)

clarify sign in phase shift oscillator.

$AB = -1$ assumed negative feedback.

condition for oscillation:
"Barkhausen * Criterion"

Taking this into account, the amplifier

gain $A = R_F/R$. (-1 there already in $\triangleleft -1 \triangleright$)

For the RC network,

$$B = \frac{V_1}{V_0} = \frac{\omega^3 R^3 C^3}{\omega RC (\omega^2 R^2 C^2 - 5) + j(1 - 6\omega^2 R^2 C^2)}$$

B must be real for $AB = -1$ so


$$1 - 6\omega^2 R^2 C^2 = 0 \Rightarrow \omega = \omega_0 = \frac{1}{\sqrt{6}RC}$$

$$B = \frac{\omega_0^2 R^2 C^2}{(\omega_0^2 R^2 C^2 - 5)}, \quad \omega_0^2 R^2 C^2 = \frac{1}{6}$$

$$= \frac{1/6}{1/6 - 5} = \frac{1}{1 - 30} = -\frac{1}{29}$$

$$AB = -1 \Rightarrow \frac{R_F}{R} \left(-\frac{1}{29}\right) = -1$$


$$R_F = 29R$$

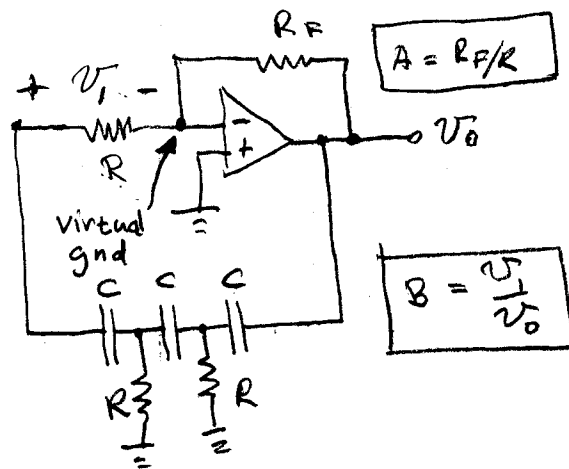

*German physicist, 1881-1956.

Simplified treatment of coupling capacitors at input or output stages of amplifiers. (Both source and load impedances are important... and must be known for an exact answer. If one is much larger than the other, simplifications are possible.)

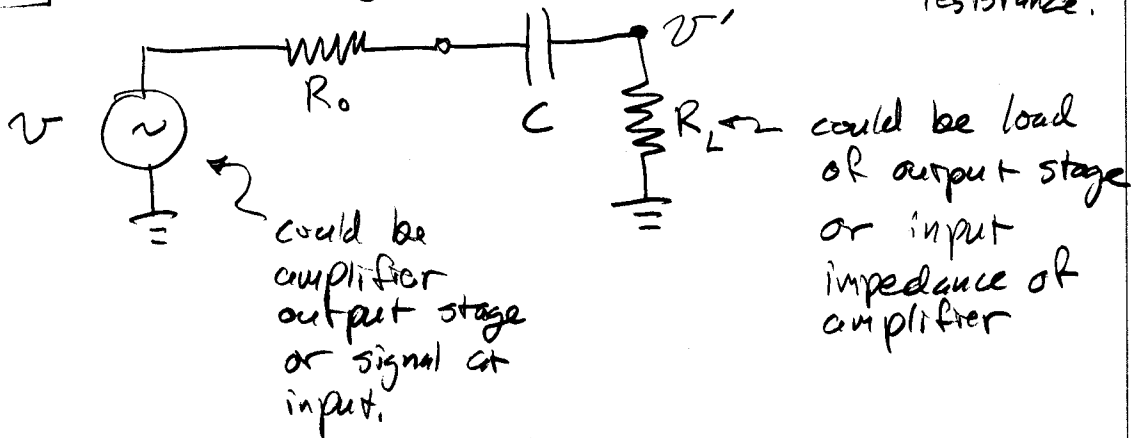High pass network usually looks like this: $R_0 =$ source resistance.




$v = v_0 e^{j\omega t}$. At high frequency, this is a resistive divider: $v' = \frac{R_L}{R_0 + R_L} v$.

$$\text{In general, } v' = v \frac{R_L}{R_0 + R_L + 1/j\omega C} = \left[\frac{v R_L}{R_0 + R_L} \right] \frac{(R_0 + R_L)}{(R_0 + R_L) + 1/j\omega C}$$

Thus this has a -3dB point relative to the value at high frequency where $|1/j\omega C| = R_0 + R_L$


$$\text{or } f_c = \frac{1}{2\pi(R_0 + R_L)C}$$

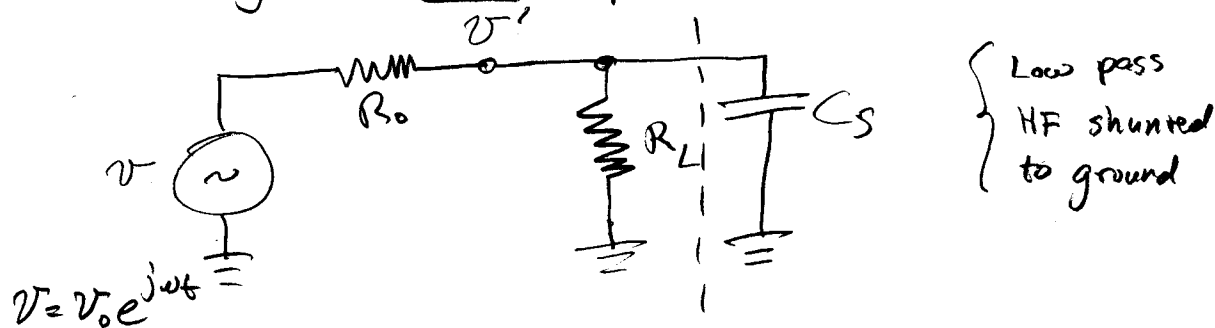Similarly, for shunt capacitance, we have:



At low frequency, $v' \approx \frac{R_L}{R_0 + R_L} v$.

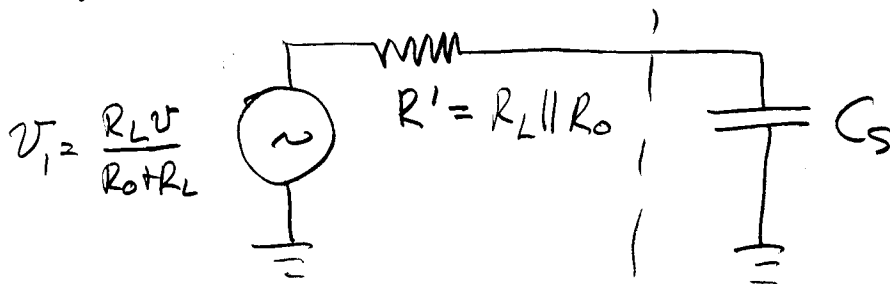The Thevenin equiv. of things to the left of the dotted line is



so $f_c = \frac{1}{2\pi R' C_S}$.

$R' = \frac{R_L R_0}{R_L + R_0}$.


If $R_L \gg R_0$ (but $R_0 \neq 0$), $R' \approx R_0$.

If we want f_c to be large*, R_0 must be small. [We could make R_L small but if R_0 is still large, $R_L / (R_0 + R_L)$ is small - signal reduced by voltage divider at input].

* e.g. HF response of amplifier.

Note we want f_c to be small for emitter (or source) bypass capacitor.



HF BJT model

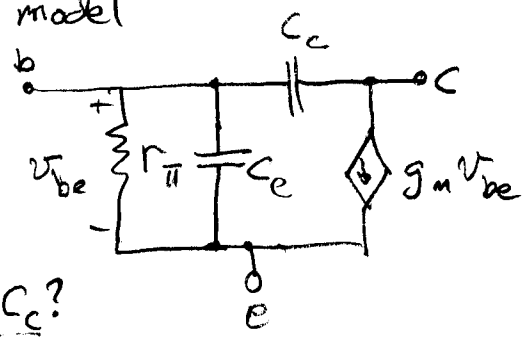

$C_c \approx 5 \text{ pF}$
 $C_e \approx 100 \text{ pF}$
 $g_m = \left. \frac{dI_c}{dV_{BE}} \right|_Q \approx \frac{1}{r_e}$
 $r_n \approx h_{fe} r_e$

What about C_c ?

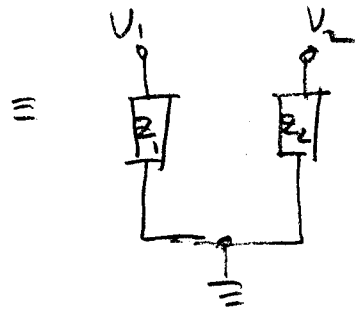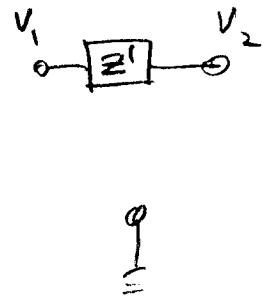Miller's Theorem:
IF $V_2/V_1 = k$
 (as for input and output nodes of a voltage amplifier)




$Z_1 = \frac{Z'}{1-k}$

$Z_1 = \frac{Z'}{1-k}, Z_2 = \frac{kZ'}{k-1}$

IF $Z' = 1/j\omega C'$ (capacitor) and $k = -A$ (inverting amplifier)
 then $C_1 = (A+1)C'$, $C_2 = \frac{A+1}{A}C'$.



HF BJT model with Miller's thm:

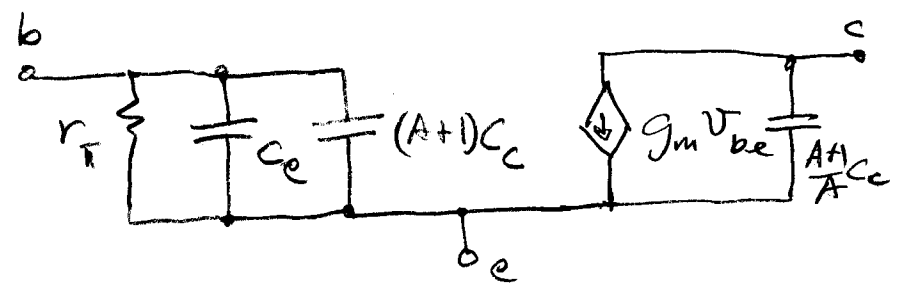

This allows us to separate input and output networks.

Miller's Theorem proof:

$$V_2/V_1 = k$$

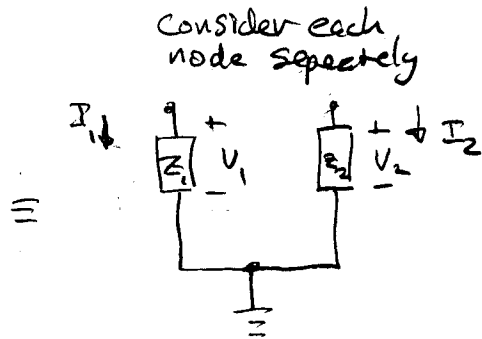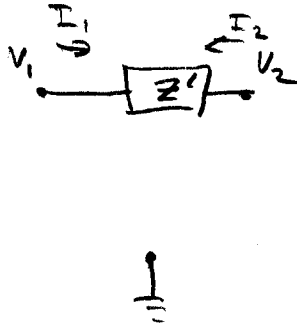

Same currents,
Same voltages.

$$I_1 = \frac{V_1 - V_2}{Z'}$$


$$= \frac{(1-k)V_1}{Z'}$$

$$\frac{V_1}{I_1} = Z_1 = \frac{Z'}{1-k}$$


$$I_2 = \frac{V_2 - V_1}{Z'} = \frac{V_2(1 - \frac{1}{k})}{Z'}$$

$$\frac{V_2}{I_2} = Z_2 = \frac{Z'}{1 - \frac{1}{k}} = \frac{kZ'}{k-1}$$

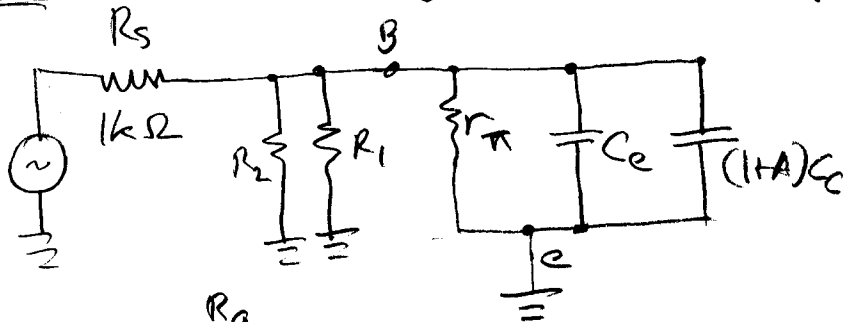Input stage after applying Miller's thm (high freq. case)



Equiv.:

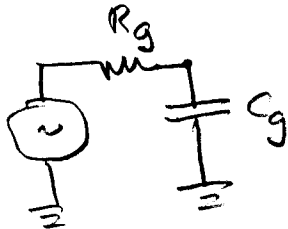


$$R_g = R_s \parallel R_1 \parallel R_2 \parallel r_e \quad f_c = \frac{1}{2\pi R_g C_g}$$


$$C_g = C_e + (1+A)C_c$$

(Following text notation - g must stand for "lag" (low pass) network)


Output stage

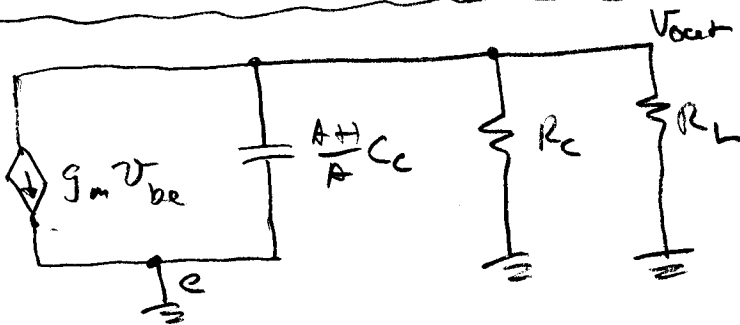


Norton:

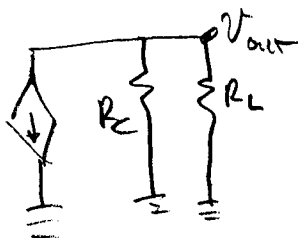

Thevenin

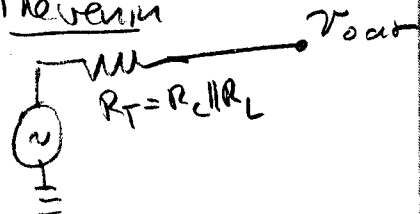

Circuit:

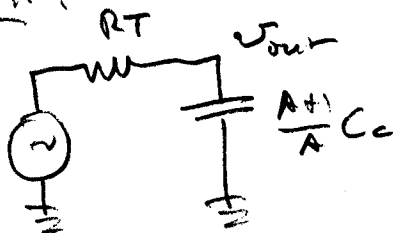

$$f_c = \frac{1}{2\pi R_T \left(\frac{A+1}{A}\right) C_c}$$

Note that the output circuit displays approx const. gain-bandwidth product (assuming LF extends to ∞)


$$BW = f_c$$

$$A = \frac{R_T}{r_e} = g_{mT} \gg 1 \quad (A_v = -A)$$

$$\text{Gain-BW product} = A \times BW = \frac{R_T}{r_e} \times \frac{1}{2\pi L_T \left(\frac{A+1}{A}\right) C_c} \approx \frac{1}{2\pi r_e C_c}$$

If the input circuit BW does not limit (i.e. \gg this BW) amp. BW, then we get this constant gain-BW product

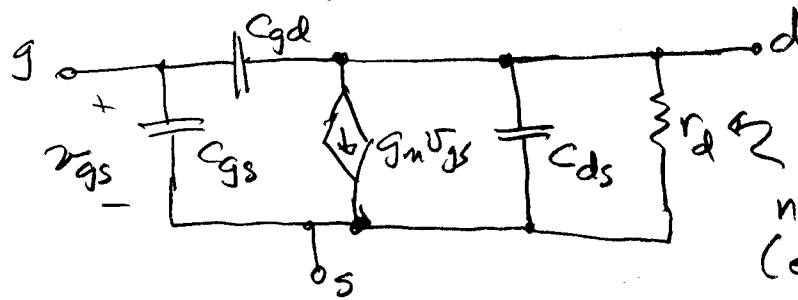Exact same analysis applies to FETs, except the FET model is slightly different:



$$C_{gs}, C_{gd} \approx 1-3 \text{ pF}$$

$$C_{ds} \approx 1 \text{ pF}$$

if necessary
(esp. MOSFET)
May neglect
for JFET


Again, split C_{gd} into (via Miller)

$(A+1)C_{gd}$ in input circuit

parallel to C_{gs} , $\left(\frac{A+1}{A}\right)C_{gd}$ in output

circuit \parallel to C_{ds} .

9.54

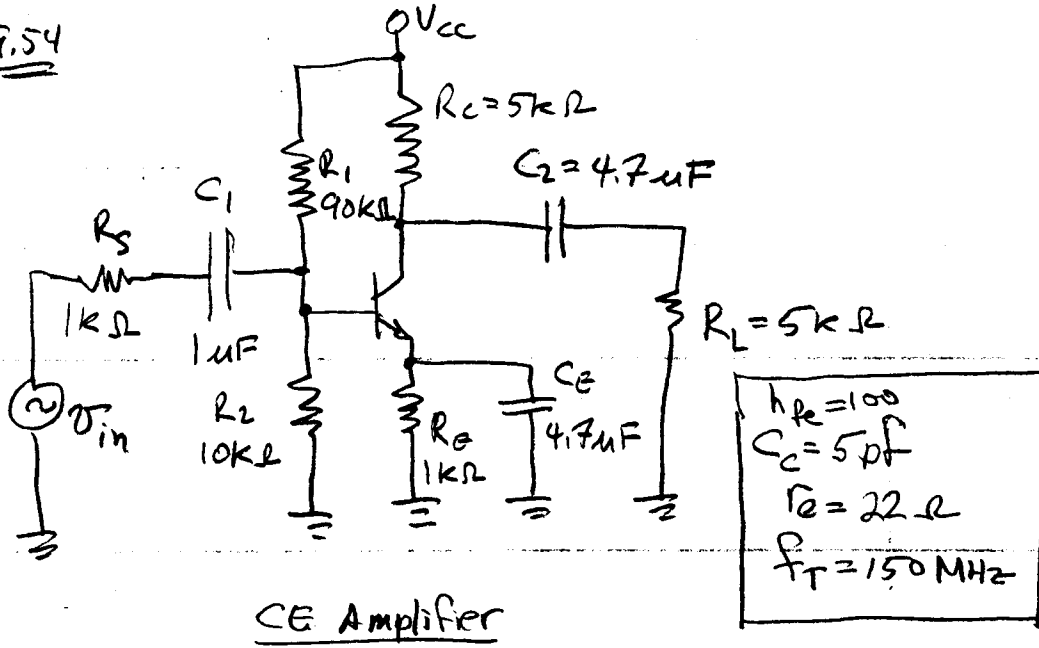

Terminology : $C_c \equiv C_{BC}$, $C_e \equiv C_{BE}$

$$f_T \equiv \text{current gain bandwidth product}$$

$$\approx \frac{1}{2\pi(C_c + C_e)r_e}$$

(a) Lower cutoff frequency: treat each part separately to see if any one part is dominant:

i) Input circuit (assume $C_E \rightarrow \infty$)

$$f_c = \frac{1}{2\pi(R_S + R_1 \parallel R_2 \parallel r_{\pi})C_1}$$

$$r_{\pi} \approx h_{fe}r_e = 2200\Omega$$

$$= \frac{1}{2\pi(1k\Omega + 1.77k\Omega) \times 1\mu F} = \underline{58 \text{ Hz}}$$

ii) Output circuit :

$$f_c = \frac{1}{2\pi(R_C + R_L)C_2} = \frac{1}{2\pi \times 10k\Omega \times 4.7\mu F} = \underline{3.4 \text{ Hz}}$$

iii) Emitter circuit HF f_c due to C_E shunt capacitance, assuming $C_1 \rightarrow \infty$ (ineffective below f_c):

$$R_{equiv} = \text{resistance looking into emitter} = r_e + \frac{R_1 \parallel R_2 \parallel R_S}{h_{fe} + 1}$$

$$= 22\Omega + \frac{1}{101}(900\Omega) \approx \underline{31\Omega}$$

$$f_c = \frac{1}{2\pi(R_{equiv} \parallel R_E)C_E} = \boxed{1.13 \text{ kHz}} \leftarrow \text{Determines LF -3dB point.}$$

9.54 (b) Upper cutoff frequency

i. Consider input (base) circuit with Miller effect w.r.t. $C_c \equiv C_{CB}$. We need to know mid-band gain, $A \equiv -A_v(\text{midband}) = \frac{R_c \parallel R_L}{r_e}$ for this circuit

$$A = \frac{2.5 \text{ k}\Omega}{22 \text{ k}\Omega} = 114$$

The text defines quantities which are equivalent to what was done in class: $\omega_g \equiv 2\pi f_B = \frac{1}{R_g C_g}$

where $R_g = R_s \parallel R_p \parallel r_{\pi}$ and $R_p = R_1 \parallel R_2$ (assumes R_E bypassed)

and $C_g = C_e + (1+A)C_c \equiv C_{BE} + (1-A_v)C_{BC}$.

Now we need C_e but we have

↑ Miller effect

$$C + C_e = \frac{1}{2\pi f_T r_e} = \frac{1}{2\pi \times 150 \text{ MHz} \times 22 \Omega} = 48 \text{ pF}$$

$$C_e = 48 \text{ pF} - 5 \text{ pF} = 43 \text{ pF}$$

$$C_g = 43 \text{ pF} + 115 \times 5 \text{ pF} = 618 \text{ pF}$$

$$f_c = \frac{1}{2\pi R_g C_g} = \frac{1}{2\pi \times 639 \Omega \times 618 \text{ pF}} = 403 \text{ kHz}$$

ii. Consider output (collector) circuit with Miller effect.

Again, the text defines quantities which are equivalent to what was done in class.

$$\omega_T \equiv 2\pi f_B = \frac{1}{R_T C_T} \text{ where}$$

Miller effect


$$R_T = R_c \parallel R_L \text{ and } C_T = \frac{1+A}{A} C_c \left(= \frac{A_v+1}{A_v} C_{BC} \right)$$

$$f_c = \frac{1}{2\pi \times 2.5 \text{ k}\Omega \times \frac{115}{114} \times 5 \text{ pF}} = 12.6 \text{ MHz}$$

Thus the input circuit dominates and the HF $f_c = 403 \text{ kHz}$.

(c) Bandwidth = $403 \text{ kHz} - 1 \text{ kHz} = \underline{\underline{402 \text{ kHz}}}$.

9.57

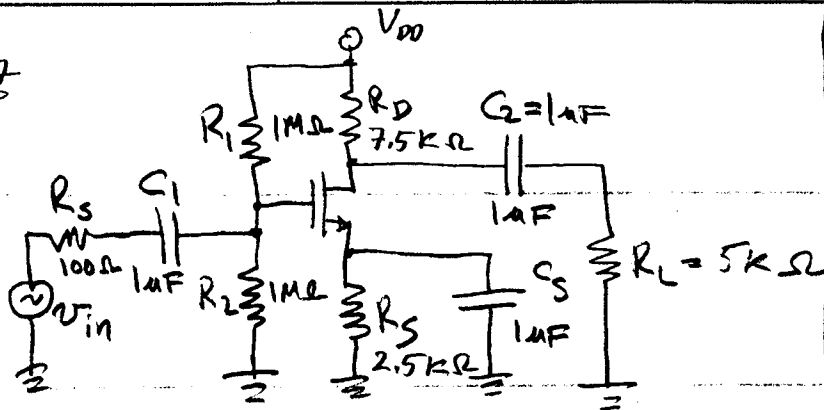

$g_m = 0.8 \text{ mS}$
 $C_{gs} = 4 \text{ pF}$
 $C_{gd} = 2 \text{ pF}$
 $C_{ds} = 1 \text{ pF}$
 $r_d = 10 \text{ k}\Omega$
 (see Fig. 9.37)

(a) Lower cutoff frequency:

i) Input circuit (assume $C_S \rightarrow \infty$)

$$f_c = \frac{1}{2\pi(R_s + R_1 \parallel R_2)C_1} = \frac{1}{2\pi(100\Omega + 500\text{k}\Omega) \times 1\mu\text{F}} = 0.3 \text{ Hz}$$

ii) Output circuit: assume $C_S \rightarrow \infty$ and take r_d into account (see p. 614):

$$f_c = \frac{1}{2\pi(R_D \parallel r_d + R_L)C_2} = \frac{1}{2\pi \times 9.29\text{k}\Omega \times 1\mu\text{F}} = 17 \text{ Hz}$$

iii) Source circuit HF f_c due to C_S shunt, taking r_d into account (see pp. 615-616):

$$f_c = \frac{1}{2\pi R_{os} C_S} \quad \left\{ \begin{array}{l} \text{where } R_{os} = R_S \parallel \frac{1}{g_m} \parallel r_d, \\ \text{according to text, with } r_d. \end{array} \right.$$

$$= \frac{1}{2\pi \times 769\Omega \times 1\mu\text{F}}$$

$$f_c = 207 \text{ Hz} \quad \leftarrow \text{determines LF -3dB point.}$$

(b) Upper cutoff frequency: See pp. 621-623. The FET circuit is related to the equiv. HF circuit of the BJT common emitter amplifier (see prob. 9.54 solution):

i) Input $f_c = \frac{1}{2\pi R_g C_g}$

$$f_c = \frac{1}{2\pi \times 100\Omega \times 9.7\text{pF}} = 164 \text{ MHz}$$

$$\left\{ \begin{array}{l} R_g = R_s \parallel R_1 \parallel R_2 \approx 100\Omega \\ C_g = C_{gs} + (1+A)C_{gd} \\ A = g_m [r_d \parallel R_D \parallel R_L] \\ \quad = 0.8 \text{ mS} \times 2.31 \text{ k}\Omega \\ \quad = 1.85 \\ C_g = 4 \text{ pF} + 2.85 \times 2 \text{ pF} = 9.7 \text{ pF} \end{array} \right.$$

9.57 (b) ii) output circuit, again related to CE BJT analysis,

$$f_c = \frac{1}{2\pi R_T C_T}$$
$$= \frac{1}{2\pi \times 2.31 \text{ k}\Omega \times 4.1 \text{ pF}}$$

where $R_T = r_d \parallel R_D \parallel R_L = 2.31 \text{ k}\Omega$

$$C_T = C_{ds} + \frac{1+A}{A} C_{gd}$$
$$= 1 \text{ pF} + \frac{2.85}{1.85} \times 2 \text{ pF}$$
$$= 4.1 \text{ pF}$$

$f_c = 16.8 \text{ MHz}$ ← determines HF cutoff

(c) $BW = f_{c \text{ HIGH}} - f_{c \text{ LOW}} = 16.8 \text{ MHz}$