Find I_3, V_3 .Planar circuituse mesh
current
analysis.Define mesh currents i_1, i_2 as shown.Note $I_1 = i_1, I_2 = -i_2, I_3 = i_1 - i_2$.

USE KVL for the two loops:

$$V_A = V_1 + V_3$$

$$V_3 + V_2 = V_B$$

In terms of mesh currents,

$$V_1 = i_1 R_1, V_3 = (i_1 - i_2) R_3, V_2 = -i_2 R_2.$$

Two equations in two unknowns:

$$\left. \begin{aligned} i_1 R_1 + (i_1 - i_2) R_3 &= V_A \\ (i_1 - i_2) R_3 - i_2 R_2 &= V_B \end{aligned} \right\} \Rightarrow \begin{aligned} (R_1 + R_3) i_1 - R_3 i_2 &= V_A \\ R_3 i_1 - (R_2 + R_3) i_2 &= V_B \end{aligned}$$

Solve using Cramer's rule:

$$A = \begin{bmatrix} R_1 + R_3 & -R_3 \\ R_3 & -(R_2 + R_3) \end{bmatrix}$$

$$\Delta \equiv \det A =$$

$$= -(R_1 + R_3)(R_2 + R_3) + R_3^2$$

$$= -(R_1 R_2 + R_2 R_3 + R_1 R_3)$$

$$i_1 = \frac{\begin{vmatrix} V_A & -R_3 \\ V_B & -(R_2 + R_3) \end{vmatrix}}{\Delta}$$

$$i_2 = \frac{\begin{vmatrix} R_1 + R_3 & V_A \\ R_3 & V_B \end{vmatrix}}{\Delta}$$

$$i_1 = \frac{-V_A(R_2 + R_3) + V_B R_3}{-(R_1 R_2 + R_2 R_3 + R_1 R_3)}$$

$$i_2 = \frac{V_B(R_1 + R_3) - R_3 V_A}{-(R_1 R_2 + R_2 R_3 + R_1 R_3)}$$

$$i_1 = \frac{(R_2 + R_3)V_A - R_3 V_B}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

$$i_2 = \frac{R_3 V_A - (R_1 + R_3)V_B}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

check result:

$$I_1 = i_1 \quad I_2 = -i_2$$

Due to symmetry, the result for I_2 should equal the result for I_1 , if we swap V_A and V_B and also swap R_1 and R_2 .

$$I_1 = \frac{(R_2 + R_3)V_A - R_3 V_B}{R_1 R_2 + R_2 R_3 + R_1 R_3} \Rightarrow \begin{array}{l} V_A \leftrightarrow V_B \\ R_1 \leftrightarrow R_2 \\ I_1 \leftrightarrow I_2 \end{array}$$

$$\Rightarrow I_2 \stackrel{?}{=} \frac{(R_1 + R_3)V_B - R_3 V_A}{R_2 R_1 + R_2 R_3 + R_1 R_3}$$

$$I_2 = -i_2 = \frac{(R_1 + R_3)V_B - R_3 V_A}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$


agree so OK
so far.

Final desired results:

$$\left\{ \begin{array}{l} I_3 = i_1 - i_2 = \frac{(R_2 + R_3)V_A - R_3 V_B}{R_1 R_2 + R_2 R_3 + R_1 R_3} + \frac{(R_1 + R_3)V_B - R_3 V_A}{R_1 R_2 + R_2 R_3 + R_1 R_3} \\ \quad = \frac{R_2 V_A + R_1 V_B}{R_1 R_2 + R_2 R_3 + R_1 R_3} \\ V_3 = I_3 R_3 = \frac{R_2 R_3 V_A + R_1 R_3 V_B}{R_1 R_2 + R_2 R_3 + R_1 R_3} \end{array} \right.$$

Another approach:

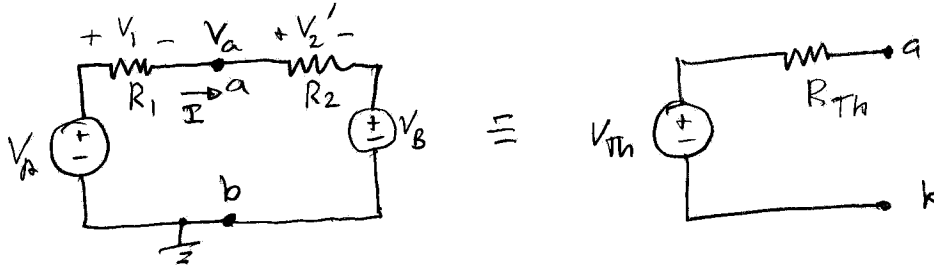Find Thévenin equivalent of circuit driving R_3 then use it to find I_3 and V_3 .



Find Open circuit voltage: $V_a \equiv V_{ab} = \text{open circuit voltage} = V_{Th}$

$$V_A = V_1 + V_2' + V_B = IR_1 + IR_2 + V_B$$


$$I = \frac{V_A - V_B}{R_1 + R_2}, \quad V_a \equiv V_{Th} = V_B + V_2' = V_B + IR_2$$

$$= V_B + \frac{V_A - V_B}{R_1 + R_2} R_2$$

$$= \frac{V_B R_1 + V_B R_2 + V_A R_2 - V_B R_2}{R_1 + R_2}$$


$$V_{Th} = \frac{R_2 V_A + R_1 V_B}{R_1 + R_2}$$

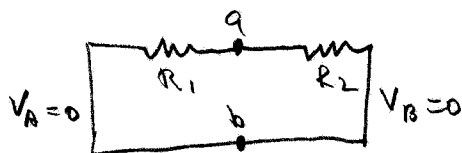Find Thévenin equiv. resistance by setting independent sources to 0 and finding resistance of network between a and b:



$$R_{Th} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

Now find I_3 :

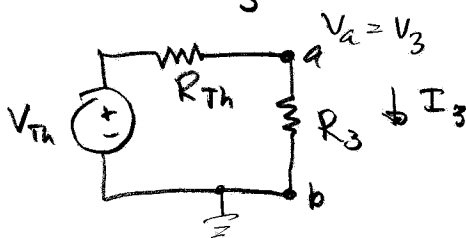

$$I_3 = \frac{V_{Th}}{R_{Th} + R_3} = \frac{\frac{R_2 V_A + R_1 V_B}{R_1 + R_2}}{\frac{R_1 R_2}{R_1 + R_2} + R_3}$$

$$I_3 = \frac{R_2 V_A + R_1 V_B}{R_1 R_2 + R_1 R_3 + R_2 R_3} \quad (\text{as before})$$

$$\text{and } V_3 = I_3 R_3 = \frac{R_2 R_3 V_A + R_1 R_3 V_B}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$