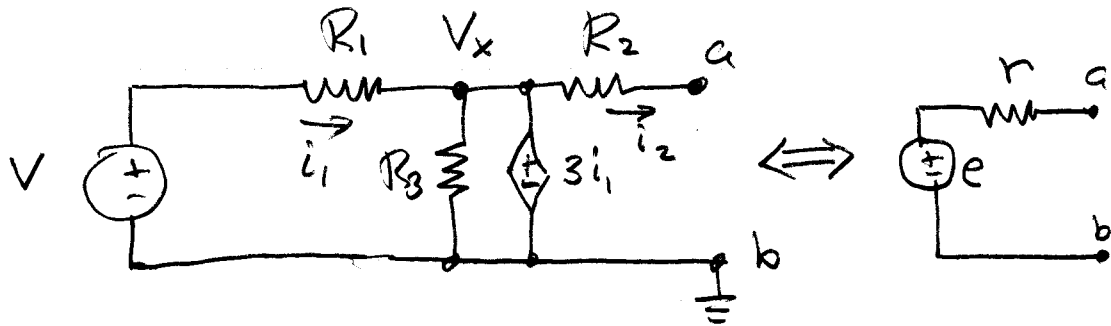


Find Thévenin equn: (3.I. units)



(4) Find $V_{oc} = V_{th} \equiv e$
 $= V_x$ since $i_2 = 0$


$$V - V_x = i_1 R_1, \quad V_x = 3i_1$$

$$V - V_x = \frac{V_x}{3} R_1$$

$$V_x = \frac{V}{1 + \frac{R_1}{3}} = \frac{3V}{R_1 + 3}$$

[note units:
 V_x (volts) = $3 \frac{\text{Volts}}{\text{Ampere}} i_1$ (A)]
 (unit is Ohms)

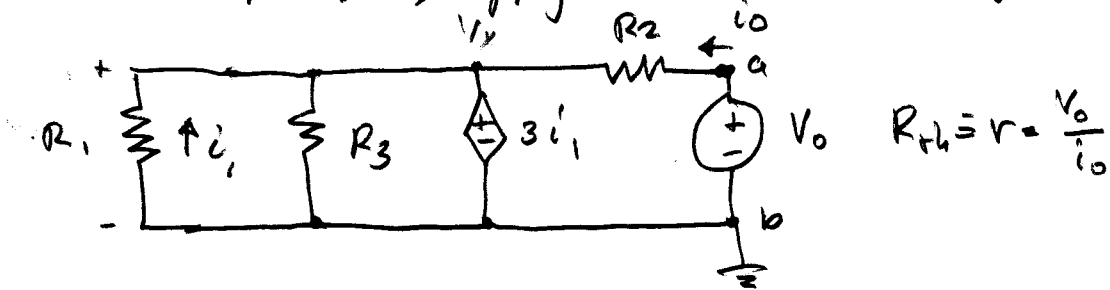(b) Find $R_{th} \equiv r$. Set indep. sources to 0, leave dep. as-is, apply source if necessary.



Eliminate V_x, i_1 , find $\frac{V_0}{i_0} \equiv r$.

$$\frac{V_0 - V_x}{R_2} = i_0, \quad V_x = 3i_1, \quad V_x = -i_1 R_1 \quad (\text{note sign})$$

$$3i_1 = -i_1 R_1 \Rightarrow i_1(3 + R_1) = 0$$

$$\Rightarrow i_1 = 0$$

(unless $R_1 = -3$)
(assume R is just a resistor)
(must be positive)


$$V_x = 3i_1 \Rightarrow V_x = 0.$$

$$V_0 = i_0 R_2 \Rightarrow \frac{V_0}{i_0} \equiv r = \underline{\underline{R_2}}.$$




Check simple case: $V = 1V$, $R_1 = R_2 = R_3 = 1\Omega$

Connect $R_{Load} = 1\Omega$

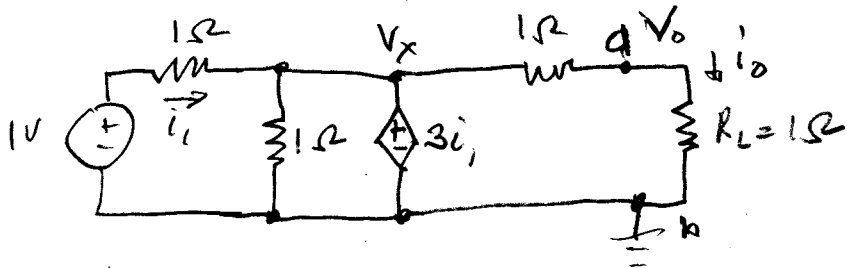
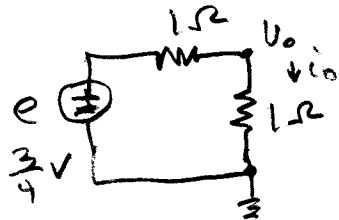
$$\left. \begin{aligned} \frac{1 - V_x}{1} = i_1, \quad V_x = 3(1)i_1 \\ 1 - V_x = \frac{V_x}{3} \Rightarrow V_x = \frac{3}{4}V \end{aligned} \right\} \begin{aligned} V_o &= \frac{1}{2} V_x = \frac{3}{8}V \\ i_o &= \frac{V_o}{R_L} = \frac{3}{8}A \end{aligned}$$



$$\begin{aligned} V_o &= \frac{3}{8}V \\ i_o &= \frac{3}{8}A \end{aligned}$$