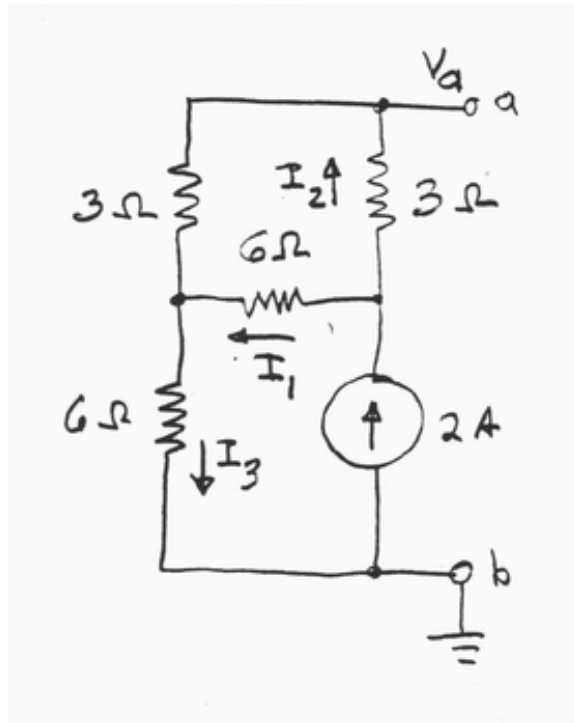



# Physics 116A: Exam 1

2/3/2000

Closed book and notes except for one  $8.5 \times 11$  in<sup>2</sup> sheet of paper. Show reasoning for full credit. There are 4 problems and 100 points.



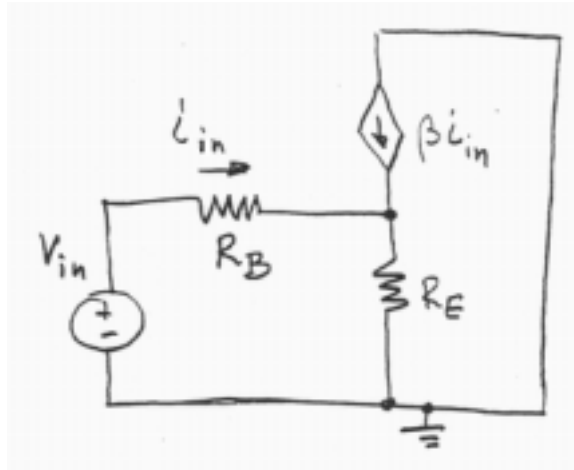
1. Consider the circuit above with node b taken as the reference node (“ground”).
  - (a) Find the currents,  $I_1$ ,  $I_2$  and  $I_3$ .
  - (b) Find the open-circuit voltage,  $V_{oc}$ , between the nodes a and b (i.e.,  $V_a$ ).
  - (c) Find the Thévenin equivalent of the circuit connected to the nodes a and b.
    - i. Does setting the current source to zero result in (a) a short circuit or (b) an open circuit in its place?
  - (d) Find the output voltage,  $V_a$ , if a  $6.75 \Omega$  resistor is connected between a and b.



2. For the circuit above,

- derive an expression for  $V_{in}$  in terms of  $i_{in}$ ,  $R_B$ ,  $R_E$  and  $\beta$ .
- Find the effective resistance,  $R_{eff} = \frac{V_{in}}{i_{in}}$ .
- Estimate  $R_{eff}$  for  $R_B = 2500 \Omega$ ,  $R_E = 200 \Omega$  and  $\beta = 100$ .

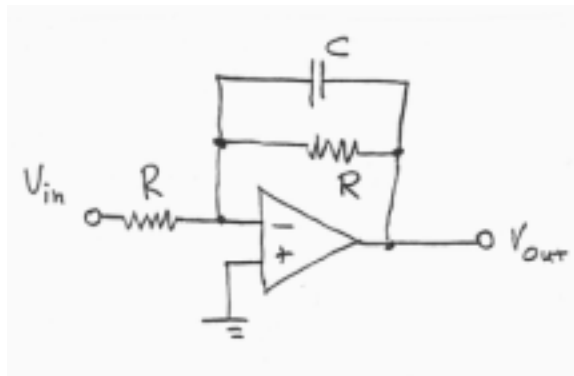
3. For the circuit below, assume the op-amp is ideal.



- Is there a *virtual ground* in this circuit, and if so, where?
- Find  $\mathbf{H}(j\omega) = \mathbf{V}_{out}/\mathbf{V}_{in}$ . Note that complex quantities are given in **boldface** type.
- Let  $\omega_0 = 1/RC$ . Find an expression for  $|\mathbf{H}(j\omega)|$  and approximate expressions when
  - $\omega \gg \omega_0$
  - $\omega \ll \omega_0$ .

How would you characterize this circuit as a filter circuit (e.g., high pass, low pass, band pass, etc.)?

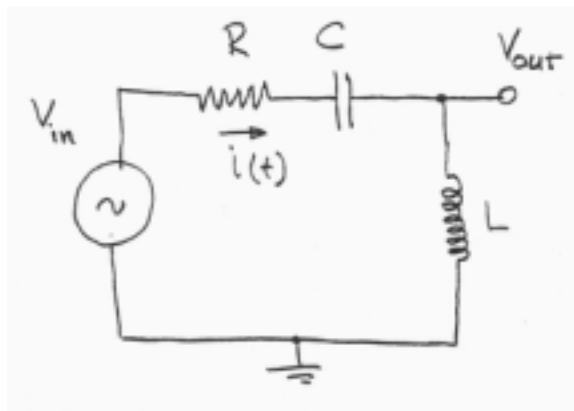- Suppose  $V_{in} = 2.0 \text{ V} \cos(\omega_0 t)$ . Find the amplitude and relative phase of the output voltage.



4. (a) For the circuit above, find an expression for  $\mathbf{H}(j\omega) = \mathbf{V}_{out}/\mathbf{V}_{in}$  in terms of  $\omega$ ,  $R$ ,  $L$  and  $C$ .
- (b) Let  $\omega_R = 1/\sqrt{LC}$ . Find  $|\mathbf{H}(\omega/\omega_R)|$ .
- (c) Find  $\mathbf{H}(s)$ .
- (d) Does  $\mathbf{H}(s)$  have any zeros? If so, where?
- (e) Suppose the circuit has  $L = 2.0$  mHy,  $R = 2.0 \Omega$  and  $C = 0.10 \mu\text{F}$ . Then  $f_R = \omega_R/2\pi = 11.3$  KHz and  $Q = 70.7$ . There is a sharp peak in a plot of the amplitude of the current against frequency. Estimate the full width of this peak at the half-power point.
- (f) For the values above, where would you expect the poles of  $\mathbf{H}(s)$  to be in the complex  $s$  plane among the following choices:
- on the negative real axis;
  - complex conjugate points in the left half-plane;
  - complex conjugate points on the imaginary axis;
  - none of the above.