
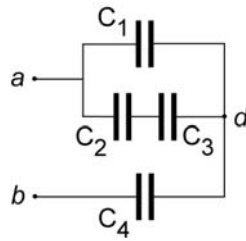


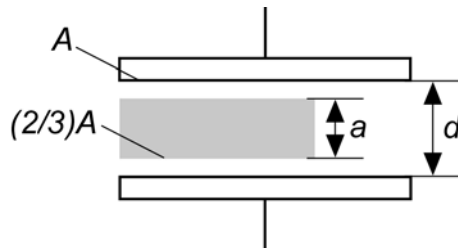
1. In the following circuit, $C_1 = C_2 = C_3 = C_4 = 8 \mu\text{F}$, and $V_{ab} = V_a - V_b = 20 \text{ V}$.
- (8 points) Find the equivalent capacitance between a and b ;
 - (8 points) Find the charge on each capacitor;
 - (4 points) Find the potential difference across each capacitor.




2. A slab of dielectric material with $\kappa = 6$, thickness a and area $(2/3)A$ is inserted between the plates of an air parallel-plate capacitor with plate area A and plate separation d . Here $d \geq a$.
- (10 points) Find the capacitance C of the capacitor in this arrangement in terms of the capacitance C_0 when the dielectric slab is removed;
 - (5 points) Find the capacitance C in terms of C_0 when $a = 0$;
 - (5 points) Find the capacitance C in terms of C_0 when $a = d$.



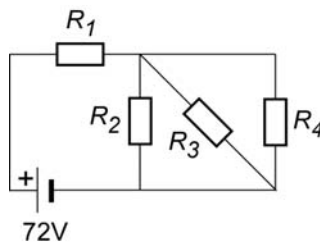3. In the following direct-current circuit, $R_1 = R_2 = R_3 = R_4 = 6 \Omega$, and $\mathcal{E} = 72 \text{ V}$ with negligible internal resistance.
- (10 points) find the power dissipated in R_1 and R_2 ;
 - (10 points) Now remove R_4 from the circuit, and find the current through each of the remaining three resistors.



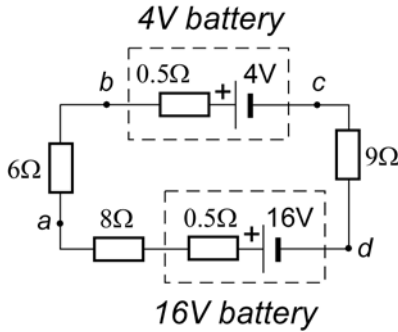4. In the following direct-current circuit,
- (a) (8 points) Find the magnitude and direction of the current in the circuit;
 - (b) (6 points) Find the terminal voltage of the 4V battery, $V_{bc} = V_b - V_c$;
 - (c) (6 points) Find the potential difference $V_{ad} = V_a - V_d$.



5. In the following direct-current circuit,
- (a) (10 points) Find the current (direction and magnitude) in each branch;
 - (b) (10 points) Find the potential difference $V_{ab} = V_a - V_b$.

