

Solutions to Physics 9C-A MT#2 (2016)

1-(a) Since $V_{10} = 120V = Q_{10}/C_{10}$,

$$Q_{10} = C_{10}V_{10} = 960 \mu C.$$

Since $V_{20} = 0 = Q_{20}/C_{20}$

$$Q_{20} = 0.$$

1-(b) From charge conservation, $Q_1 + Q_2 = Q_{10}$.
The potential drop $V_1 = V_2$, and is related to $Q_1 + Q_2 = Q_{10}$ through the network capacitance $C_{\text{network}} = C_{10} + C_{20}$ as

$$V_1 = V_2 = \frac{Q_1 + Q_2}{C_{\text{network}}} = \frac{Q_{10}}{C_{10} + C_{20}}$$
$$= \frac{960 \mu C}{8 \mu F + 4 \mu F} = 80V.$$

Thus

$$Q_1 = C_{10} \cdot V_1 = 640 \mu C$$

$$Q_2 = C_{20} \cdot V_1 = 320 \mu C.$$

1- (c) Again the charge conservation requires

$$Q_1 + Q_2 = Q_{i0} = 960 \mu\text{C}$$

But now $C_2 = kC_{20} = 8 \mu\text{C}$. As a result the network capacitance

$$C_{\text{network}} = C_{10} + C_2 = 16 \mu\text{C}$$

$$\text{Thus } V_1 = V_2 = \frac{Q_1 + Q_2}{C_{\text{network}}} = \frac{960 \mu\text{C}}{16 \mu\text{C}} = 60\text{V}$$

Sanity check:

$$Q_1 = C_{10} \cdot V_1 = 480 \mu\text{C}$$

$$Q_2 = C_2 \cdot V_2 = 480 \mu\text{C}$$

2-(a) C_1 and C_2 are parallel, thus

$$C_{ac} = C_{12} = C_1 + C_2 = 20 \mu\text{F}$$

C_{12} and C_3 are in series, thus

$$C_{ab} = C_{123} = \frac{C_{12} \cdot C_3}{C_{12} + C_3} = 4 \mu\text{F}$$

*

2-(b) Since $V_{ab} = 40\text{V}$,

$$Q_3 = (Q_1 + Q_2) = C_{123} \cdot V_{ab} = 160 \mu\text{C}$$

Then the potential drop across a b c

$$V_{ac} = (Q_1 + Q_2) / C_{ac} = Q_3 / C_{ac} = 8\text{V}$$

$$\therefore Q_1 = V_{ac} \cdot C_1 = 88 \mu\text{C}$$

$$Q_2 = V_{ac} \cdot C_2 = 72 \mu\text{C}$$

Alternative by

$$V_{ac} = V_{cb} - V_{cb} = V_{ab} - Q_3 / C_3 = 40\text{V} - 32\text{V} \\ = 8\text{V}$$

$$\therefore Q_1 = V_{ac} \cdot C_1 = 88 \mu\text{C}; Q_2 = V_{ac} \cdot C_2 = 72 \mu\text{C}$$

$$3-(a) \quad R_{12} = R_1 + R_2 = 12\Omega$$

$$R_{123} = \frac{R_{12} \cdot R_3}{R_{12} + R_3} = \frac{12\Omega \cdot 24\Omega}{36\Omega} = 8\Omega$$

$$R_{1234} = R_{123} + R_4 = 24\Omega = R_{ab}$$

$$3-(b) \quad P_{ab} = V_{ab}^2 / R_{ab} = \epsilon^2 / R_{ab} = 216 \text{ W}$$

$$3-(c) \quad I_4 = V_{ab} / R_{ab} = 3 \text{ A}$$

$$P_4 = I_4^2 R_4 = 144 \text{ W}$$

$$V_3 = V_1 + V_2 = I_4 \cdot R_{123} = \cancel{36} 24 \text{ V}$$

$$\therefore P_3 = V_3^2 / R_3 = 24 \text{ W}$$


$$I_{12} = (V_1 + V_2) / R_{12} = V_3 / R_{12} = 2 \text{ A}$$

$$\therefore P_1 = I_{12}^2 R_1 = 12 \text{ W}$$

$$P_2 = I_{12}^2 R_2 = 36 \text{ W}$$

$$P_1 + P_2 + P_3 + P_4 = 216 \text{ W}, \text{ same as in part 3(b)}$$

4-(a)

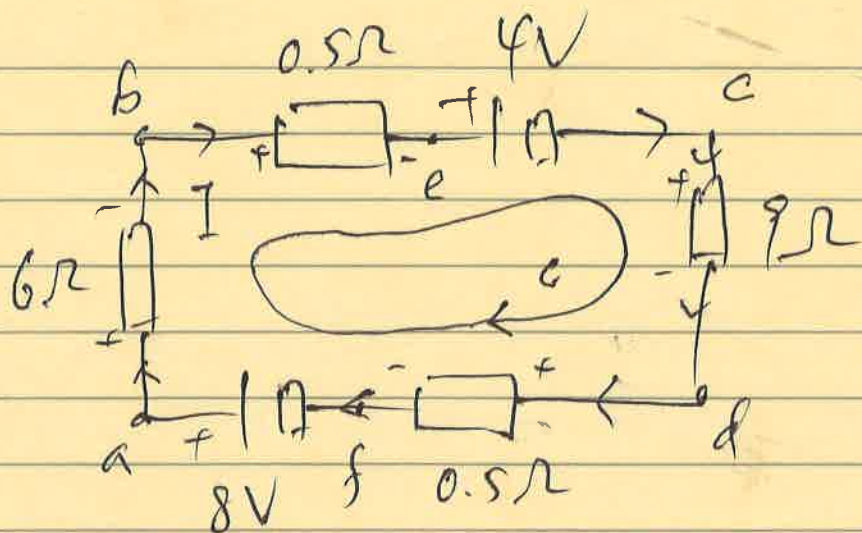

Assign I as indicated. Along a clockwise loop,

$$\oint_c \vec{E} \cdot d\vec{l} = \int_{abcdfa} \vec{E} \cdot d\vec{l}$$

$$= 6I + 0.5I + 4 + 9I + 0.5I - 8$$

$$= 0$$


$$\therefore 16I = 4$$

$I = 0.25 \text{ A}$ in the direction as assigned.

$$\begin{aligned} 4-(b) \quad V_{ac} &= V_a - V_c = V_{ab} + V_{bc} + V_{cd} = (6 + 0.5)I + 4 \\ &= 5\frac{5}{8} \text{ V} = 5.625 \text{ V} \end{aligned}$$

$$4-(c) \quad V_{bd} = V_{bc} + V_{cd} + V_{da} = (9.5) \cdot I + 4 = 6\frac{3}{8} \text{ V} = 6.375 \text{ V} \quad *$$

5-(a)

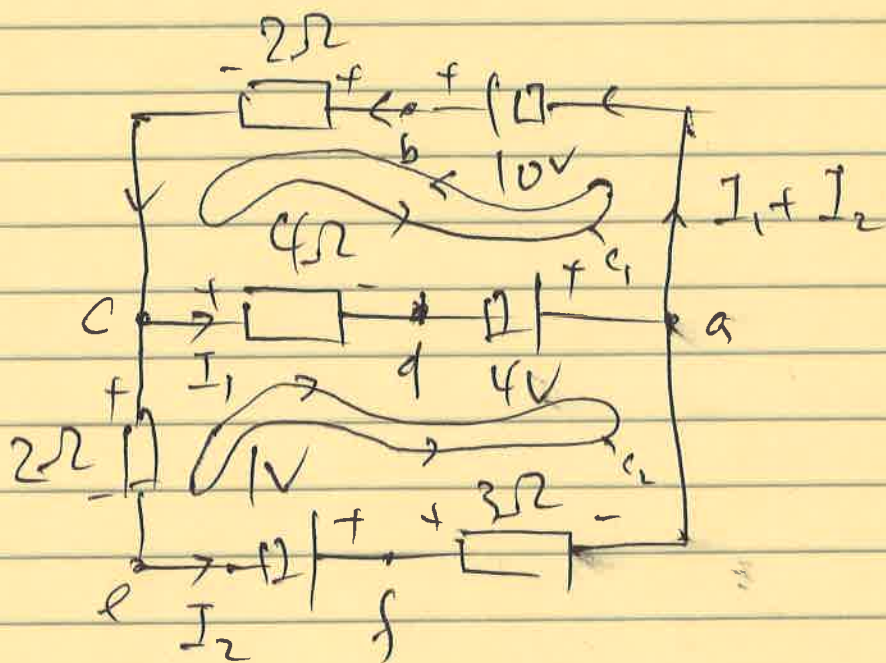

Assign two currents I_1 and I_2 as indicated.
Assign two clockwise loops c_1 and c_2 as indicated.

Along c_1 :

$$\oint_{c_1} \vec{E} \cdot d\vec{l} = 0 = \int_{abceda} \vec{E} \cdot d\vec{l}$$

$$= -10 + (I_1 + I_2) \cdot 2 + 4I_1 - 4 = 0$$

$$\therefore 6I_1 + 2I_2 = 14 \quad \text{or} \quad 3I_1 + I_2 = 7 \quad \dots \textcircled{1}$$

Along c_2 :

$$\oint_{c_2} \vec{E} \cdot d\vec{l} = 0 = \int_{adcefa} \vec{E} \cdot d\vec{l}$$

$$\oint \vec{E} \cdot d\vec{l} = 0 = 4 - 4I_1 + 2I_2 - 1 + 3I_2 = 0$$

adefca

$$\therefore 4I_1 - 5I_2 = 3 \dots \dots (2)$$

$$(1) \times 5 + (2):$$

$$19I_1 = 38 \dots \dots (3)$$

$$\therefore I_1 = \frac{2}{1} A \text{ as assigned in direction}$$

From Eq. (1):

$$I_2 = 7 - 3I_1 = 1 A \text{ as assigned in direction}$$

$$\therefore I_1 = 2A \text{ (through } 4\Omega)$$

$$I_2 = 1A \text{ (through } 2\Omega \text{ and } 3\Omega)$$

$$I_1 + I_2 = 3A \text{ (through } 2\Omega \text{ at the top)}$$

$$5-(b) \quad V_{df} = V_{da} + V_{af} = -4V - 3I_2 = -7V$$

✘