
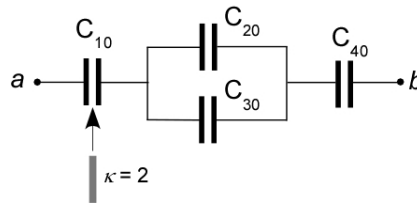


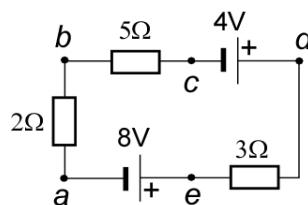1. Four *air-gapped* capacitors, $C_{10} = 10 \mu\text{F}$, $C_{20} = 5 \mu\text{F}$, $C_{30} = 15 \mu\text{F}$, and $C_{40} = 20 \mu\text{F}$ are connected as shown in the following figure. A battery maintains a potential difference $V_{ab} = +60 \text{ V}$ between a and b . Initially the dielectric slab with $\kappa = 2$ is not inserted in C_{10} .




- (a) **(5 points)** Find the equivalent capacitance between a and b .;
- (b) **(10 points)** Find the potential difference across C_{10} and C_{20} ;
- (c) **(10 points)** Find energies stored on C_{20} and C_{30} ;
- (d) **(10 points)** Maintaining the potential difference $V_{ab} = +60 \text{ V}$, insert the dielectric slab with $\kappa = 2$ to *fill* the air-gap in C_{10} and make it C_1 . Find the potential drop across C_1 now.
- (e) **(Extra 10 points)** For Part (d), before the dielectric slab is inserted, the capacitor network between a and b is first disconnected from the battery. Now the dielectric slab is inserted in C_{10} . Find the potential drops across C_1 and C_{40} .

2. In the following circuit,




- (a) **(10 points)** Find the direction and magnitude of the current in the circuit;
- (b) **(5 points)** Find the energy dissipated in the 5Ω resistor;
- (c) **(5 points)** Find the potential difference $V_{ad} = V_a - V_d$.

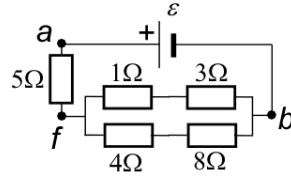3. In the following circuit, $\varepsilon = +16\text{V}$,



- (a) **(10 points)** Find the network resistance R_{ab} ;
 (b) **(5 points)** Find the potential drop across the 5Ω resistor;
 (c) **(10 points)** Find the current and power dissipated in the 8Ω resistor;
 (d) **(Extra 5 points)** Explicitly show that the sum of the power dissipated in all five resistors equals to the power dissipated in the network resistor R_{ab} .

4. In the following circuit,

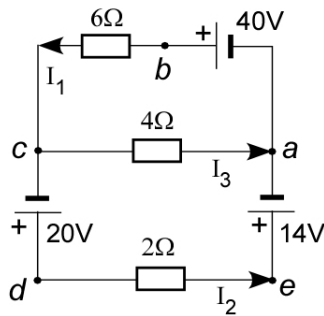

- (a) **(15 points)** Find the currents through all three resistors;
 (b) **(5 points)** Find the potential difference $V_{bd} = V_b - V_d$.