

Physics 9HD, Problem Set 5, due Mon. Nov. 2, 2009, 5:00 p.m.

Purcell 4.1, 4.8, 4.17, 4.20, 4.21, 4.22

Additional Problem:

Find the current in every branch and the voltage at every node in the following circuit.

